

# Frequency Compensation

M Sai Mehar\*

Parameter	Value
$C_1$	$150pF$
$C_2$	$5pF$
$g_m$	$40mA/V$
$f_1$	$10^5Hz$
$f_2$	$10^6Hz$
$f_3$	$2 \times 10^6Hz$

TABLE 0: Uncompensated System.

An op amp with an open loop voltage gain of 80dB and poles at  $10^5Hz$ ,  $10^6Hz$  and  $2 \times 10^6Hz$  is said to be compensated to be stable for unity  $\beta$ . Assume that op amp incorporates an amplifier circuit equivalent to Fig. 0 with input parameters in Table 0

where  $f_1$  is caused by input circuit and  $f_2$  by the output circuit of this amplifier. Find the required value of compensating miller capacitance  $C_f$  and the new frequency of the output pole

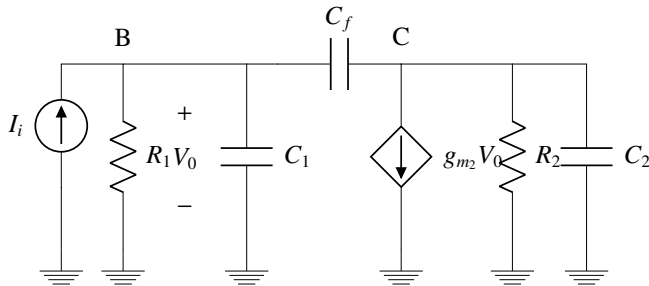


Fig. 0: Equivalent amplifier circuit

1 WITHOUT COMPENSATION:  $C_f = 0$

1.1. Find the gain of the opamp  $G(s)$  and draw the block diagram of the unity feedback system.

**Solution:** The transfer function of the opamp is

$$G(s) = \frac{10^4}{\left(1 + \frac{s}{2\pi \times 10^5}\right) \left(1 + \frac{s}{2\pi \times 10^6}\right) \left(1 + \frac{s}{2\pi \times 2 \times 10^6}\right)} \quad (1.1.1)$$

The block diagram is available in Fig. 1.1

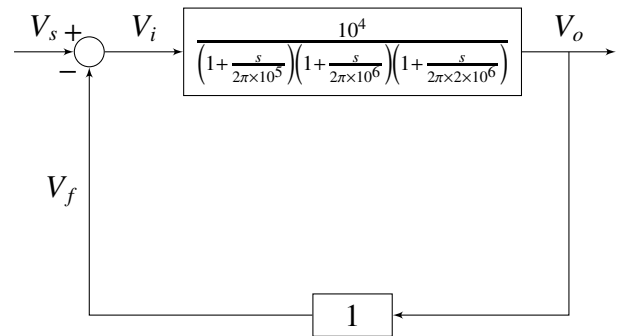


Fig. 1.1

1.2. Design the feedback circuit

**Solution:** See Fig. 1.2

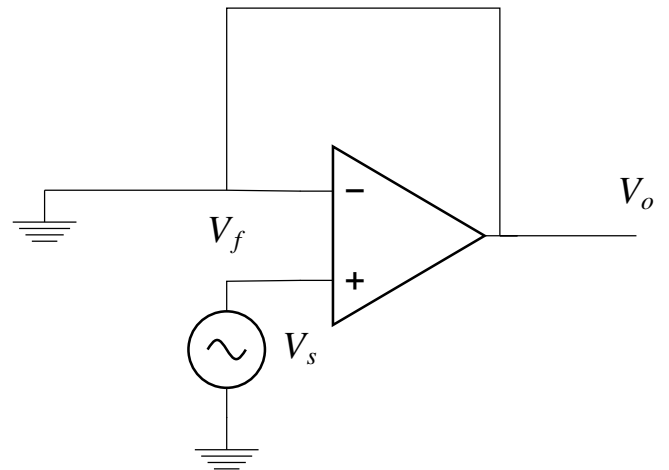


Fig. 1.2

1.3. Find  $\frac{V_o}{I_i}$  in Fig. 0 for  $C_f = 0$ .

**Solution:**

$$\frac{V_o}{I_i} = \frac{-g_m R_1 R_2}{1 + sP + s^2Q} \quad (1.3.1)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

Parameter	Value
$R_1$	$10.61k\Omega$
$R_2$	$31.8k\Omega$

TABLE 1.5: Resistance values in Fig. 0

where

$$P = C_1 R_1 + C_2 R_2 \quad (1.3.2)$$

$$Q = C_1 C_2 R_1 R_2 \quad (1.3.3)$$

- 1.4. Let  $\omega_1, \omega_2$  be the poles in (1.3.1). Find  $\omega_1$  and  $\omega_2$ .

**Solution:** From (1.3.1),

$$1 + sP + s^2Q = \left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right) \quad (1.4.1)$$

$$P \Rightarrow \frac{1}{\omega_1} + \frac{1}{\omega_2} \quad (1.4.2)$$

$$Q = \frac{1}{\omega_1 \omega_2} = Q \quad (1.4.3)$$

yielding

$$\omega_1 = \frac{1}{R_1 C_1} \quad (1.4.4)$$

$$\omega_2 = \frac{1}{R_2 C_2}$$

- 1.5. Find the values of  $R_1$  and  $R_2$

**Solution:** From (1.4.4)

$$R_1 = \frac{1}{2\pi C_1 f_1} \quad (1.5.1)$$

$$R_2 = \frac{1}{2\pi C_2 f_2} \quad (1.5.2)$$

which can be computed using the parameters in Table 2.3 and are listed in Table 1.5

- 1.6. Investigate the stability of the closed loop system in Fig. 1.1 by finding the step response of Fig. 1.2 using spice.

**Solution:** The following netlist simulates the uncompensated system

```
codes/ee18btech11029/spice/
ee18btech11029_2.net
```

The following code plots the output of the uncompensated system generated by the above netlist in Fig.1.6

```
codes/ee18btech11029/spice/
ee18btech11029_2.py
```

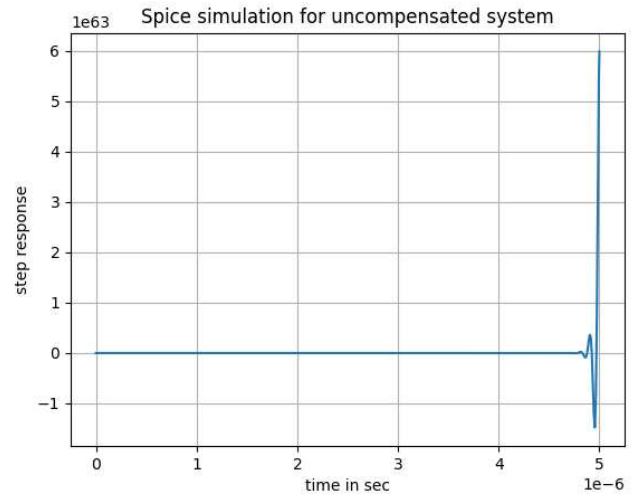


Fig. 1.6: Step response of Uncompensated system

## 2 WITH COMPENSATION: $C_f \neq 0$

- 2.1. Find  $\frac{V_o}{I_i}$  in Fig. 0 for  $C_f \neq 0$ .

**Solution:**

$$\frac{V_0}{I_i} = \frac{(sC_f - g_m)R_1 R_2}{1 + sP + s^2Q} \quad (2.1.1)$$

where

$$P = C_1 R_1 + C_2 R_2 + C_f (g_m R_1 R_2 + R_1 + R_2) \quad (2.1.2)$$

$$Q = (C_1 C_2 + C_f (C_1 + C_2)) R_1 R_2 \quad (2.1.3)$$

- 2.2. Let  $\omega_1, \omega_2$  be the poles in (2.1.1). Find  $\omega_1$  and  $\omega_2$ .

**Solution:**

$$1 + sP + s^2Q = \left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right) \quad (2.2.1)$$

$$\Rightarrow \frac{1}{\omega_1} + \frac{1}{\omega_2} = P \quad (2.2.2)$$

$$\text{or, } \frac{1}{\omega_1} \approx P \because (\omega_1 < \omega_2) \quad (2.2.3)$$

From (2.1.2), assuming that  $g_m \gg 1$ ,

$$P \approx C_f g_m R_1 R_2 \quad (2.2.4)$$

$$\Rightarrow \omega_1 = \frac{1}{P} = \frac{1}{C_f g_m R_1 R_2} \quad (2.2.5)$$

From (2.2.1),

Parameter	Value
$C_f$	$58.9pF$
$f_1$	$200Hz$
$f_2$	$37.95MHz$

TABLE 2.4: Compensated System

$$Q = \frac{1}{\omega_1 \omega_2} \quad (2.2.6)$$

$$\Rightarrow \omega_2 = \frac{1}{Q\omega_1} = \frac{g_m C_f}{C_1 C_2 + C_f (C_1 + C_2)} \quad (2.2.7)$$

upon substituting from (2.1.3) and (2.2.5).

2.3. For the compensated system, let

$$f_1 = \frac{f_3}{G} \quad (2.3.1)$$

$$= \frac{2 \times 10^6}{10^4} = 200Hz \quad (2.3.2)$$

Find the value of Miller capacitance  $C_f$ .

**Solution:** From (2.2.5),

$$C_f = \frac{1}{2\pi g_m R_1 R_2 f_1} \quad (2.3.3)$$

$$\Rightarrow C_f = 58.9pF \quad (2.3.4)$$

upon substituting the values from Tables and 1.5.

2.4. Find  $f_2$ .

**Solution:** From (2.2.7),

$$f_2 = \frac{g_m C_f}{2\pi [C_1 C_2 + C_f (C_1 + C_2)]} \quad (2.4.1)$$

$$f_2 = 37.95MHz \quad (2.4.2)$$

All unknown parameters for the compensated system are listed in Table 2.4

2.5. Find  $G(s)$  for the compensated system and sketch the block diagram.

**Solution:** The transfer function of the opamp is

$$G(s) = \frac{10^4}{\left(1 + \frac{s}{2\pi \times 200}\right) \left(1 + \frac{s}{2\pi \times 37.95 \times 10^6}\right) \left(1 + \frac{s}{2\pi \times 2 \times 10^6}\right)} \quad (2.5.1)$$

and the block diagram is available in Fig. 2.5

2.6. Through Bode plots, show how  $C_f$  affects  $G(s)$

**Solution:**

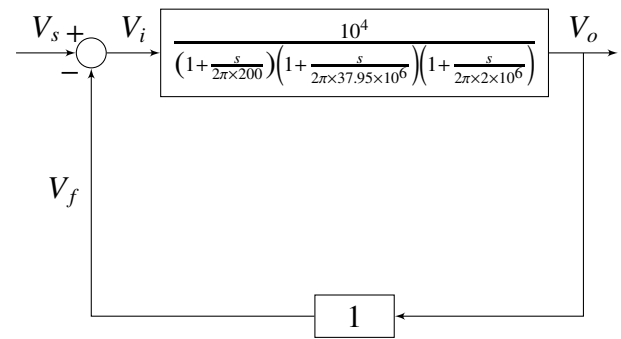


Fig. 2.5: Compensated system

- $C_f$  downshifts the first pole by factor of  $\frac{10^5}{200} = 500$
- $C_f$  upshifts the second pole by factor of  $\frac{37.95 \times 10^6}{10^6} = 37.95$

This is visible in Fig. 2.6 plotted using

codes/ee18btech11029/ee18btech11029\_1.py

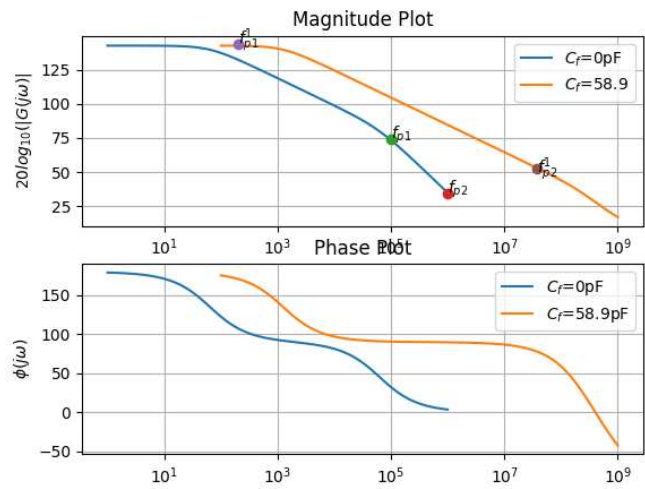


Fig. 2.6

2.7. Show that the compensated system is stable by plotting the step response. **Solution:** The following netlist simulates the compensated system

codes/ee18btech11029/spice/  
ee18btech11029\_3.net

The following code plots the output of the compensated system generated by the above netlist in Fig.2.7

codes/ee18btech11029/spice/  
ee18btech11029\_3.py

Instructions for simulations are given in  
`codes/ee18btech11029/spice/README.md`

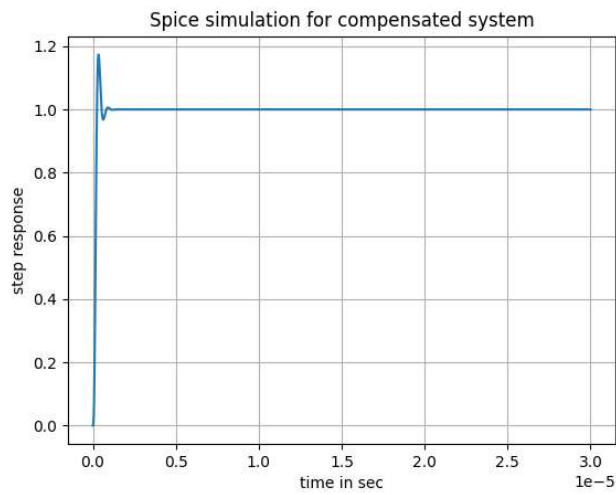


Fig. 2.7: Step response of compensated system