

Trans-Resistance Amplifier

Sudeep Veggalam*

CONTENTS

For the feedback transresistance amplifier in Fig. , use small-signal analysis to find the open-loop gain G , the feedback H , and the closed loop gain G_m . Neglect r_o of each of the transistors and assume $R_C \ll \beta_2 R_E$ and $R_E \ll R_F$, and that the feedback causes the signal voltage at the input node to be nearly zero. Evaluate $\frac{V_o}{I_s}$ for the following component values: $\beta_1 = \beta_2 = 100$, $R_C = R_E = 10k\Omega$ and $R_F = 100k\Omega$.

1. Draw the small-signal equivalent of the circuit in Fig.??.

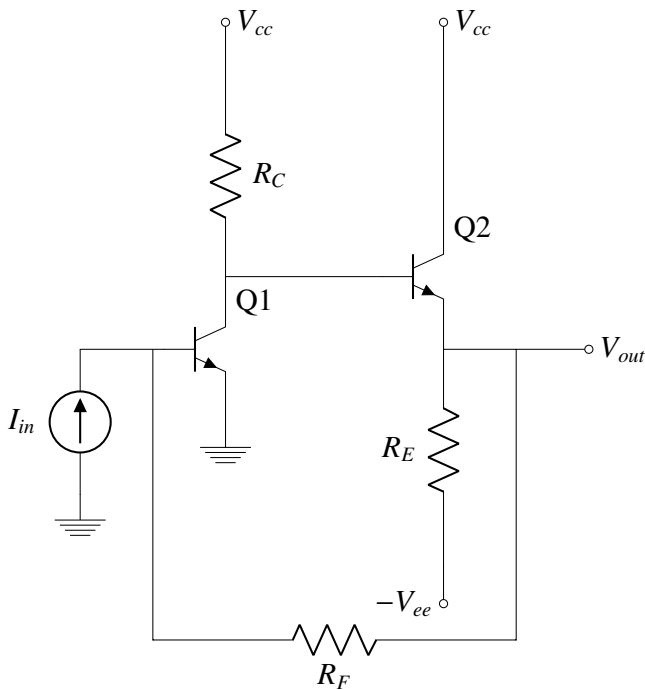


Fig. 1

Solution:

The equivalent circuit is Fig.??

2. Find the expression for the open loop Gain(G) of the system.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

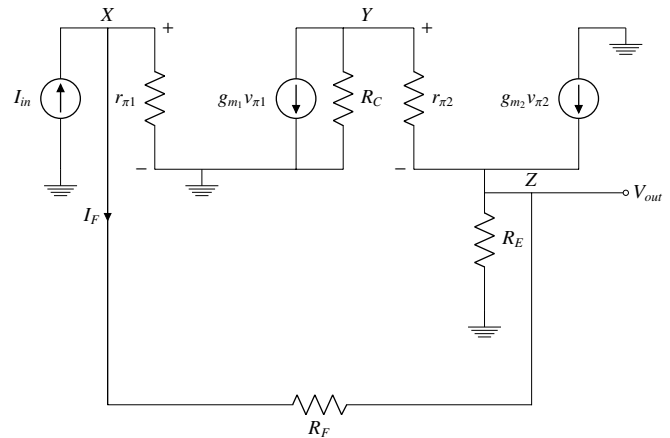


Fig. 1

Solution:

The given system is a cascaded system of Q_1 and Q_2 . The signal flow graph is illustrated in Fig. ??

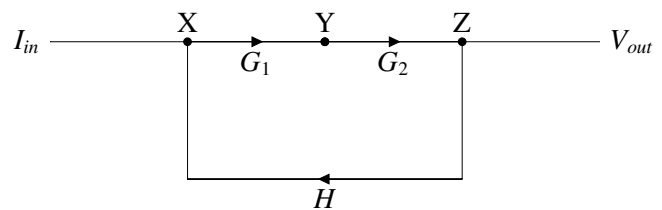


Fig. 2

So, if the gain of Q_1 and Q_2 are G_1 and G_2 respectively, the open-loop gain (G) is given by:

$$G = G_1 G_2 \quad (2.1)$$

Q_1 is in CE(Common-emitter) stage. The input signal is I_{in} . From fig. ??,

$$I_X = I_{in} \quad (2.2)$$

$$\beta = \frac{I_c}{I_b} \quad (2.3)$$

Applying Kirchoff's Law in the loop connect-

ing Y to ground,

$$\Rightarrow V_Y = \beta I_{in} R_C \quad (2.4)$$

$$G_1 = \frac{V_{out}}{I_{in}} = \frac{V_Y}{I_X} \quad (2.5)$$

$$= \beta R_C \quad (2.6)$$

Q_2 is in emitter follower topology.

$$V_{\pi 2} = V_Y - V_Z \quad (2.7)$$

Applying Kirchoff's Law,

$$\frac{V_Y - V_Z}{r_\pi} + g_{m2}(V_Y - V_Z) = \frac{V_Z}{R_E} \quad (2.8)$$

$$\Rightarrow \frac{V_Z}{V_Y} = \frac{R_E}{\frac{1}{g_{m2}} + R_E} \quad (2.9)$$

$$\Rightarrow G_2 = \frac{R_E}{\frac{1}{g_{m2}} + R_E} \quad (2.10)$$

From (??), the open loop gain (G):

$$G = (\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right) \quad (2.11)$$

3. Find the feedback factor(H) of the given circuit.

Solution:

From Fig.??, the feedback circuit consists of only a resistor R_F :

$$\therefore H = \frac{I_F}{V_{out}} = \frac{1}{R_F} \quad (3.1)$$

4. Find the closed loop gain of the system.

Solution:

The closed loop gain of a system is given by:

$$G_L = \frac{G}{1 + GH} \quad (4.1)$$

From (??) and (??). The closed loop gain of the circuit is given by:

$$G_L = \frac{(\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right)}{1 + \frac{(\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right)}{R_F}} \quad (4.2)$$

$$= \frac{R_F R_C R_E \beta}{\beta R_C R_E + R_F \left(\frac{1}{g_{m2}} + R_E \right)} \quad (4.3)$$

5. Find G,H and G_L for the given problem. Parameters are summarised in table ??.

Parameters	Value
V_{cc}	5V
β_1	100
β_2	100
R_C	10K Ω
R_E	10K Ω
R_F	100K Ω

TABLE 5

Solution:

To calculate the bias values of Q1, Q2. Remove the input and output, the resultant circuit is shown in fig.??

Applying KVL to the circuit, we get:

$$0.7 + I_{b1} R_F + (I_{b1} - (\beta + 1) I_{b2}) R_E = -V_{ee} \quad (5.1)$$

$$0.7 + I_{b1} R_F + 0.7 + (\beta I_{b1} + I_{b2}) R_C = V_{cc} \quad (5.2)$$

Solving the above equations, we get:

$$I_{b1} = \frac{\frac{V_{cc}-1.4}{R_C} - \frac{V_{ee}+0.7}{R_E(\beta+1)}}{\frac{R_F+\beta R_C}{R_C} + \frac{R_E+R_F}{R_E(\beta+1)}} \quad (5.3)$$

$$= 3.22 * 10^{-6} \quad (5.4)$$

$$I_{b2} = \frac{\frac{V_{cc}-1.4}{\beta R_C + R_F} + \frac{V_{ee}+0.7}{R_E+R_F}}{\frac{R_C}{R_F+\beta R_C} + \frac{R_E(\beta+1)}{R_E+R_F}} \quad (5.5)$$

we know,

$$g_m = \frac{I_c}{V_T} \quad (5.6)$$

where, $V_T = 26\text{mV}$, and

$$r_\pi = \frac{\beta}{g_m} \quad (5.7)$$

$$\therefore g_{m1} = \frac{\beta I_{b1}}{V_T} \quad (5.8)$$

$$= 0.0123 \quad (5.9)$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} \quad (5.10)$$

$$= 8130\Omega \quad (5.11)$$