# Phase Margin

## Pedavegi Aditya\*

Consider an op amp having a single pole open loop response  $G_0 = 10^5$  and  $f_p = 10$  Hz. Let the OPAMP be ideal connected in non-inverting terminal with a nominal low frequency of closed loop gain of 100

- (a) A manufacturing error introducing a second pole at 10 kHz. Find the frequency at which |GH| = 1 and the corresponding phase margin.
- (b) For what values of H is the phase margin greater than  $45^{\circ}$ ?
- 1. Find the transfer function of the two pole OPAMP.

**Solution:** For a two-pole amplifier open loop transfer function is

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)} \tag{1.1}$$

Poles are at  $f_1 = 10$  and  $f_2 = 10^4$ 

$$G(f) = \frac{G_0}{\left(1 + J\frac{f}{f_0}\right)\left(1 + J\frac{f}{f_0}\right)} \tag{1.2}$$

$$= \frac{10^5}{\left(1 + J\frac{f}{10}\right)\left(1 + J\frac{f}{10^4}\right)} \tag{1.3}$$

2. Find the feedback *H*.

**Solution:** Since the closed loop gain

$$|T| = 100$$
 (2.1)

and for nominal low frequency  $|GH| \gg 1$ ,

$$H \approx \frac{1}{|T|} = 0.01 \tag{2.2}$$

3. Find the PM and the crossover frequency.

**Solution:** From (1.3) and (2.2)

$$|GH| = 1 \tag{3.1}$$

1

$$\implies \frac{10^3}{\left(\sqrt{1 + \frac{f^2}{100}}\right)\left(\sqrt{1 + \frac{f^2}{10^8}}\right)} = 1 \tag{3.2}$$

or 
$$f_{180} = 7.8615 \, kHz$$
. (3.3)

using the following python code.

codes/ee18btech11034/ee18btech11034.py

From (1.3), ::  $/H = 0^{\circ}$ ,

$$/G(f)H(f) = /G(f) \tag{3.4}$$

$$-\tan^{-1}\left(\frac{f}{10}\right) - \tan^{-1}\left(\frac{f}{10^4}\right)$$
 (3.5)

$$\implies PM = 180^{\circ} + /G(f_{180})$$
 (3.6)

$$= 180^{\circ} - 128.1^{\circ} = 51.9^{\circ} \tag{3.7}$$

4. Verify your result using a Bode plot.

**Solution:** The following code generates Fig. 4

codes/ee18btech11034/ee18btech11034\_1.py


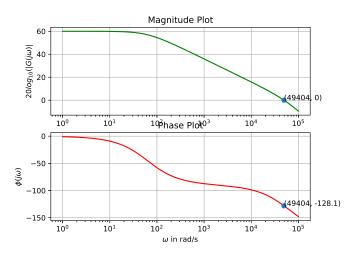


Fig. 4

<sup>\*</sup>The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

5. Realise the above system with  $PM = 51.9^{\circ}$  using a feedback circuit.

#### **Solution:**

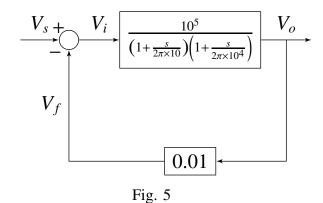

The transfer function of OPAMP is


$$G(s) = \frac{10^5}{\left(1 + \frac{s}{2\pi \times 10}\right)\left(1 + \frac{s}{2\pi \times 10^4}\right)}$$
 (5.1)

6. For the feedback gain H
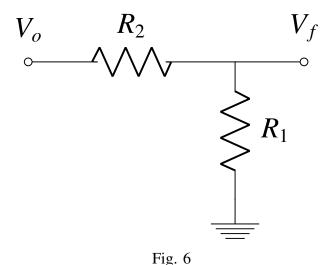
#### **Solution:**

Choose a resistance network such that

$$H = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \approx 0.01 \tag{6.1}$$



Choose  $R_1$  and  $R_2$  as

$$R_1 = 10\Omega \tag{6.2}$$

$$R_2 = 990\Omega \tag{6.3}$$

$$H = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 990} = 0.01 \tag{6.4}$$

7. Feedback Circuit for  $PM = 51.9^{\circ}$  Solution:

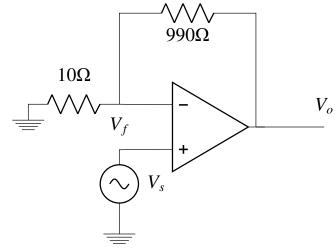


Fig. 7

8. Verification using spice circuit simulation **Solution:** For H = 0.01 the closed loop response is

$$|T| \approx \frac{1}{H} = 100 \tag{8.1}$$

The following is the netlist file for spice

spice/ee18btech11034/ee18btech11034\_1.net


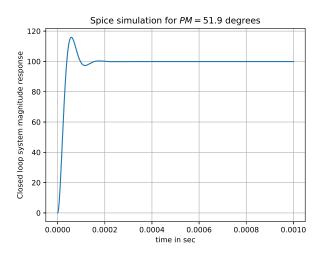


Fig. 8

The following python code plots the closed loop step response verses time

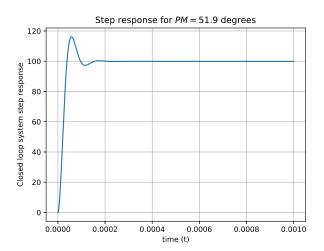9. Verification of step response through python **Solution:** For H = 0.01 step response through python



The following python code is for the above verification

Fig. 9

From Fig.8 and Fig.9 we can see the circuit simulation output and python output are same for step signal input.

10. Find H such that  $PM = 45^{\circ}$ .

**Solution:** From (3.4), assuming constant H,

$$\underline{/G(f_{180})} = 45^{\circ} - 180^{\circ} = -135^{\circ}$$

(10.1)

$$\implies -\tan^{-1}\left(\frac{f}{10}\right) - \tan^{-1}\left(\frac{f}{10^4}\right) = -135^{\circ}$$
(10.2)

$$\implies \frac{\frac{f}{10} + \frac{f}{10^4}}{1 - \frac{f^2}{10^5}} = -1 \quad (10.3)$$

or, 
$$f_{180} \approx 10 \, kHz$$
 (10.4)

From (1.3),

$$: |G(f_{180})H| = 1, (10.5)$$

$$\frac{\left(10^{5}\right)H}{\left(\sqrt{1+\frac{10^{8}}{100}}\right)\left(\sqrt{1+\frac{10^{8}}{10^{8}}}\right)} = 1$$

$$\implies H = 1.414 \times 10^{-2}$$

$$\Rightarrow H = 1.414 \times 10 \tag{10.7}$$

or, 
$$H_{max} = 1.414 \times 10^{-2}$$
 (10.8)

which is the value of H for which  $PM > 45^{\circ}$ .

11. Verify the above using a Bode plot.

**Solution:** The following code plots Fig. 11.

codes/ee18btech11034/ee18btech11034 2.py


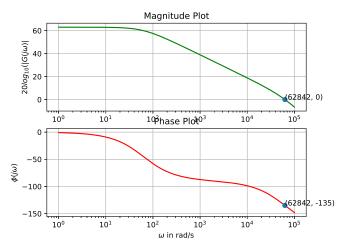


Fig. 11

12. Realise the above system with  $PM = 45^{\circ}$  using a feedback circuit.

### **Solution:**

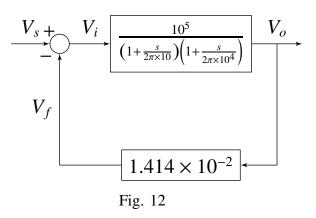

13. For the feedback gain H **Solution:** 

$$R_1 = 10\Omega \tag{13.1}$$

$$R_2 = 700\Omega \tag{13.2}$$

$$H = \frac{R_1}{R_1 + R_2} \implies \frac{10}{10 + 700} \approx 1.41 \times 10^{-2}$$
 (13.3)

14. Feedback Circuit for  $PM = 45^{\circ}$  Solution:

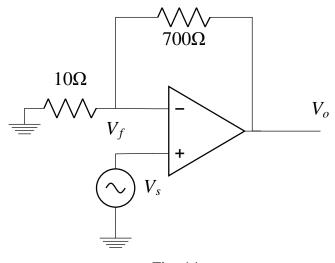


Fig. 14

15. Verification using spice circuit simulation **Solution:** For H = 0.014 the closed loop response is

$$|T| \approx \frac{1}{H} = 70.72 \tag{15.1}$$

The following is the netlist file for spice

spice/ee18btech11034/ee18btech11034\_2.net

The following python code plots the closed loop step response verses time

16. Verification of step response through python **Solution:** For H = 0.014 step response through python The following python code is for the above verification

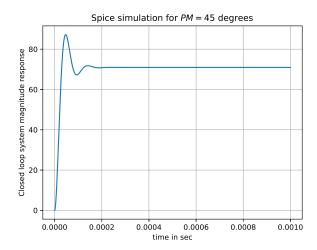


Fig. 15

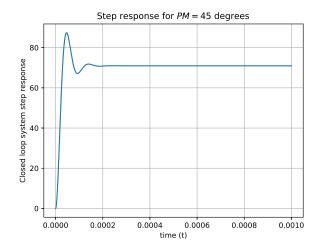


Fig. 16

From Fig.15 and Fig.16 we can see the circuit simulation output and python output are same for step signal input.

Follow the instructions in below file for running spice files

spice/ee18btech11034/README.md

17. Check for unstability

**Solution:** For a closed loop system to be unstable PM of GH is negative

$$PM < 0^{\circ} \tag{17.1}$$

$$\implies /G(f)H(f) < -180^{\circ} \tag{17.2}$$

For the given GH

$$\frac{/G(f)H(f)}{/G(f)H(f)} = \frac{/G(f)}{10} - \tan^{-1}\left(\frac{f}{10^4}\right) - \tan^{-1}\left(\frac{f}{10^4}\right)$$
(17.4)

At 
$$f = \infty$$

$$/G(f) = -90^{\circ} - 90^{\circ} = -180^{\circ}$$
 (17.5)

So there will be no positive f where  $\underline{/G(f)}$  <  $-180^{\circ}$ 

Hence,the system is stable for any constant feedback gain H