

# Oscillator

Ayush kumar\*

For the circuit shown in Fig. 1.1, find the loop gain  $L(s) = G(s)H(s)$ ,  $L(j\omega)$ , the frequency for zero loop phase, and  $R_2/R_1$  for oscillation.

1. Draw the equivalent control system representation for the circuit in Fig. 1.1 as well as the small signal model.

**Solution:** See Figs. 1.2, 1.3 and 1.4. Oscillators do not include input signal.

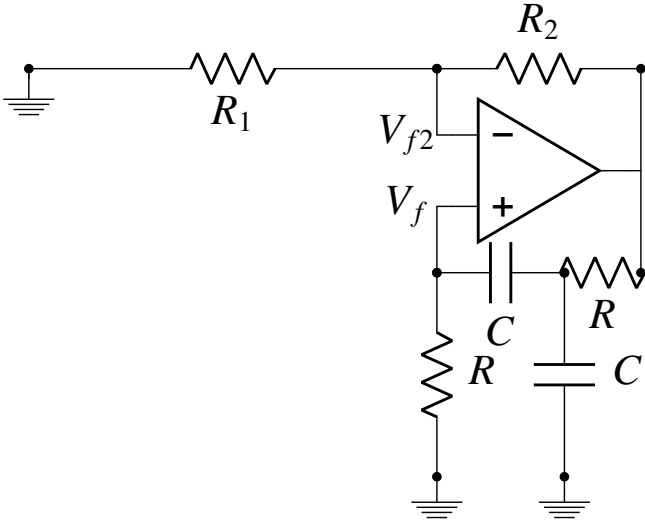


Fig. 1.1

2. Draw the block diagram and circuit diagram for  $H$ .

**Solution:** See Figs. 2.5 and 2.6.

3. Find  $H$ .

**Solution:** In Fig. 2.6, let  $I_o$  be the current flowing from  $V_o$ . Then

$$I_o = \frac{V_o}{R + \frac{1}{sc} \parallel \left( \frac{1}{sc} + R \right)} \quad (3.1)$$

Using current division,

$$V_f = I_o \frac{\frac{1}{sc}}{\frac{1}{sc} + \left( \frac{1}{sc} + R \right)} \times R \quad (3.2)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

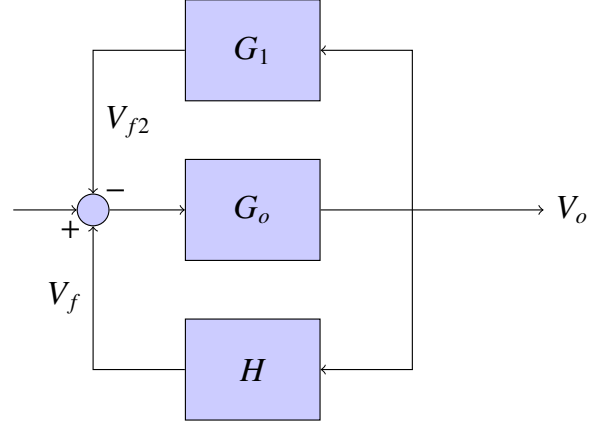


Fig. 1.2: Block diagram

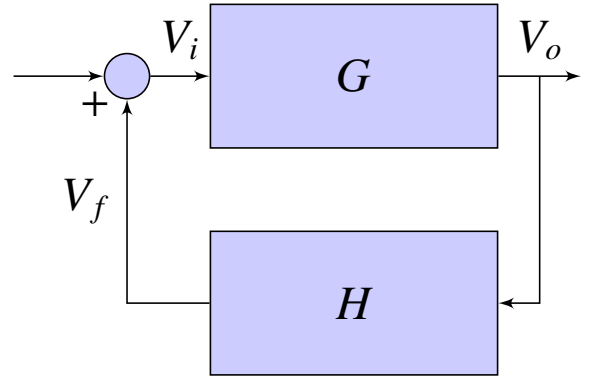


Fig. 1.3: Simplified equivalent block diagram

From (3.1) and (3.2),

$$\frac{V_f}{V_o} = \frac{\frac{1}{sc}}{\frac{1}{sc} + \left( \frac{1}{sc} + R \right)} \times R \quad (3.3)$$

$$\times \frac{1}{R + \frac{1}{sc} \parallel \left( \frac{1}{sc} + R \right)} \quad (3.4)$$

On further simplification we get,

$$\Rightarrow H = \frac{1}{\left( 3 + sRC + \frac{1}{sRC} \right)} \quad (3.5)$$

4. Find  $R_{11}$  and  $R_{22}$  from Fig. 2.6.

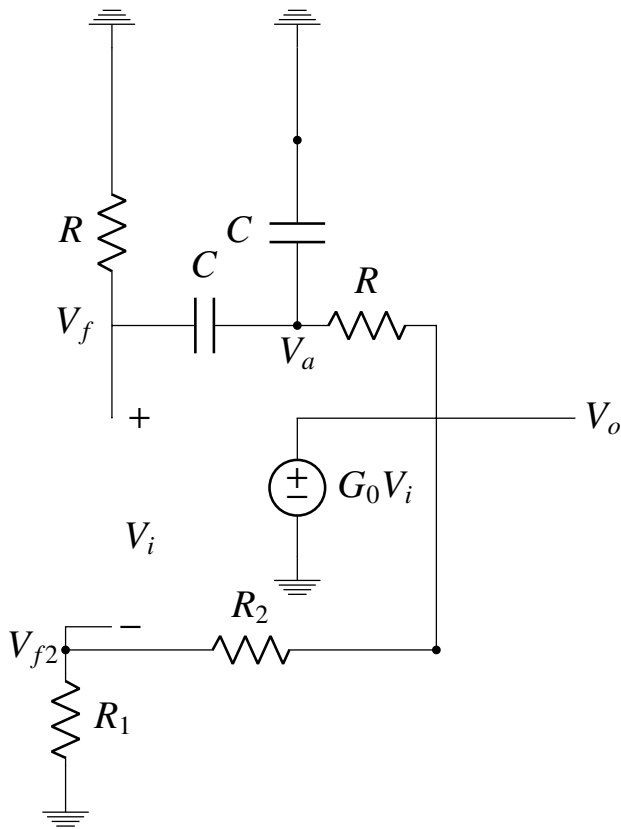


Fig. 1.4

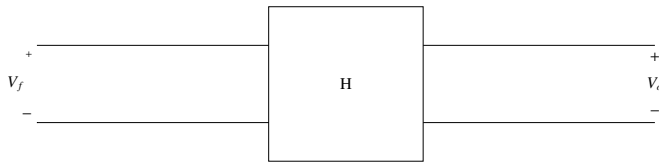


Fig. 2.5: Feedback block diagram

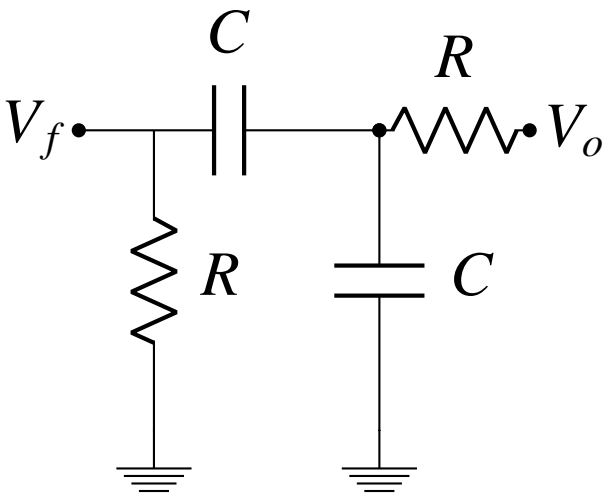


Fig. 2.6: Feedback circuit

**Solution:** Shorting  $V_o$  to ground,

$$R_{11} = R \parallel \left( \frac{1}{sC} + \frac{1}{sC} \parallel R \right) \quad (4.1)$$

Shorting  $V_f$  to ground,

$$R_{22} = \frac{1}{2sC} + R \quad (4.2)$$

5. Draw the block diagram and circuit diagram for  $G$ .

**Solution:** See Figs. 5.1 for the block diagram and Figs. 5.2 for the circuit diagram.

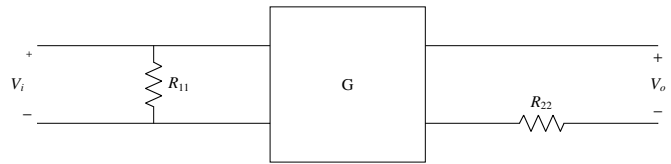


Fig. 5.1: Open loop block diagram

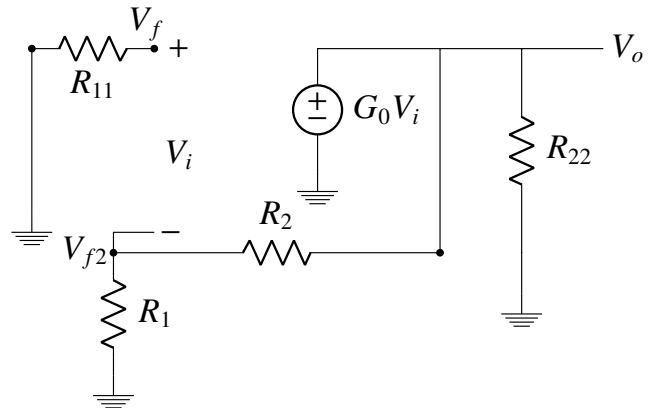


Fig. 5.2: Open loop circuit diagram

6. Find  $G$ .

**Solution:** From Fig. 5.2,

$$V_{f2} = \left( \frac{R_1}{R_1 + R_2} \right) V_o \quad (6.1)$$

From Fig. 1.2,

$$G_1 = \frac{V_{f2}}{V_o} \quad (6.2)$$

$$= \frac{R_1}{R_1 + R_2} \quad (6.3)$$

From Fig.1.2,  $G_1$  is the negative feedback factor and  $G_0$  is the gain of the op-amp.

Therefore, equivalent  $G$  is given by

$$G = \frac{G_0}{1 + G_0 G_1} \quad (6.4)$$

$$= \frac{1}{\frac{1}{G_0} + G_1} \quad (6.5)$$

On substituting  $G_0 \rightarrow \infty$

$$G \approx \frac{1}{G_1} \quad (6.6)$$

$$G = \frac{R_1 + R_2}{R_1} \quad (6.7)$$

$$\Rightarrow G = 1 + \frac{R_2}{R_1} \quad (6.8)$$

7. Find the loop gain  $L(s)$ .

**Solution:** From (6.8) and (3.5),

$$L(s) = G(s)H(s) \quad (7.1)$$

$$\Rightarrow L(s) = \left( \frac{1 + \frac{R_2}{R_1}}{3 + sRC + \frac{1}{sRC}} \right) \quad (7.2)$$

8. Find the closed loop gain  $T(s)$ .

**Solution:** From Fig. 1.3,

$$T(s) = \frac{G}{1 - GH(s)} = \frac{G}{1 - L(s)} \quad (8.1)$$

$$\Rightarrow \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 - \left(\frac{1 + \frac{R_2}{R_1}}{3 + sRC + \frac{1}{sRC}}\right)} \quad (8.2)$$

9. Find the conditions for oscillation.

**Solution:** For oscillations to start,

- $T(s)$  should have imaginary poles.
- $L(0) \geq 1$

For  $T(s)$  to have imaginary poles,

$$\text{Im}\{L(j\omega)\} = 0 \quad (9.1)$$

$$\Rightarrow L(j\omega) = \left( \frac{1 + \frac{R_2}{R_1}}{3 + j\left(\omega RC - \frac{1}{\omega RC}\right)} \right) \quad (9.2)$$

From (7.2),

$$L(j\omega) = \left( \frac{1 + \frac{R_2}{R_1}}{3 + j\left(\omega RC - \frac{1}{\omega RC}\right)} \right) \quad (9.3)$$

$$\Rightarrow j\left(\omega RC - \frac{1}{\omega RC}\right) = 0 \quad (9.4)$$

$$\text{or, } \omega = \frac{1}{RC} \quad (9.5)$$

Also, from equation (7.2)

$$L(0) \geq 1 \quad (9.6)$$

$$= \left( \frac{1 + \frac{R_2}{R_1}}{3 + j(0)} \right) \geq 1 \quad (9.7)$$

$$\Rightarrow \frac{R_2}{R_1} \geq 2 \quad (9.8)$$

10. Find the frequency for some arbitrary  $R$ ,  $C$  values given in Table 10.

Parameter	Value
$R$	$250\Omega$
$C$	$1mF$
$R_2$	$2030\Omega$
$R_1$	$1000\Omega$

TABLE 10

**Solution:** The following code plots the impulse response of the system. This, in fact is the output of Fig. 1.1.

codes/es17btech11002/es17btech11002.py

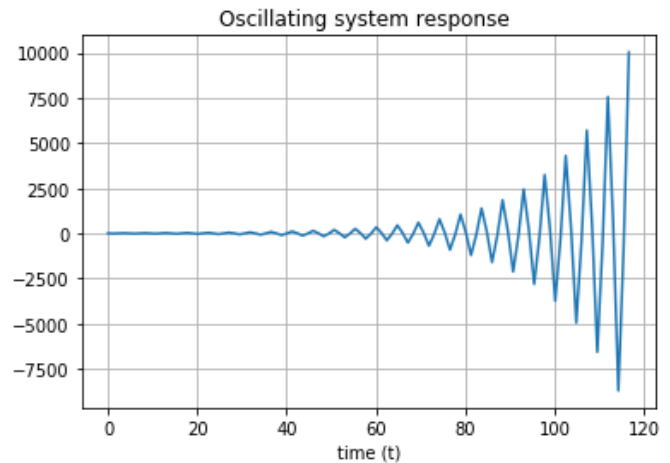


Fig. 10

**Frequency:** From equation (9.5)

$$\omega = \frac{1}{RC} = 4\text{rad/sec} \quad (10.1)$$

$$f = \frac{\omega}{2\pi} = 0.636\text{Hz} \quad (10.2)$$

11. Verify the frequency using spice simulation.

**Solution:** The following readme file provides necessary instructions to simulate the circuit in spice.

```
codes/es17btech11002/spice/README
```

The following netlist simulates the given circuit.

```
codes/es17btech11002/spice/es17btech11002.
net
```

The following code plots the output from the oscillator spice simulation which is shown in Fig. 11.1.

```
codes/es17btech11002/spice/
es17btech11002_spice.py
```

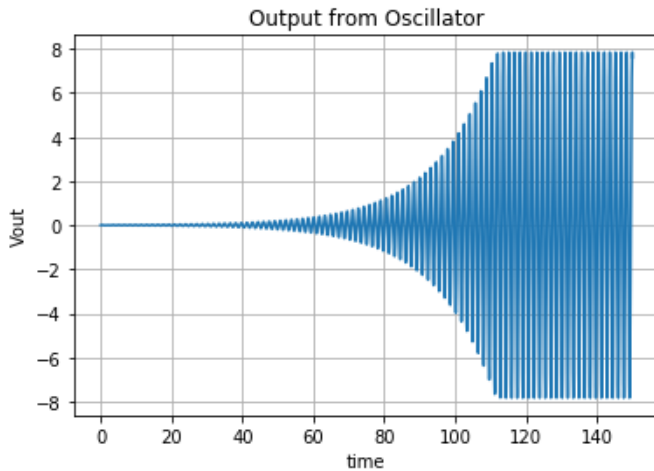


Fig. 11.1

The following code plots a part of the spice output from which we can observe a clear sinusoidal output shown in Fig. 11.2.

```
codes/es17btech11002/spice/
es17btech11002_spice2.py
```

**Frequency:** From Fig. 11.2 time period is calculated by any two end points of one cycle,

$$T = 124.150 - (122.160) = 1.61\text{sec} \quad (11.1)$$

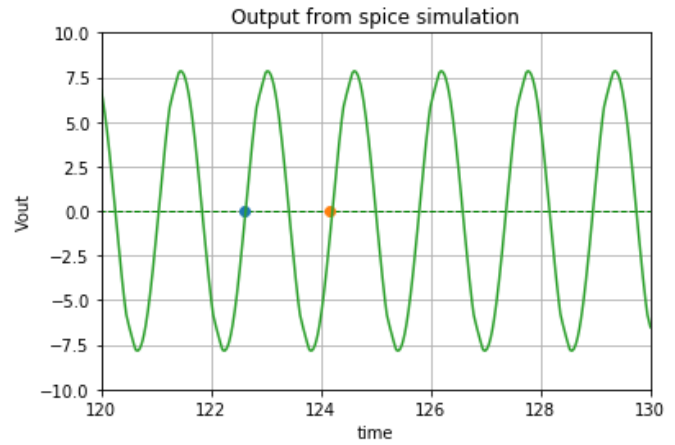


Fig. 11.2

$$f = \frac{1}{T} = 0.64\text{Hz} \quad (11.2)$$

Hence, the frequency is verified through the spice simulation.