

# Oscillator

Mohammed Sadiq\*

1. For the circuit in Fig. ??, break the loop at node X and find the loop gain (working backward for simplicity to find  $V_X$  in terms of  $V_O$ ). For  $R = 10 \text{ k}\Omega$ , find  $C$  and  $R_f$  to obtain sinusoidal oscillations at 10 kHz.

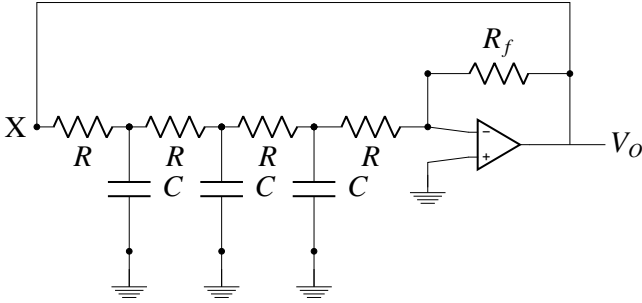


Fig. 1

2. **Solution:** We first calculate the relation between  $I_4$  and  $V_X$  in fig ?? by using the relation between the currents and the fact that the inverting terminal of the Op-Amp is virtually grounded as follows:

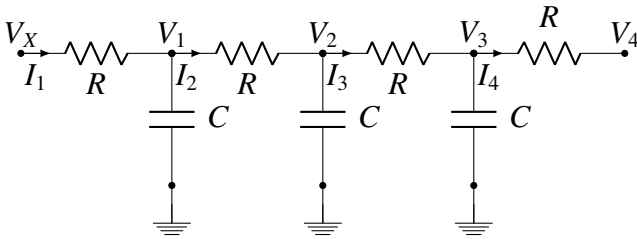


Fig. 2

Here,  $V_4$  has zero voltage. Applying KVL between  $V_3$  and  $V_4$ , we get

$$V_3 = I_4 R \quad (2.1)$$

Starting at node  $V_3$  to node  $V_X$ , applying KCL and KVL sequentially, and substituting the

previous two equations gives:

$$I_3 = I_4 + V_3 sC \Rightarrow I_3 = I_4(1 + sRC) \quad (2.2)$$

$$V_2 = V_3 + I_3 R \Rightarrow V_2 = I_4 R(2 + sRC) \quad (2.3)$$

$$I_2 = I_3 + V_2 sC \Rightarrow I_2 = I_4(1 + 3sRC + (sRC)^2) \quad (2.4)$$

$$V_1 = V_2 + I_2 R \Rightarrow V_1 = I_4 R(3 + 4sRC + (sRC)^2) \quad (2.5)$$

$$I_1 = I_2 + V_1 sC \Rightarrow I_1 = I_4(1 + 6sRC + 5(sRC)^2 + (sRC)^3) \quad (2.6)$$

$$V_X = V_1 + I_1 R \Rightarrow V_X = I_4 R(4 + 10sRC + 6(sRC)^2 + (sRC)^3) \quad (2.7)$$

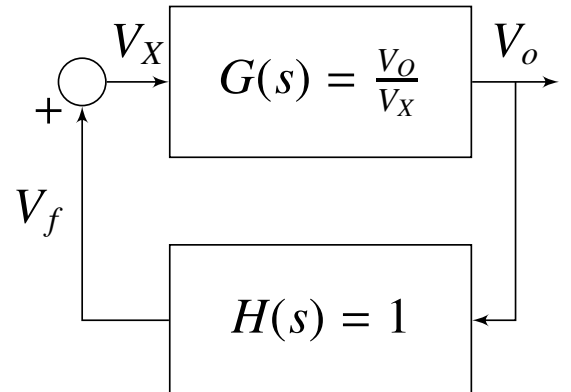


Fig. 2

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.