

Control Systems

Adyasa Mohanty*

CONTENTS

1 Feedback Circuits

Abstract—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/codes>

1 FEEDBACK CIRCUITS

Figure 0 shows a feedback transconductance amplifier implemented using an op amp with open-loop gain μ , a very large input resistance, and an output resistance r_o . The output current I_o that is delivered to the load resistance R_L is sensed by the feedback network composed of the three resistances R_M , R_1 , and R_2 , and a proportional voltage V_f is fed back to the negative-input terminal of the op amp. Find G, H and T. If the loop gain is large, find an approximate expression for T and state precisely the condition for which this applies. The parameters given are shown in the TABLE.0

Parameter	Value
input resistance	∞
output resistance	r_o
Input voltage	V_s
Output Voltage	V_o

TABLE 0: 1

1. Draw the block diagram and the equivalent circuit for Fig. 0

Solution: The equivalent circuit of the amplifier is in Fig. 1

2. Draw the block diagram and equivalent circuit for H .

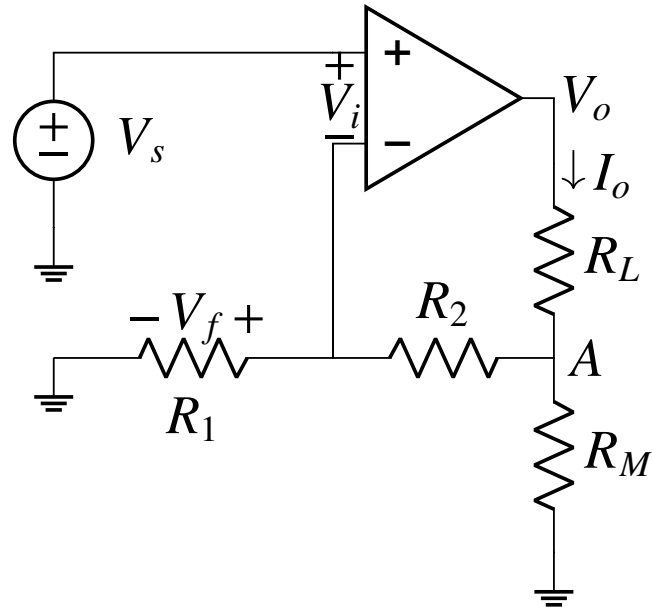


Fig. 0

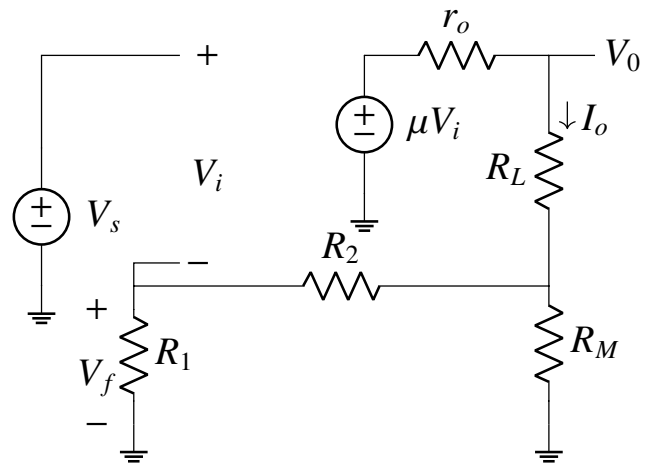


Fig. 1

3. Find H .
- Solution:** See Fig. 2.3 and 2.4.
- Solution:** From Fig. 2.3 and 2.4,

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

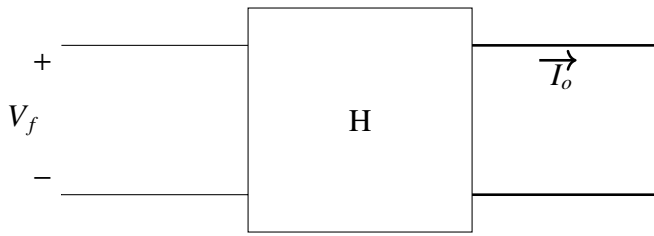


Fig. 2.3

Solution:

$$T = \frac{G}{1 + GH} \quad (5.1)$$

$$= \frac{\mu(R_1 + R_2 + R_M)}{R_1 + R_2 + R_M + \mu R_1 R_M} \quad (5.2)$$

$$\approx \frac{1}{H} = \frac{R_1 + R_2 + R_M}{R_1 R_M} \quad (5.3)$$

6. Summarize your results in a table.

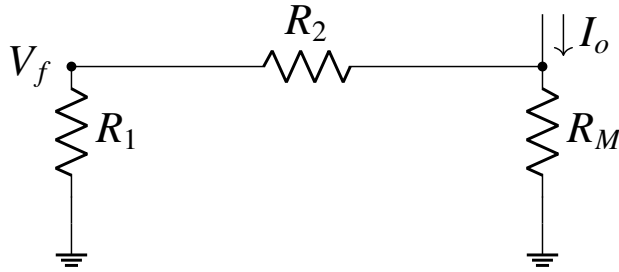
Solution: See Table 6

Fig. 2.4

$$H = \frac{V_f}{I_o} \quad (3.1)$$

$$= \frac{R_1 R_M}{R_1 + R_2 + R_M} \quad (3.2)$$

4. Find G .**Solution:** From Fig. 1,

$$G = \frac{I_o}{V_i} \quad (4.1)$$

$$= \mu \quad (4.2)$$

5. Find T .7. Find I_o for the parameters given in Table 7.**Solution:** The following code computes the

Parameter	Value
R_1	1000 Ω
R_2	1000 Ω
R_L	1000 Ω
R_M	1000 Ω
V_s	1V

TABLE 7

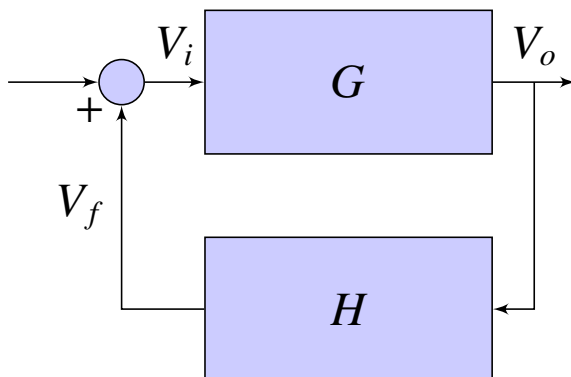


Fig. 5.5

value of I_o using the fact that

$$I_o = \frac{V_s}{H} \quad (7.1)$$

$$(7.2)$$

```
codes/ee18btech11048/ee18btech11048_fbc.py
```

On running this code value of I_o is printed on terminal. The value obtained is 0.003 A.

8. Verify your result through spice.

Solution: The following readme file provides

necessary instructions to simulate the circuit in spice.

`codes/ee18btech11048/spice/README`

The following netlist simulates the given circuit.

`codes/ee18btech11048/spice/feedback.net`

On running the spice simulations the I_o value is printed on terminal. The value printed is 0.003003266 A.

We observe that the value obtained using SPICE simulation is very close to the value obtained from the python code.

So the approximation for T gives accurate results.