

# Hartley Oscillator

Harsh kabra \*

Find the frequency of oscillation for the Hartley circuit in Fig. 0. Also find the condition on  $g_m$ .

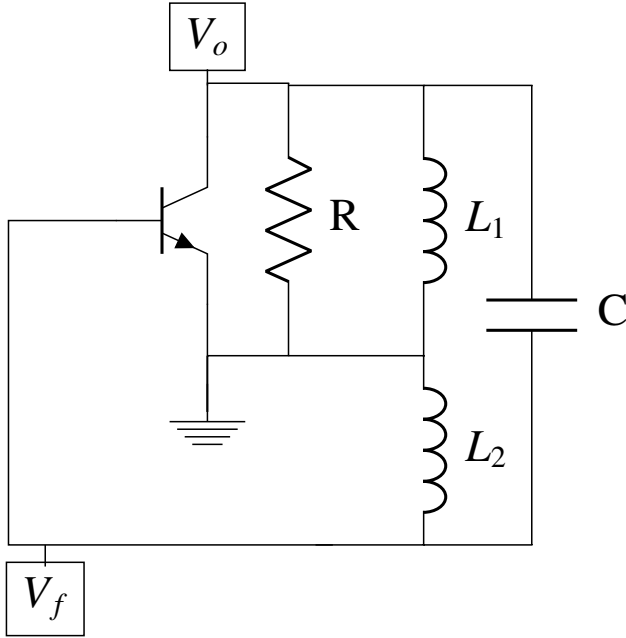


Fig. 0: Hartley oscillator

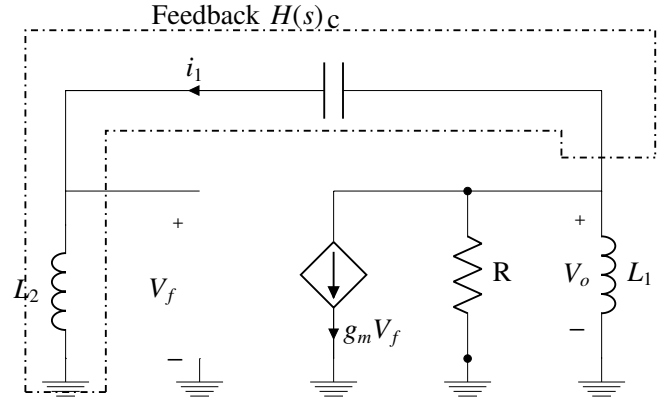


Fig. 1.1: Small signal model

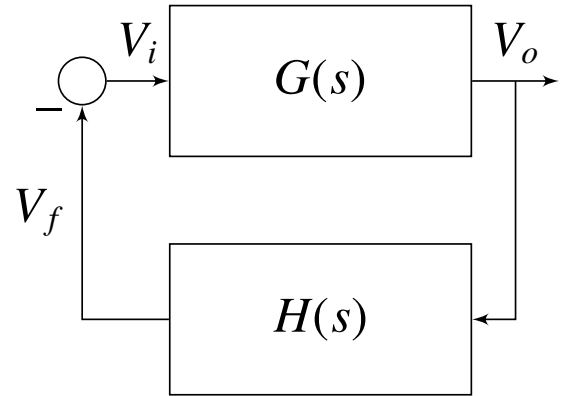


Fig. 1.2: Block diagram

1. Draw the small signal model for Fig. 0 and the block diagram for the equivalent control system.

**Solution:** See Figs. 1.1 and 1.2.

2. Draw the circuit for  $H$  and find it.

**Solution:** From Fig. 2,

$$H(s) = \frac{V_f}{V_o} \quad (2.1)$$

$$= \left( \frac{s^2 CL_2}{s^2 CL_2 + 1} \right) \quad (2.2)$$

3. Draw the circuit for  $G$  and find it.

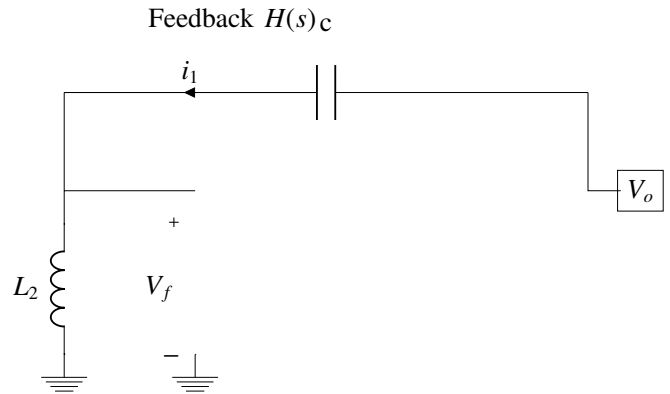


Fig. 2: Small signal H(s)

**Solution:** In Fig. 3

$$i_1 = \frac{V_i}{sL_2} \quad (3.1)$$

$$V_o = I(sL_1 \parallel R) \quad (3.2)$$

$$I = i_1 + g_m V_i \quad (3.3)$$

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

yielding

$$\frac{V_o}{V_i} = G(s) = \left( g_m + \frac{1}{sL_2} \right) \left( \frac{RsL_1}{R + sL_1} \right) \quad (3.4)$$

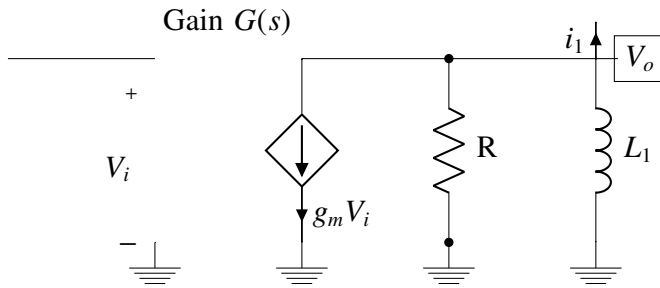


Fig. 3: Small signal  $G(s)$

4. Find the frequency of oscillation.

**Solution:** From 3.4 and 3.4,

$$1 + G(s)H(s) = 0 \quad (4.1)$$

$$\Rightarrow s^3(g_m CL_1 L_2 + CL_1 L_2) + s^2(RCL_1 + RCL_2) + sL_1 + R = 0 \quad (4.2)$$

For oscillations, substituting  $s = j\omega$ ,

$$(R - \omega^2(RC(L_1 + L_2))) + j(\omega L_1 - \omega^3(g_m R + 1)CL_1 L_2) = 0 \quad (4.3)$$

Equating the real part of the above to 0,

$$\omega^2(RC(L_1 + L_2)) = R \quad (4.4)$$

$$\Rightarrow \omega = \frac{1}{\sqrt{C(L_1 + L_2)}} \quad (4.5)$$

Similarly, from the imaginary part,

$$g_m R + 1 = \frac{C(L_1 + L_2)}{CL_2} \quad (4.6)$$

$$\Rightarrow g_m R = \frac{L_1}{L_2} \quad (4.7)$$

For stable oscillations,

$$g_m R > \frac{L_1}{L_2} \quad (4.8)$$

5. Simulate the oscillator using Fig. 5.1 and Table 5.

**Solution:** The closed loop impulse response is plotted in Fig. 5.2 using the following code.

```
codes/ee18btech11019_1.py
```

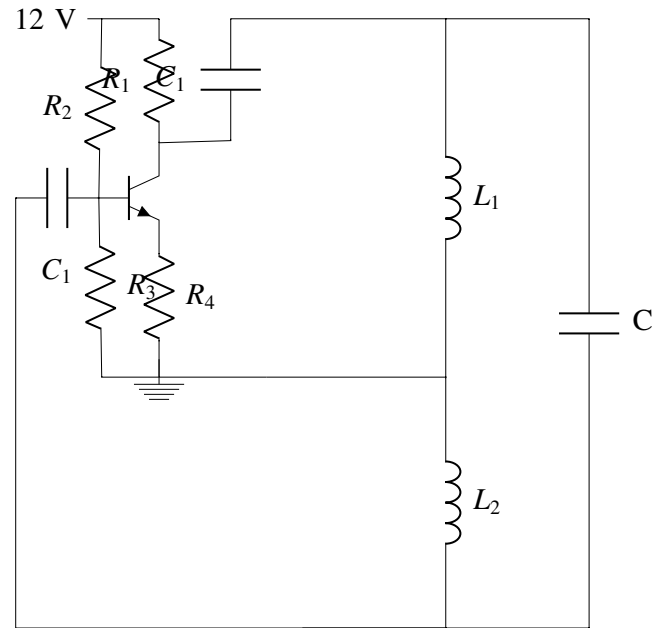


Fig. 5.1: Simulation circuit

Parameter	Value
$R_1$	$1.2k\Omega$
$R_2$	$50.5k\Omega$
$R_3$	$10.5k\Omega$
$R_4$	$298\Omega$
$C_1$	$22\mu F$
$C_2$	$22\mu F$
$C$	$1.1\mu F$
$L_1$	$1mH$
$L_2$	$1mH$

TABLE 5

The spice simulations are done using the following netlist

```
spice/Draft3.net
```

and plotted in Fig. 5.3 using the following code.

```
spice/ee18btech11019_2.py
```

From Fig. 5.3, the frequency obtained is 3.384 kHz. From 4.5, the expected frequency is

$$f = \frac{1}{2\pi \sqrt{C(L_1 + L_2)}} \quad (5.1)$$

$$= 3.394 \text{ kHz} \quad (5.2)$$

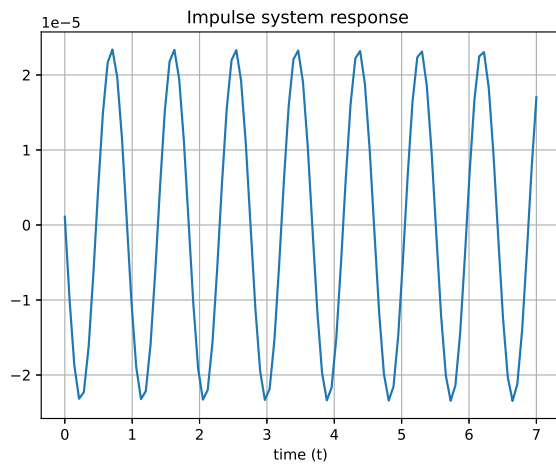


Fig. 5.2: Output when taken from transfer function

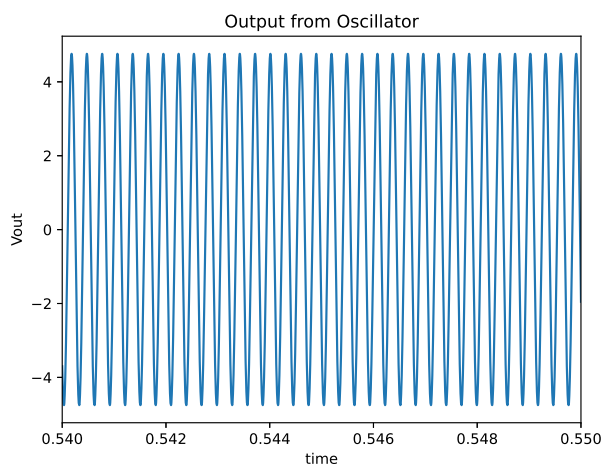


Fig. 5.3: Simulation result