

# Control Systems

Durbha Krishna Srikar\*

## CONTENTS

1	Circuit Design from Bode Plot	1
2	Phase Margin	3

### 1 CIRCUIT DESIGN FROM BODE PLOT

1.1. Consider the Magnitude Bode Plot and Phase Bode Plot 1.1 of Open-Loop Transfer Function of an Amplifier. Estimate the Open-Loop Transfer Function. (Assume 'A' as 'G' and 'β' as 'H')

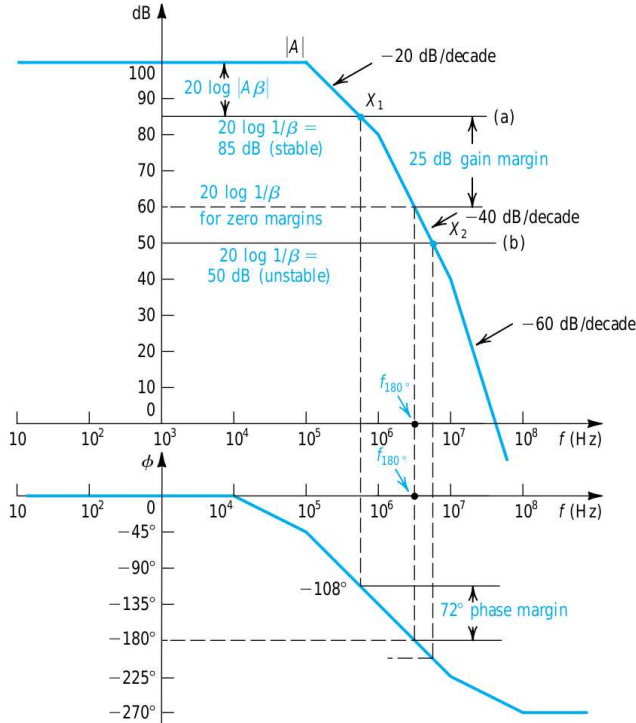


Fig. 1.1: Magnitude and Phase Bode Plot

**Solution:** Let  $G(f)$  be the Open-Loop Transfer Function,

$$G(f) = \begin{cases} 100 & 0 < f < 10^5 \\ 200 - 20 \log(f) & 10^5 < f < 10^6 \\ 320 - 40 \log(f) & 10^6 < f < 10^7 \\ 460 - 60 \log(f) & 10^7 < f \end{cases} \quad (1.1.1)$$

$$\nabla G(f) = \frac{d(G(f))}{d(\log(f))} = \begin{cases} 0 & 0 < f < 10^5 \\ -20 & 10^5 < f < 10^6 \\ -40 & 10^6 < f < 10^7 \\ -60 & 10^7 < f \end{cases} \quad (1.1.2)$$

As we know that, **When a pole is encountered the slope always decreases by 20 dB/decade and When a zero is encountered the slope always increases by 20 dB/decade.** So, by observing Fig. 1.1 it can be concluded that we are having Poles at  $f = 10^5 \text{ Hz}$ ,  $10^6 \text{ Hz}$ ,  $10^7 \text{ Hz}$  and No Zeros.

So, the Open-Loop Transfer Function  $G(f)$  is

$$G(f) = \frac{10^5}{\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{10^6}\right)\left(1 + j\frac{f}{10^7}\right)} \quad (1.1.3)$$

1.2. Calculate the Phase of Open-Loop Transfer Function.

**Solution:**

$$\phi(f) = - \left[ \tan^{-1} \left( \frac{f}{10^5} \right) + \tan^{-1} \left( \frac{f}{10^6} \right) + \tan^{-1} \left( \frac{f}{10^7} \right) \right] \quad (1.2.1)$$

1.3. Verify (1.1.3) by plotting the Magnitude and Phase Bode Plots of  $G(f)$  and comparing with (1.1.1)

**Solution:** See Fig. 1.3

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

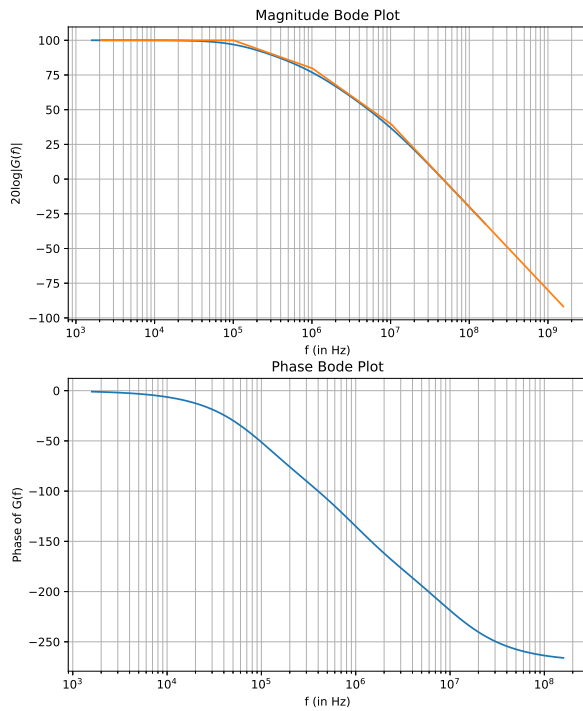


Fig. 1.3: Magnitude Bode Plot

Python Code for Bode Plot is at

codes/ee18btech11014/Bode\_Plot.py

1.4. Find the PM from Fig. 1.1, given that the feedback gain  $H(f)$  is constant and given by

$$20 \log \left( \frac{1}{H(f)} \right) = 85 \text{ dB} \quad (1.4.1)$$

$$\text{or, } H(f) = 5.623 \times 10^{-5}. \quad (1.4.2)$$

**Solution:** From the figure,

$$20 \log |G(f_1)| = 85 \text{ dB} \quad (1.4.3)$$

$$\Rightarrow 20 \log |G(f_1)| = 20 \log \left( \frac{1}{H(f_1)} \right) \quad (1.4.4)$$

$$\text{or, } |G(f_1)H(f_1)| = 1 \quad (1.4.5)$$

and

$$f_1 = 0.493 \text{ MHz}, \quad (1.4.6)$$

from (1.4.3) and (1.1.3). Also,

$$\because \angle H(f) = 0, \forall f \quad (1.4.7)$$

$$\angle G(f_1)H(f_1) = \angle G(f_1) = -108^\circ \quad (1.4.8)$$

$$\Rightarrow PM = 180^\circ - 108^\circ = 72^\circ \quad (1.4.9)$$

using (1.4.6) in (1.2.1).

1.5. Find the GM.

**Solution:** The crossover frequency  $f_\pi$  is defined as

$$\angle G(f_\pi)H(f_\pi) = 180^\circ \quad (1.5.1)$$

$$\Rightarrow \angle G(f_\pi) = 180^\circ \quad (1.5.2)$$

$$\Rightarrow f_\pi = 3.34 \text{ MHz} \quad (1.5.3)$$

by solving (1.2.1). From Fig. 1.1,

$$20 \log |G(f_\pi)| = 60 \text{ dB} \quad (1.5.4)$$

$$\Rightarrow 20 \log |G(f_\pi)| - 20 \log \left( \frac{1}{H(f_\pi)} \right) = (60 - 85) \text{ dB} \quad (1.5.5)$$

$$\Rightarrow GM = |20 \log |G(f_\pi)H(f_\pi)|| = 25 \text{ dB} \quad (1.5.6)$$

1.6. Break the Transfer Function  $G(s)$  into Simple Blocks and create a block diagram.

**Solution:** From (1.1.3)

$$G(s) = \frac{10^5}{\left(1 + \frac{s}{2\pi \times 10^5}\right) \left(1 + \frac{s}{2\pi \times 10^6}\right) \left(1 + \frac{s}{2\pi \times 10^7}\right)} \quad (1.6.1)$$

The block diagram is available in Fig. 1.6

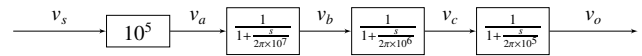


Fig. 1.6

1.7. Find the Gain of RC-Circuit in Fig. 1.7 and identify the pole location.

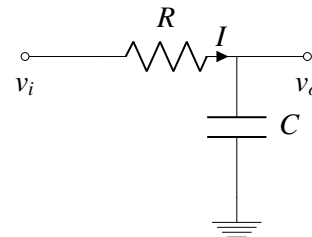


Fig. 1.7

**Solution:**

$$v_o = v_i \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \quad (1.7.1)$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{1}{1 + sCR} \quad (1.7.2)$$

Thus, there is a pole at

$$s = -\frac{1}{RC} \quad (1.7.3)$$

1.8. Design a circuit for  $G(s)$ .

**Solution:** (1.6.1) can be expressed as

$$\therefore G(s) = \frac{G_0}{(1 + sC_1R_1)(1 + sC_2R_2)(1 + sC_3R_3)} \quad (1.8.1)$$

where the parameters are available in Table 1.8. Choosing an OPAMP of gain  $G_0$  and noting from (1.7.2) that each of the blocks in Fig. 1.6 can be realised through the RC circuit in Fig. 1.7 with parameters in Table 1.8, the circuit design is available in Fig. 1.8.

Circuit Element	Value
$G_0$	100dB
$R_1$	100Ω
$R_2$	1kΩ
$R_3$	10kΩ
$C_1$	$\frac{1}{2\pi}nF$
$C_2$	$\frac{1}{2\pi}nF$
$C_3$	$\frac{1}{2\pi}nF$

TABLE 1.8

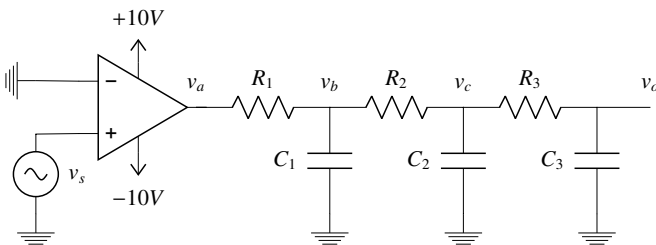


Fig. 1.8

1.9. Design a circuit for  $H(s)$ .

**Solution:** From (1.4.2),  $H$  is constant and should not involve any Reactive Elements. The

simplest way to realise  $H$  is through a voltage divider as shown in Fig. 1.9. Thus,

$$H = \frac{R_F}{R_F + R_M} \quad (1.9.1)$$

with resistance values available in Table 1.9.

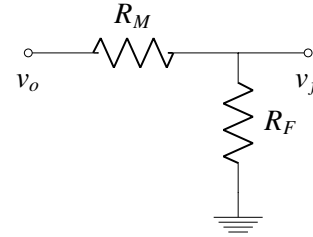


Fig. 1.9

Circuit Element	Value
$R_M$	$1.778 \times 10^5 \Omega$
$R_F$	10Ω

TABLE 1.9

1.10. Find the closed loop transfer function  $T(s)$  and draw the equivalent circuit.

**Solution:** The closed loop circuit is easily obtained from Figs. 1.8 and 1.9 as shown in Fig. 1.10

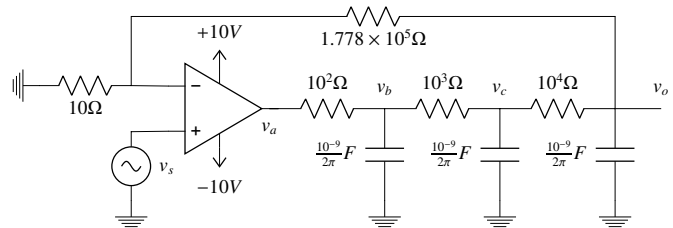


Fig. 1.10

The closed loop gain,

$$T(s) = \frac{G(s)}{1 + G(s)H} \quad (1.10.1)$$

$$= \frac{10^5}{\left(1 + \frac{s}{2\pi 10^5}\right) \left(1 + \frac{s}{2\pi 10^6}\right) \left(1 + \frac{s}{2\pi 10^7}\right) + 5.623} \quad (1.10.2)$$

## 2 PHASE MARGIN

2.1. Find the frequency for which  $PM = 90^\circ$ . Assume  $H$  to be constant.

**Solution:**  $\because \angle H(f) = 1,$

2.4. Repeat all the above for  $PM = 45^\circ$ .

$$\angle G(f_{90}) H(f_{90}) = \angle G(f_{90}) = 90^\circ - 180^\circ \quad (2.1.1)$$

$$= -90^\circ \quad (2.1.2)$$

The Bode plot in Fig. 1.1 shows that

$$|G(f)| < 1, \quad f > 10^8 \quad (2.1.3)$$

Also,

$$\tan^{-1}\left(\frac{f}{10^7}\right) \approx 0, \quad f < 10^8 \quad (2.1.4)$$

Thus, from (1.2.1) and (2.1.2),

$$\phi(f) \approx -\left[\tan^{-1}\left(\frac{f}{10^5}\right) + \tan^{-1}\left(\frac{f}{10^6}\right)\right] \quad (2.1.5)$$

$$= -90^\circ \quad (2.1.6)$$

$$\Rightarrow f_{90} = 3.162 \times 10^5 \quad (2.1.7)$$

after simplification.

2.2. Find  $H$  when the  $PM = 90^\circ$ .

**Solution:** By definition of the PM,

$$|G(f_{90}) H(f_{90})| = 1 \quad (2.2.1)$$

$$\Rightarrow |H(f_{90})| = \frac{1}{|G(f_{90})|} \quad (2.2.2)$$

From (1.1.1),

$$20 \log |G(f)| = 200 - 20 \log(3.162 \times 10^5) \quad (2.2.3)$$

$$= 90dB \quad (2.2.4)$$

$$\Rightarrow |G(f)| = 3.1625 \times 10^4 \quad (2.2.5)$$

$$\Rightarrow H = 3.162 \times 10^{-5} \quad (2.2.6)$$

using (2.2.2).

2.3. Design the closed loop circuit for  $PM = 90^\circ$

**Solution:** See Fig. 2.3, where Fig. 1.9 is used for the feedback  $H$  with  $R_M = 0.3162M\Omega$  and  $R_F = 10\Omega$ .

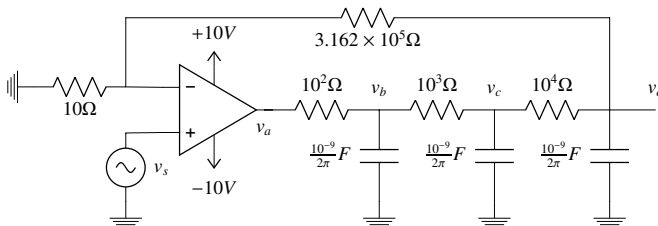


Fig. 2.3