

Feedback Circuits

P. Aashrith *

A dc amplifier having a single-pole response with pole frequency 10Hz and unity-gain frequency of 1MHz is operated in a loop whose frequency-independent feedback factor is 0.01. Find the low-frequency gain, the 3-dB frequency, and the unity-gain frequency of the closed-loop amplifier. By what factor does the pole shift?

1. Find $G(s)$.

Solution: The open-loop gain of the amplifier can be expressed as

$$G(s) = \frac{G_0}{1 + \frac{s}{\omega_p}} = \frac{G_0}{1 + \frac{s}{2\pi \cdot 10}} \quad (1.1)$$

Let $f_0 = 1$ MHz.

$$\because |G(j\omega_0)| = 1, \quad (1.2)$$

$$\Rightarrow |G_0| = \left| 1 + j \frac{2\pi \cdot 10^6}{2\pi \cdot 10} \right| \quad (1.3)$$

$$\text{or, } G_0 \approx 10^5 \quad (1.4)$$

Thus,

$$G(s) = \frac{10^5}{1 + \frac{s}{2\pi \cdot 10}} \quad (1.5)$$

2. Given that $H = 0.01$, find $T(s)$.

Solution: From (1.5),

$$T(s) = \frac{G(s)}{1 + G(s)H(s)} \quad (2.1)$$

$$= \frac{99.90}{1 + \frac{s}{2\pi \cdot 10010}} \quad (2.2)$$

The block diagram is shown in Fig. 2.

Block diagram representation of the amplifier

3. Find the low frequency gain $T(0)$.

Solution: From (2.2)

$$T(0) = 99.900 \quad (3.1)$$

4. Find the 3-dB frequency of the closed loop

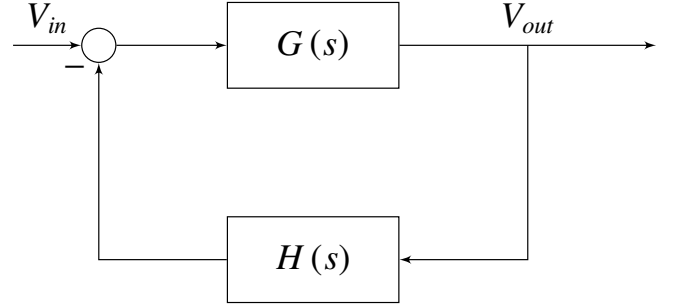


Fig. 2

amplifier.

Solution: From (2.2)

$$f_{3dB} = 10.01 \text{ kHz} \quad (4.1)$$

5. Find the unity gain frequency of the closed loop amplifier

Solution:

$$|T(j\omega_1)| = 1 \quad (5.1)$$

$$\Rightarrow 99.90 = \left| 1 + \frac{j\omega}{2\pi \cdot 10010} \right| \quad (5.2)$$

$$\text{or, } f_1 = 999.94 \text{ kHz} \quad (5.3)$$

upon substitution from (2.2) and some algebra.

6. By what factor does the pole shift?

Solution: From (1.5) and (2.2), the ratio of the poles is

$$\frac{2\pi \times 10010}{2\pi \times 10} = 1001 \quad (6.1)$$

7. Tabulate the DC Gain, Bandwidth and Gain bandwidth product for $G(s)$ and $T(s)$.

Solution: See Table 7

\therefore , by using feedback we can get desired Gain of an amplifier while maintaining constant Gain Bandwidth product (for a first-order op-amp).

8. Design the circuit for H .

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

	$G(s)$	$T(s)$
Gain	10^5	99.9
Band-width	20π	$20\pi.1001$
Gain band-width product	$2\pi.10^6$	$2\pi.10^6$

TABLE 7

Solution: See Fig. 8. For

$$R_1 = 10\Omega \quad (8.1)$$

$$R_f = 990\Omega, \quad (8.2)$$

$$H = \frac{V_f}{V_{out}} = \frac{R_1}{R_1 + R_f} \quad (8.3)$$

$$= 0.01 \quad (8.4)$$

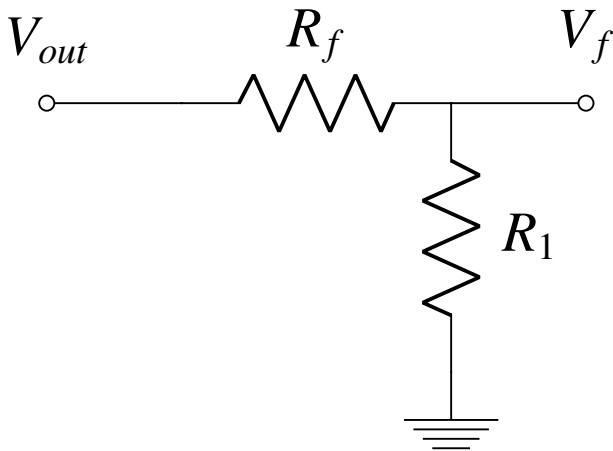


Fig. 8

9. Design the closed loop circuit for $T(s)$.

Solution: See Fig. 9. Table 9 lists the various parameters.

Circuit Element	Parameter Value
Op-amp Gain	10^5
Op-amp pole	$10Hz$
R_1	10Ω
R_f	990Ω

TABLE 9

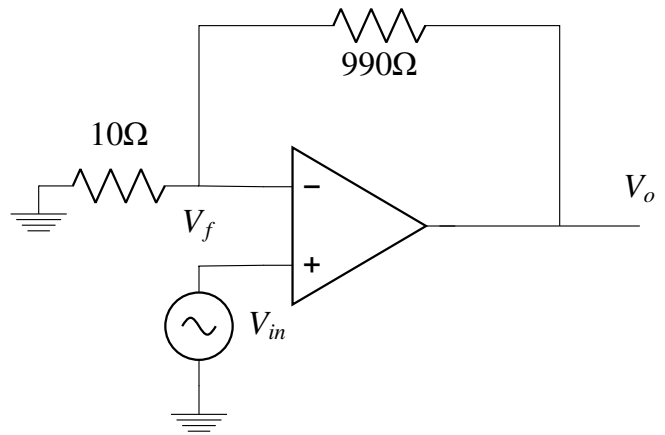


Fig. 9

10. Verify the gain of closed loop Circuit using spice

Solution: Follow the Instructions for SPICE simulation:

spice/README.md

Netlist file for simulation:

spice/ee18btech11035_spice2.net

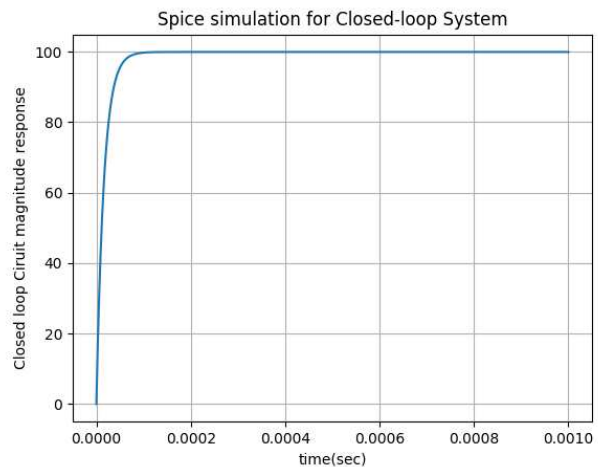


Fig. 10.1: Spice simulation of Closed-loop Transfer Function

The following python code plots the spice output in Fig. 10.1.

codes/ee18btech11035_spice2.py

The following code generates Fig. 10.2.

codes/ee18btech11035_pythonverify2.py

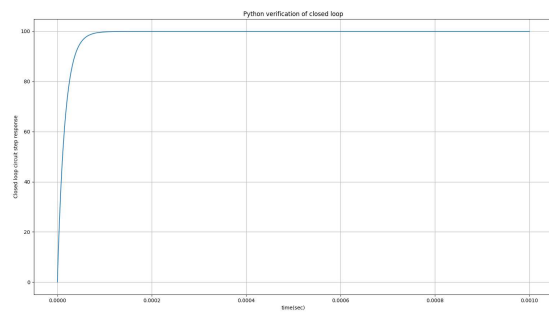


Fig. 10.2: Python verification of closed-loop Transfer Function