

Feedback Voltage Amplifier: Shunt-Shunt

Deep*

CONTENTS

The circuit in Fig. 0 utilizes a voltage amplifier with gain μ in a shunt-shunt feedback topology with the feedback network composed of resistor R_F . In order to be able to use the feedback equations you should first convert the signal source to its Norton Representation.

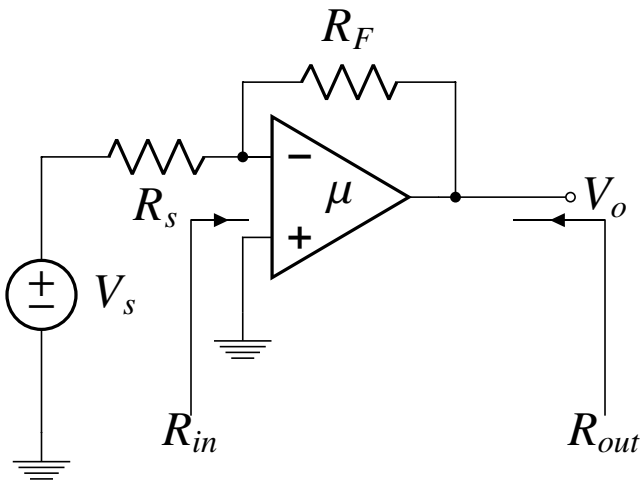


Fig. 0

- 1) If the loop gain is very large, what approximate closed loop voltage gain V_o/V_s is realized? If $R_s = 1\text{k}\Omega$, give the value of R_F that will result in $V_o/V_s \approx -10\text{V/V}$.
 - 2) If the amplifier μ has a dc gain of 10^3 V/V , an input resistance $R_{id} = 100\text{k}\Omega$, and an output resistance $r_o = 1\text{k}\Omega$, find the actual V_o/V_s realized. Also find R_{in} and R_{out} .
 - 3) If the amplifier μ has an upper 3-dB frequency of 1 kHz and a uniform -20-dB/decade gain rolloff, what is the 3-dB frequency of the gain $|V_o/V_s|$.
1. Draw the Norton Representation of Fig. 0 and the equivalent block diagram and the equivalent

control system.

Solution: See Figs. 1.1, 1.2 and 1.3 respectively.

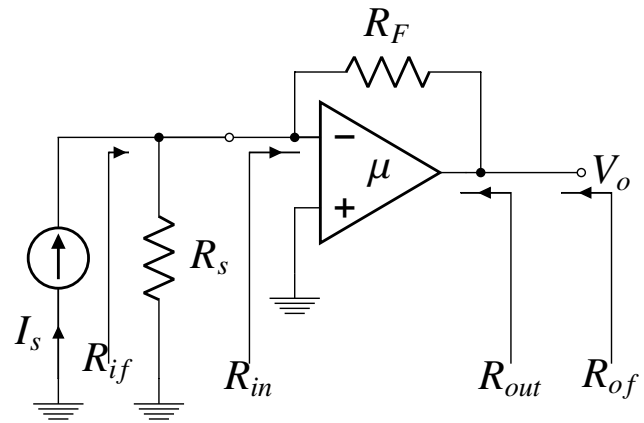


Fig. 1.1

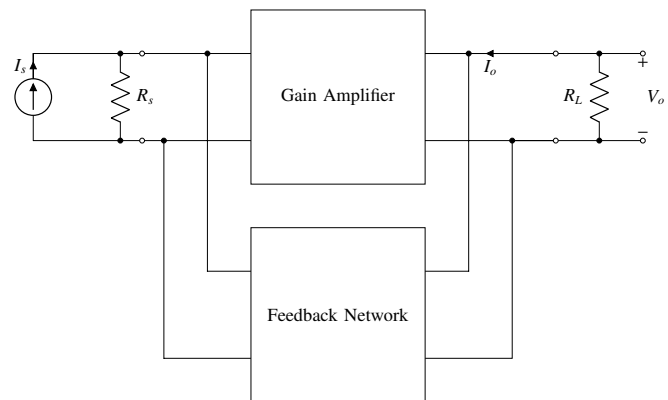


Fig. 1.2: Shunt Shunt Amplifier Block Diagram

2. Draw the circuit for H and find it.

Solution: From Fig. 2.

$$H = \frac{I_f}{V_o} = -\frac{1}{R_F} \quad (2.1)$$

$$(2.2)$$

3. Draw the equivalent circuit for G and find it.

Solution: See Figs. 3.1 and 3.2 denoting the

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

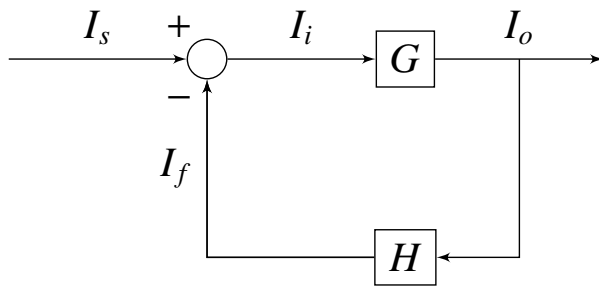


Fig. 1.3: Block Diagram

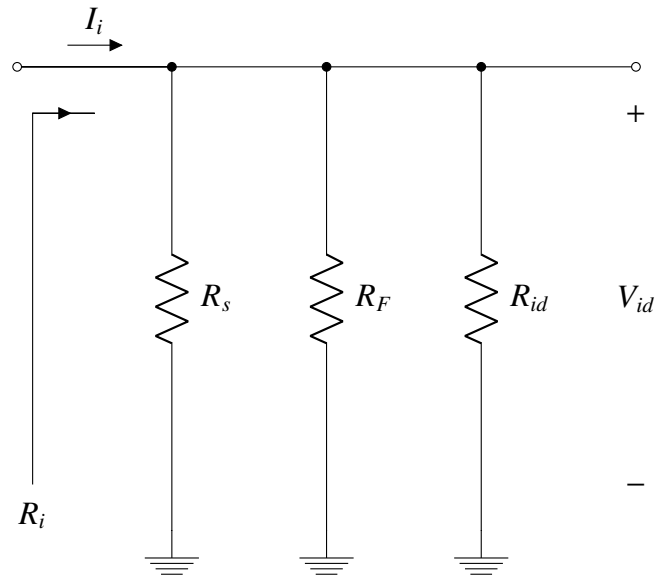


Fig. 3.1

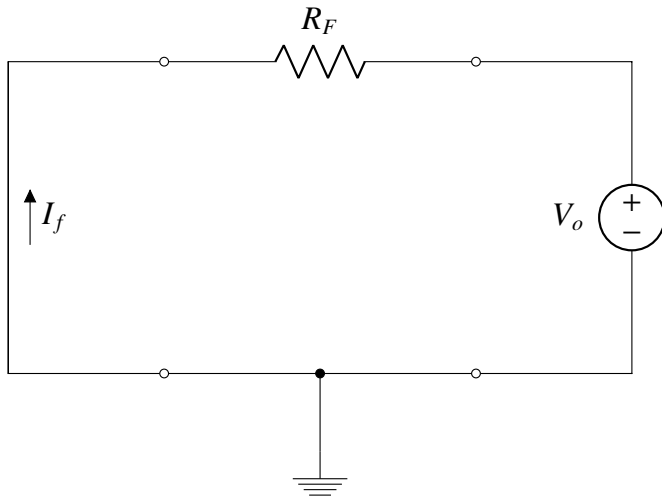


Fig. 2

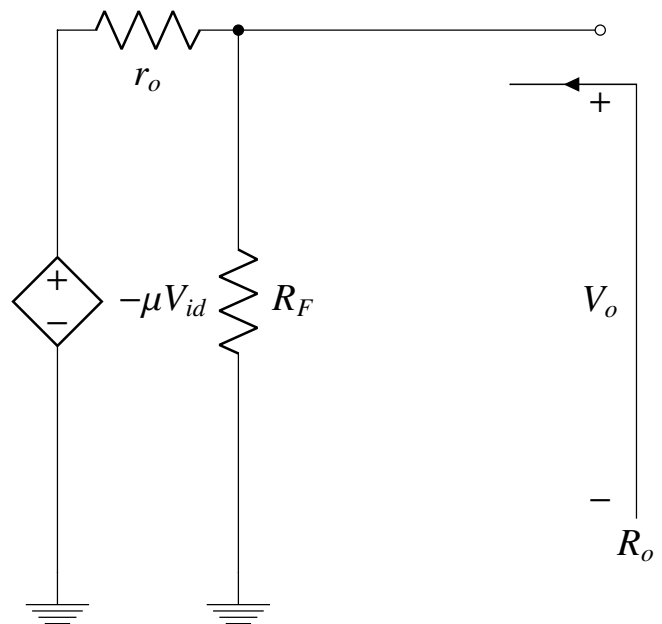


Fig. 3.2

input and output parts of the circuit for G . Refer to Table 3 for the various parameters.

$$R_o = r_o \parallel R_F \quad (3.1)$$

$$V_o = -\mu V_{id} \frac{R_F}{r_o + R_F} \quad (3.2)$$

$$R_i = R_{id} \parallel R_F \parallel R_s \quad (3.3)$$

$$= 100k \parallel 10k \parallel 1k = 0.90k\Omega \quad (3.4)$$

$$V_{id} = I_i R_i \quad (3.5)$$

$$G = \frac{V_o}{I_i} = -\mu \frac{R_F}{r_o + R_F} (R_{id} \parallel R_F \parallel R_s) = -819.00k\Omega \quad (3.6)$$

4. If the loop gain is very large, what approximate closed-loop voltage gain V_o/V_s is realized? Also if $R_s = 1\text{ k}\Omega$, give the value of R_F that will result in $V_o/V_s \approx -10\text{ V/V}$.

Solution: For

$$GH \gg 1, \quad (4.1)$$

$$T = \frac{V_o}{I_s} \approx \frac{1}{H} \quad (4.2)$$

$$\Rightarrow \frac{V_o R_s}{V_s} = -R_F \quad (4.3)$$

$$\text{or, } \frac{V_o}{V_s} = -\frac{R_F}{R_s} \quad (4.4)$$

$$\Rightarrow R_F = 10k\Omega \quad (4.5)$$

Parameters	Description
G	Open Loop Gain
H	Feedback Factor
T	Closed Loop Gain
V_o	Output Voltage
V_s	Signal Source Voltage
V_{id}	Input Voltage of Opamp
I_s	Signal Source Current
I_f	Feedback Current
R_i	Total Input Resistance
R_{out}	Total Output Resistance
R_{id}	Input resistance of Opamp
r_o	Output resistance of Opamp
R_i	Input resistance of Open Loop
R_o	Output resistance of Open Loop
R_{if}	Input resistance of Feedback
R_{of}	Output resistance of Feedback
R_s	Resistance of Current Source
V_f	Voltage across R_s
V_{in}	Voltage at -ve terminal of opamp
f	Closed loop 3-dB freq.

TABLE 3

5. If the amplifier μ has a dc gain of 10^3 V/V, an input resistance $R_{id} = 100$ k Ω , and an output resistance $r_o = 1$ k Ω , find the actual V_o/V_s realized. Also find R_{in} and R_{out} .

Solution:

From equation 2.1 and 3.6

$$T = \frac{G}{1 + GH} \quad (5.1)$$

$$\Rightarrow \frac{V_o}{V_s} = -9.88 \quad (5.2)$$

$$R_{if} = \frac{R_i}{1 + GH} \quad (5.3)$$

$$\Rightarrow R_{if} = 10.87 \Omega \quad (5.4)$$

$$R_{in} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_s}} \quad (5.5)$$

$$\Rightarrow R_{in} = \frac{1}{\frac{1}{10.87} - \frac{1}{1000}} = 10.99 \Omega \quad (5.6)$$

Because R_L is not there in the circuit so we

take its value as ∞ ,

$$R_{of} = \frac{R_o}{1 + GH} = \frac{0.91}{82.9} \quad (5.7)$$

$$\Rightarrow R_{of} = 10.97 \Omega \quad (5.8)$$

$$R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}} \quad (5.9)$$

$$\Rightarrow R_{out} = \frac{1}{\frac{1}{10.97} - \frac{1}{\infty}} = 10.97 \Omega \quad (5.10)$$

Verify the above calculations using the following Python code.

```
codes/ee18btech11011/ee18btech11011_cal.
ipynb
```

6. If the amplifier μ has an upper 3-dB frequency of 1 kHz and a uniform -20-dB/decade gain rolloff, what is the 3-dB frequency of the gain $|V_o/V_s|$.

Solution: To find the 3-dB frequency i.e., ω_{3dB} we need to look at the Fig.6.

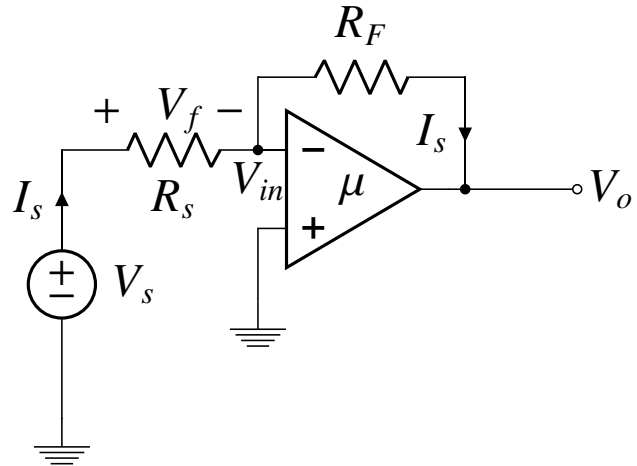


Fig. 6

The open loop gain G is given as follows in terms of frequency:

$$G = \frac{\mu}{1 + \frac{jf}{f_c}} \quad (6.1)$$

From Fig.6 we can say that:

$$V_{in} = V_s - V_f \quad (6.2)$$

$$V_o = -GV_{in} \quad (6.3)$$

$$\frac{V_f}{R_s} = \frac{V_{in} - V_o}{R_F} \quad (6.4)$$

From equation 6.3 and 6.4 we get:

$$\frac{V_f}{R_s} = \frac{-\frac{V_o}{G} - V_o}{R_F} \quad (6.5)$$

$$\Rightarrow \frac{V_f}{V_o} = -\frac{(1+G)(R_s)}{G(R_F)} = -H \quad (6.6)$$

$$\because G \gg 1 \Rightarrow H = \frac{R_s}{R_F} \quad (6.7)$$

Now from equation 6.2, 6.3 and 6.6 we get:

$$-\frac{V_o}{G} = V_s + HV_o \quad (6.8)$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{G}{1+GH} \quad (6.9)$$

Now, for "f" to be 3-dB frequency given condition should be match i.e.,:

$$\left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{2}} \quad (6.10)$$

$$\Rightarrow \left| -\frac{G}{1+GH} \right| = \frac{1}{\sqrt{2}} \quad (6.11)$$

$$\Rightarrow \frac{\frac{\mu}{1+\frac{jf}{f_c}}}{1 + \frac{(R_s)}{(R_F)} \frac{\mu}{1+\frac{jf}{f_c}}} = \frac{1}{\sqrt{2}} \quad (6.12)$$

Parameters	Values
R_s	1k Ω
R_F	10k Ω
μ	1000
f_c	1kHz

TABLE 6

Now putting the appropriate values as given in Table 6 we get:

$$\frac{\frac{1000}{1+\frac{jf}{1000}}}{1 + \frac{(1)}{(10)} \frac{1000}{1+\frac{jf}{1000}}} = \frac{1}{\sqrt{2}} \quad (6.13)$$

$$\frac{f^2}{10^{12}} + \frac{101^2}{10^6} = 2 \quad (6.14)$$

$$f \approx 1.41 \text{ MHz} \quad (6.15)$$

$$\frac{V_o}{V_s} = -9.88 \text{ V/V} \quad (7.1)$$

So, to verify this use the following spice file.

spice/ee18btech11011/ee18btech11011.net

and finally to get the result use the following python code.

spice/ee18btech11011/ee18btech11011_spice.py

Result:

figs/ee18btech11011/
ee18btech11011_spice_result.eps

figs/ee18btech11011/
ee18btech11011_spice_result.pdf

Following are the instructions to run the spice file.

spice/ee18btech11011/README.md

7. Using ngspice verify the Closed-Loop Transfer function or V_o/V_s .

Solution: From 5.2 we know that: