

Control Systems

G V V Sharma*

CONTENTS

1	Feedback Voltage Amplifier: Series-Shunt	1
2	Feedback Current Amplifier: Shunt-Series	2
2.1	Ideal Case	2
2.2	Practical Case	4
3	Feedback Current Amplifier: Example	4
4	Feedback Transconductance Amplifier: Series-Series	7

Abstract—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/feedback/codes>

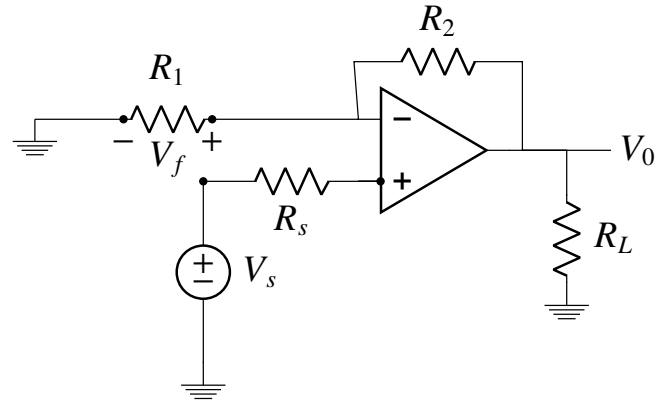


Fig. 1.1.1

Parameter	Value
input resistance	∞
output resistance	0
Input voltage	V_s
Output Voltage	V_o
Feeding resistance	R_1
Feedback resistance	R_2
Source resistance	R_s
load resistance	R_L

TABLE 1.1

1 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

1.1. Fig. 1.1.1 shows a non-inverting op-amp configuration with parameters described in Table 1.1. Draw the equivalent control system.

Solution: See Fig. 1.1.2

1.2. Draw the small signal model for Fig. 1.1.1.

Solution: The equivalent circuit of the amplifier is in Fig. 1.2

1.3. Assuming that the operational amplifier has infinite input resistance and zero output resistance, find the *feedback factor* H .

Solution: From Fig. 1.2,

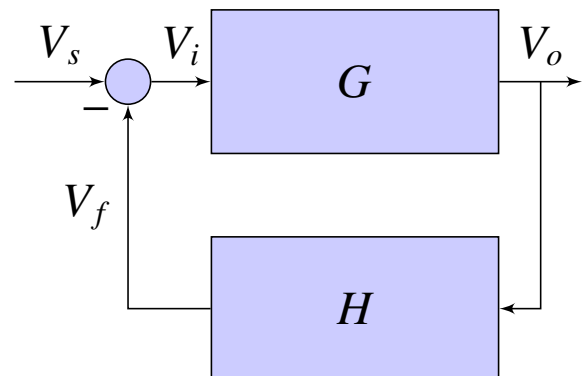


Fig. 1.1.2

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

$$V_o = GV_i \quad (1.3.1)$$

$$V_i = V_s - V_f \quad (1.3.2)$$

$$V_f = \frac{R_1}{R_1 + R_2} V_o \quad (1.3.3)$$

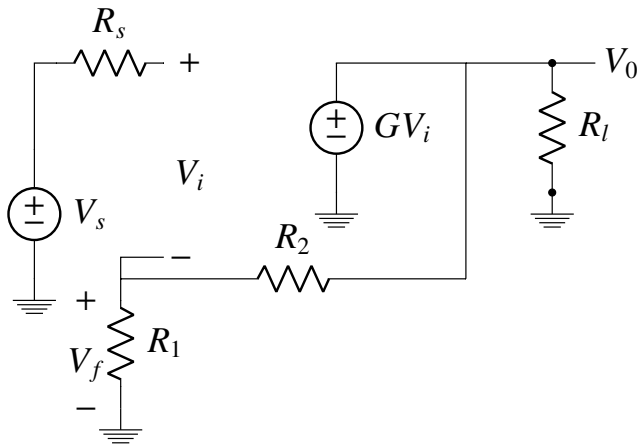


Fig. 1.2

assuming that the current through R_s is very small. Thus,

$$H = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \quad (1.3.4)$$

- 1.4. Obtain the closed loop gain T and summarize your results through a Table.

Solution: Table 1.4 provides a summary.

$$T = \frac{V_o}{V_i} = \frac{G}{1 + GH} \quad (1.4.1)$$

$$= \frac{G(R_1 + R_2)}{(R_1 + R_2) + GR_1} \quad (1.4.2)$$

Parameters	Definition	For given circuit
Open loop gain	G	G
Feedback factor	H	$\frac{R_1}{R_1 + R_2}$
Loop gain	GH	$G \frac{R_1}{R_1 + R_2}$
Amount of feedback	$1 + GH$	$1 + \frac{GR_1}{R_1 + R_2}$
Closed loop gain	$\frac{G}{1 + GH}$	$\frac{G(R_1 + R_2)}{R_1 + R_2 + GR_1}$

TABLE 1.4

- 1.5. Find the condition under which closed loop gain T is almost entirely determined by the feedback network.

Solution: If

$$GH \gg 1, \quad (1.5.1)$$

$$T \approx \frac{1}{H} = 1 + \frac{R_2}{R_1} \quad (1.5.2)$$

- 1.6. If

$$G = 10^4 \quad (1.6.1)$$

$$T = 10, \quad (1.6.2)$$

find H .

Solution: From Table 1.4

$$T = \frac{G}{1 + GH} = 10 \quad (1.6.3)$$

$$\Rightarrow H = 0.0999 \quad (1.6.4)$$

- 1.7. *Gain Desensitivity:* If G decreases by 20%, what is the corresponding decrease in T ? Comment.

Solution: From Table 1.4, Given

$$T = \frac{G}{1 + GH} \quad (1.7.1)$$

$$\Rightarrow dT = \frac{dG}{(1 + GH)^2} \quad (1.7.2)$$

$$\Rightarrow \frac{dT}{T} = \frac{1}{1 + GH} \frac{dG}{G} \quad (1.7.3)$$

From the information available so far,

$$dG = 20\%, G = 10^4, H = 0.0999 \Rightarrow \frac{dT}{T} = 0.025\% \quad (1.7.4)$$

using the following code.

```
codes/ee18btech11005/ee18btech11005.py
```

Thus the closed loop gain is almost invariant to a relatively large (20%) variation in the open loop gain G . This is known as gain desensitivity.

2 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

2.1 Ideal Case

- 2.1.1. Draw the equivalent control system for the feedback current amplifier shown in 2.1.1.1

Solution: See Fig. 2.1.1.2.

- 2.1.1.1. For the feedback current amplifier shown in 2.1.1.1, draw the Small-Signal Model. Neglect the Early effect in Q_1 and Q_2 .

Solution: See Fig. 2.1.2.

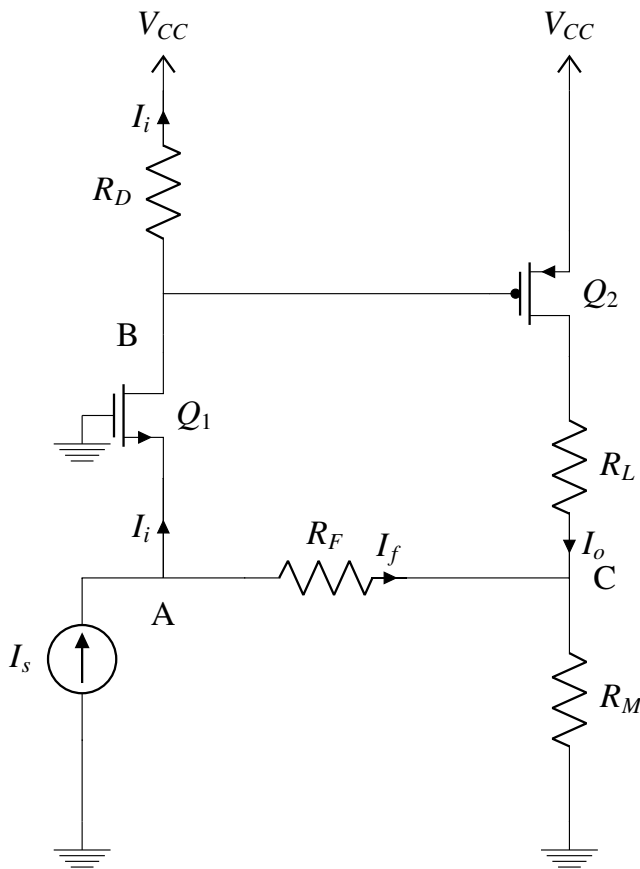


Fig. 2.1.1.1

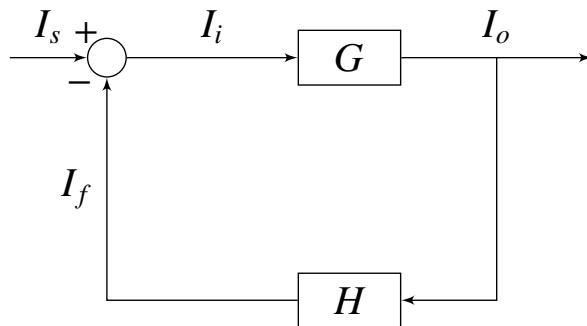


Fig. 2.1.1.2

While drawing a Small-Signal Model, we ground all constant voltage sources and open all constant current sources. All Small-Signal parameters are obtained from DC-Analysis of the circuit. Neglecting Early effect, in Small-Signal Analysis a N-MOSFET is modelled as a Current Source with value of current equal to $g_m v_{gs}$ flowing from Drain to Source. Whereas a P-MOSFET is modelled as a Current Source with value of current equal to $g_m v_{sg}$ flowing from Source to Drain.

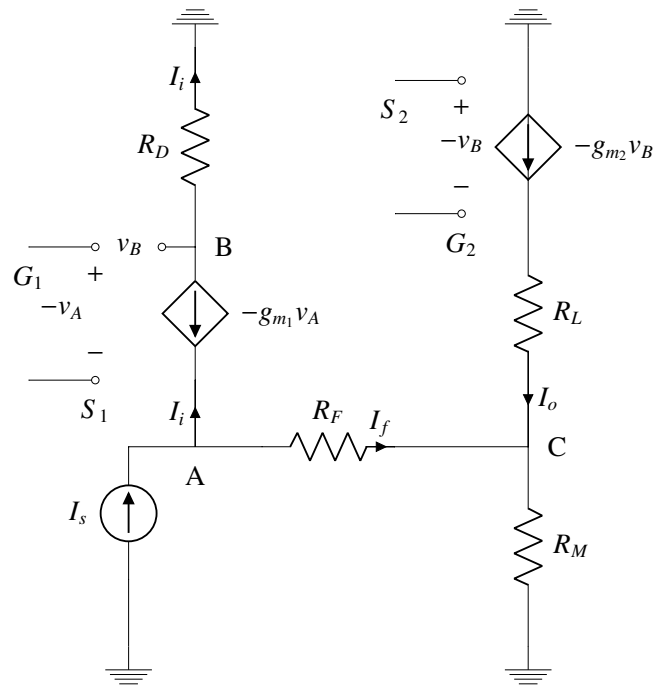


Fig. 2.1.2: Small Signal Model

2.1.3. Write all the node/loop equations using KCL/KVL.

Solution: From Figs. 2.1.1.1 and 2.1.2,

$$I_i = \frac{v_B}{R_D} \quad (2.1.3.1)$$

$$I_o = -g_{m2} v_B \quad (2.1.3.2)$$

$$v_C - v_A = -I_f R_F \quad (2.1.3.3)$$

$$v_C = (I_o + I_f) R_M \quad (2.1.3.4)$$

$$I_i = g_{m1} v_A \quad (2.1.3.5)$$

2.1.4. Find the Expression for the Open-Loop Gain G .

Solution: From (2.1.3.1) and (2.1.3.2),

$$G = \frac{I_o}{I_i} = -g_{m2} R_D \quad (2.1.4.1)$$

2.1.5. Find the Expression of the Feedback Factor H .

Solution:

$$H = \frac{I_f}{I_o}, \quad (2.1.5.1)$$

From (2.1.3.3) and (2.1.3.4),

$$(I_o + I_f) R_M - v_A = -I_f R_F \quad (2.1.5.2)$$

$$\Rightarrow (I_o + I_f) R_M + \frac{I_i}{g_{m1}} = -I_f R_F \quad (2.1.5.3)$$

from (2.1.3.5). Dividing by I_o ,

$$\Rightarrow (1 + H)R_M + \frac{1}{g_{m1}G} = -HR_F \quad (2.1.5.4)$$

upon substituting from and . Simplifying further, we obtain

$$\Rightarrow H = \frac{\frac{1}{g_{m1}g_{m2}R_D} - R_M}{R_F + R_M} \quad (2.1.5.5)$$

$$\approx -\frac{R_M}{R_F + R_M} \quad (2.1.5.6)$$

for $R_M \gg \frac{1}{g_{m1}g_{m2}R_D}$.

2.1.6. Find the Expression for the Closed-Loop Gain $T = \frac{I_o}{I_s}$.

Solution: From (2.1.5) and (2.1.5.6),

$$T = \frac{I_o}{I_s} = \frac{G}{1 + GH} \quad (2.1.6.1)$$

$$= -\frac{g_{m2}R_D}{1 + g_{m2}R_D/\left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.2)$$

2.2 Practical Case

2.2.1. Draw the Block Diagram and Circuit Diagram for H .

Solution: The Block Diagram is available in Fig. 2.2.1.1

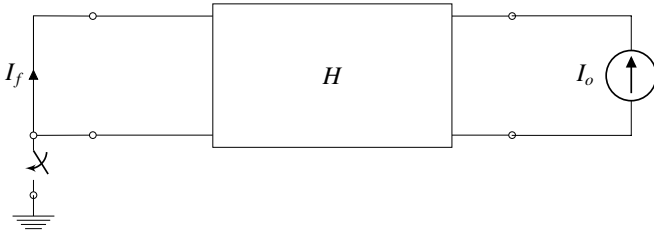


Fig. 2.2.1.1: Feedback Block Diagram

and the corresponding circuit diagram in Fig. 2.2.1.2

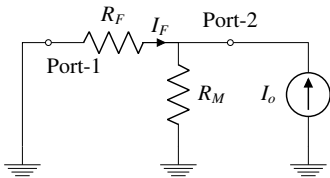


Fig. 2.2.1.2: Feedback Network

2.2.2. Find H from Fig. 2.2.1.2.

Solution: Using current division,

$$\frac{I_f}{I_o} = -\frac{R_M}{R_F + R_M} \quad (2.2.2.1)$$

$$\Rightarrow H = -\frac{R_M}{R_F + R_M} \quad (2.2.2.2)$$

2.2.3. Find R_{11} and R_{22} of Feedback Network where R_{11} is input resistance through Port-1 and R_{22} is Input Resistance through Port-2.

Solution: R_{11} is calculated by opening the current source at Port-2. Hence,

$$R_{11} = R_F + R_M \quad (2.2.3.1)$$

While calculating R_{22} , Port-1 should be shorted. Hence,

$$R_{22} = R_F || R_M \quad (2.2.3.2)$$

$$= \frac{R_F R_M}{R_F + R_M} \quad (2.2.3.3)$$

2.2.4. Draw the block diagram and circuit diagram for calculating G .

Solution: See Figs. 2.2.4.1 and 2.2.4.2

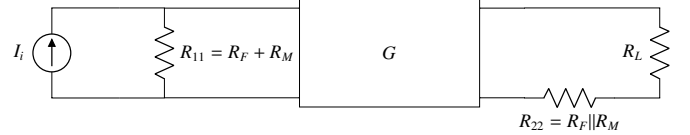


Fig. 2.2.4.1: Open-Loop Block Diagram

2.2.5. Find G .

Solution: The analysis is the same as Problem 2.1.4.

3 FEEDBACK CURRENT AMPLIFIER: EXAMPLE

3.1. Consider a Feedback Current Amplifier formed by cascading an Inverting Opamp μ with a MOSFET (NMOS) as shown in Fig. 3.1.1. The output current is the Drain Current of the NMOS. Assume that Opamp has an input resistance R_{id} , an Open Circuit Voltage Gain μ , and an output resistance r_{o1} . Express this as a control system.

Solution: See Fig. 3.1.2

3.2. Represent Fig. 3.1.1 using a Small Signal Equivalent Model.

Solution: See Fig. 3.2

3.3. Find G .

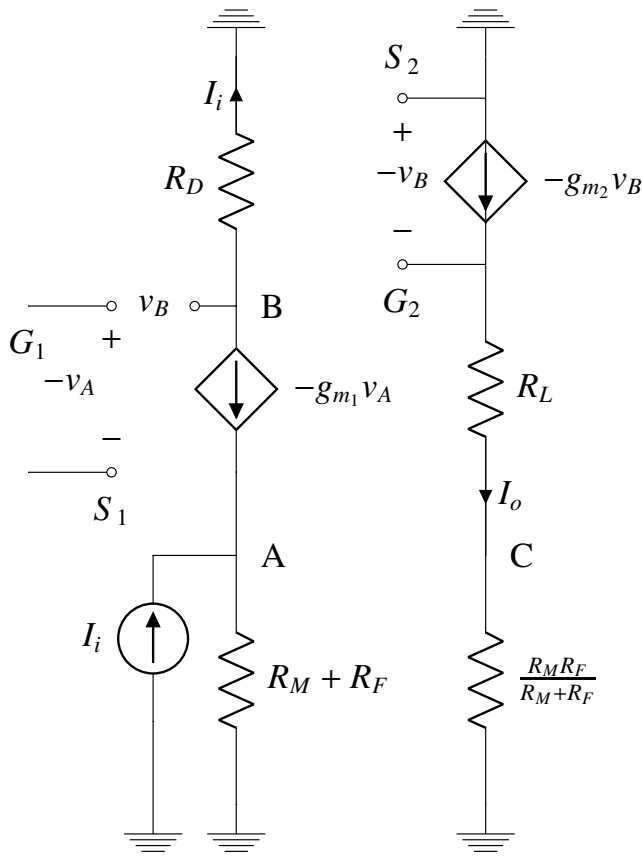


Fig. 2.2.4.2: Open-Loop Network

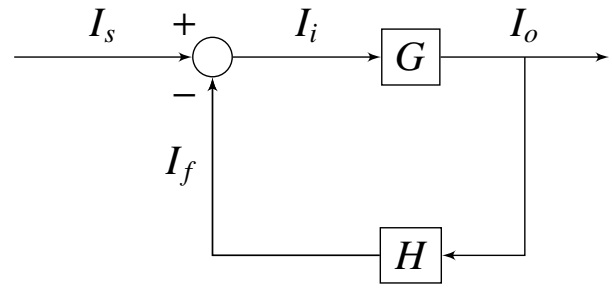


Fig. 3.1.2: Block Diagram

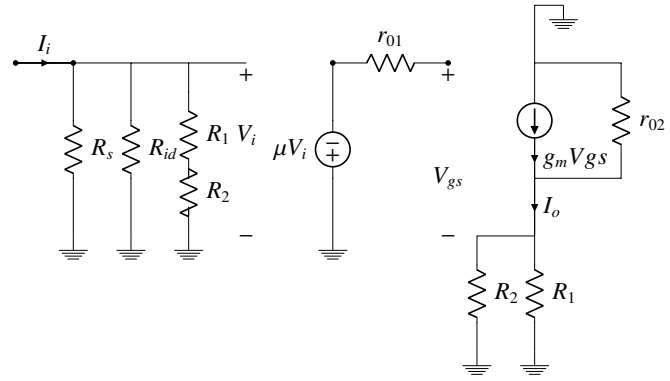


Fig. 3.2: Small Signal Model

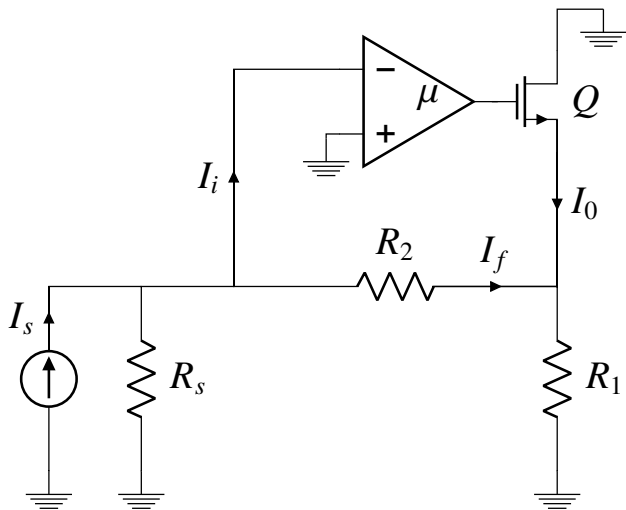


Fig. 3.1.1: Complete Circuit

equations

$$V_g = -\mu V_i \quad (3.3.1)$$

$$\frac{V_i}{R_{id}} = I_i \quad (3.3.2)$$

$$I_s = \frac{V_i}{R_s} + I_f + I_i \quad (3.3.3)$$

$$I_f = \frac{V_i - V_s}{R_2} \quad (3.3.4)$$

$$\frac{V_g}{R_2} = I_f + I_o \quad (3.3.5)$$

$$I_o = g_m (V_g - V_s) + \frac{V_s}{r_{o2}} \quad (3.3.6)$$

$$G = \frac{I_o}{I_i} \quad (3.3.7)$$

$$H = \frac{I_f}{I_o} \quad (3.3.8)$$

$$R_i = R_s || R_{id} || (R_1 + R_2) \quad (3.3.9)$$

Solution: From Fig. 3.2 we have the following

where R_i is the resistance seen by the current source I_s and R_{id} is the internal resistance of

the OPAMP.

$$V_i = I_s R_i \quad (3.3.10)$$

$$I_i = I_s \frac{R_s \parallel (R_1 + R_2)}{R_s + R_{id} + R_1 + R_2} \quad (3.3.11)$$

for small values of I_f .

$$I_o = -\mu V_i \frac{1}{1/g_m + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \quad (3.3.12)$$

$$G = \frac{I_o}{I_i} = -\mu \frac{R_i}{1/g_m + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \quad (3.3.13)$$

We use the approximation

$$1/g_m \ll (R_1 \parallel R_2 \parallel r_{o2}) \quad (3.3.14)$$

This is because the $\frac{1}{g_m}$ is in order of few Ω s but, R_1 , R_2 and r_{o2} are in order of k Ω s

$$G = -\mu \frac{R_i}{R_1 \parallel R_2} \quad (3.3.15)$$

$$R_o = r_{o2} + (R_1 \parallel R_2) + (g_m r_{o2})(R_1 \parallel R_2) \quad (3.3.16)$$

$$\Rightarrow R_o \simeq g_m r_{o2} (R_1 \parallel R_2) \quad (3.3.17)$$

3.4. Find expression for Loop Gain H

Solution:

$$H = \frac{I_f}{I_o} = -\frac{R_1}{R_1 + R_2} \quad (3.4.1)$$

3.5. If loop gain is large, find approximate expression for closed loop gain T

Solution: Given,

$$GH \gg 1 \quad (3.5.1)$$

$$T = \frac{G}{1 + GH} \simeq \frac{1}{H} \quad (3.5.2)$$

$$T \simeq \frac{1}{H} = -\left(1 + \frac{R_2}{R_1}\right) \quad (3.5.3)$$

3.6. Give expressions for GH, T , R_{if} , R_{in} , R_{of} , R_{out}

Solution:

$$GH = \mu \frac{R_i}{\frac{1}{g_m} + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \frac{R_1}{R_1 + R_2} \quad (3.6.1)$$

Once again, using the approximation,

$$\Rightarrow GH \simeq \mu \frac{R_i}{R_1 \parallel R_2} \frac{R_1}{R_1 + R_2} = \mu \frac{R_i}{R_2} \quad (3.6.2)$$

For Input Resistance,

$$R_{if} = R_i / (1 + GH) \quad (3.6.3)$$

$$\Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{\mu}{R_2} \quad (3.6.4)$$

$$\Rightarrow R_{if} = R_i \parallel \frac{R_2}{\mu} \quad (3.6.5)$$

Substituting the value of R_i ,

$$R_{if} = R_s \parallel R_{id} \parallel (R_1 + R_2) \parallel \frac{R_2}{\mu} \quad (3.6.6)$$

$$R_{if} = R_s \parallel R_{in} \quad (3.6.7)$$

$$\Rightarrow R_{in} = R_{id} \parallel (R_1 + R_2) \parallel \frac{R_2}{\mu} \quad (3.6.8)$$

$$R_{in} \simeq \frac{R_2}{\mu} \quad (3.6.9)$$

For Output Resistance,

$$R_{of} = R_o (1 + GH) \simeq GHR_o \quad (3.6.10)$$

$$R_{of} \simeq \mu \left(\frac{R_i}{R_2}\right) (g_m r_{o2}) (R_1 \parallel R_2) \quad (3.6.11)$$

$$R_{out} = R_{of} = \mu \frac{R_i}{R_1 + R_2} (g_m r_{o2}) R_1 \quad (3.6.12)$$

3.7. Given the following values

Parameter	Value
μ	1000
R_s	∞
R_{id}	∞
r_{o1}	1k Ω
R_1	10k Ω
R_2	90k Ω
g_m	5mA/V
r_{o2}	20k Ω

TABLE 3.7

Find numerical value of R_i and use it to find the value of G

Solution: Using the given numerical values on the previously obtained equations, we obtain:

$$R_i = \infty \parallel \infty \parallel (10 + 90) = 100k\Omega \quad (3.7.1)$$

$$G = -1000 \frac{100}{10 \parallel 90} = -11.11 \times 10^3 \quad (3.7.2)$$

- 3.8. Check the validity of the approximation that we use to neglect $1/g_m$

Solution:

$$1/g_m = 0.2k\Omega \ll (10 \parallel 90 \parallel 20)k\Omega = 6.2k\Omega \quad (3.8.1)$$

Hence, we can see that our approximation is valid

- 3.9. Find the value of feedback gain H and open loop gain GH

Solution:

$$H = -\frac{R_1}{R_1 + R_2} = -\frac{10}{10 + 90} = -0.1 \quad (3.9.1)$$

$$GH = 1111 \gg 1 \quad (3.9.2)$$

- 3.10. Find the approximate value of closed loop gain T

Solution:

$$T \simeq \frac{1}{H} = -\frac{1}{0.1} = -10 \quad (3.10.1)$$

- 3.11. Find the values of R_{in} and R_{out}

Solution:

$$R_{in} = \frac{R_2}{\mu} = \frac{90k\Omega}{1000} = 90\Omega \quad (3.11.1)$$

$$R_o = g_m r_{o2} (R_1 \parallel R_2) = 5 \times 20 (10 \parallel 90) = 900k\Omega \quad (3.11.2)$$

$$R_{out} = (1 + GH)R_o = 1112 \times 900 \simeq 1000M\Omega \quad (3.11.3)$$

- 3.12. Verify the above calculations using a Python code.

Solution:

```
codes/ee18btech11021/ee18btech11021_calc.py
```

Parameter	Value
R_i	$100k\Omega$
$1/g_m$	200Ω
G	-1.11×10^4
H	-0.1
GH	1111
T	-10
R_{in}	90Ω
R_o	$900k\Omega$
R_{out}	$1000M\Omega$

TABLE 3.11

4 FEEDBACK TRANSCONDUCTANCE AMPLIFIER: SERIES-SERIES

- 4.1. Part of the circuit of the MC1553 Amplifier is shown in circuit1 in Fig. 4.1.1 with values of various parameters given in Table 4.1. Draw the equivalent block diagrams.

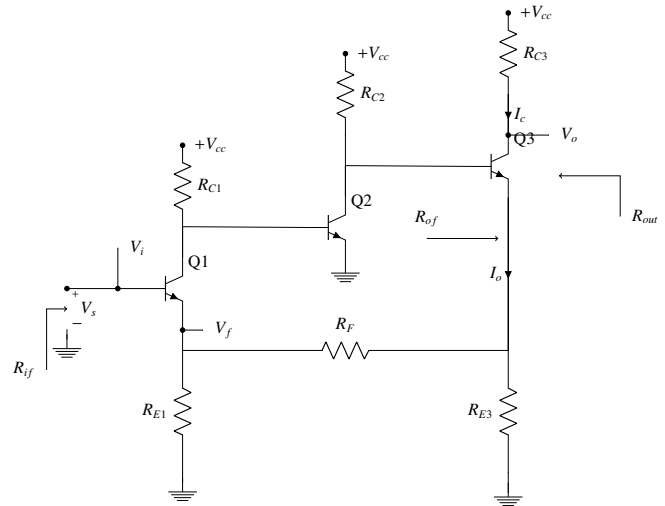


Fig. 4.1.1

Solution: The block diagrams are available in Figs. 4.1.2 and 4.1.3.

- 4.2. Draw the block diagram and equivalent circuit for H for Fig. 4.1.3.

Solution: Fig. 4.2.1 gives the required block diagram

$$H = \frac{V_f}{I_o} \Big|_{I_i=0} \quad (4.2.1)$$

and the equivalent H circuit is available in Fig. 4.2.2.

Parameter	Value
R_{C1}	$9k\Omega$
R_{E1}	100Ω
R_{C2}	$5k\Omega$
R_F	640Ω
R_{E2}	100Ω
R_{C3}	600Ω
h_{fe}	100
r_o	$\infty\Omega$
I_{C1}	0.6mA
I_{C2}	1mA
I_{C3}	4mA
r_{e1}	41.7Ω
$r_{\pi2}$	$2.5k\Omega$
α_1	0.99
g_{m2}	40mA/V
r_{e3}	6.25Ω
r_{o3}	$25k\Omega$
$r_{\pi3}$	625Ω

TABLE 4.1: parameters

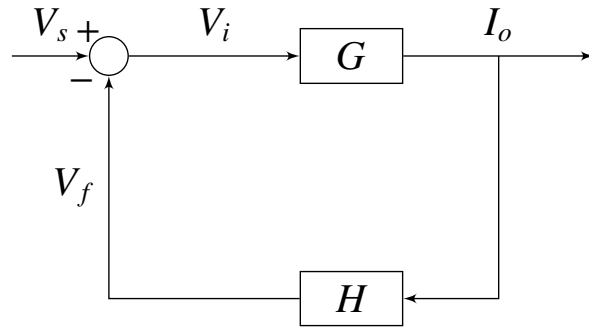


Fig. 4.1.2: block diagram

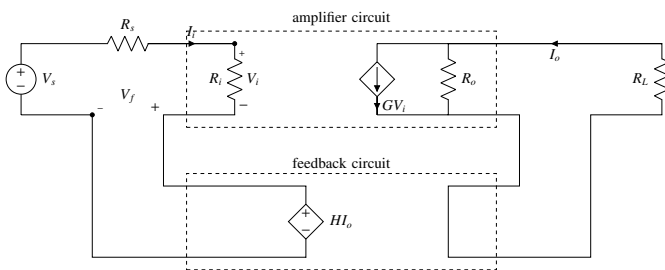


Fig. 4.1.3: Feedback Transconductance Amplifier

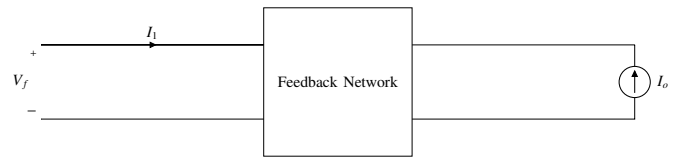


Fig. 4.2.1: Feedback circuit block diagram

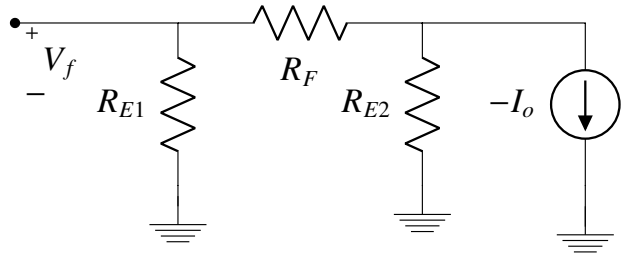


Fig. 4.2.2: H circuit

Solution: From Fig. 4.2.2,

$$H = \frac{V_f}{I_o} = \frac{R_{E1}R_{E2}}{R_{E2} + R_F + R_{E1}} \quad (4.3.1)$$

4.4. Find R_{11} and R_{22} from Figs. 4.4 and 4.2.2

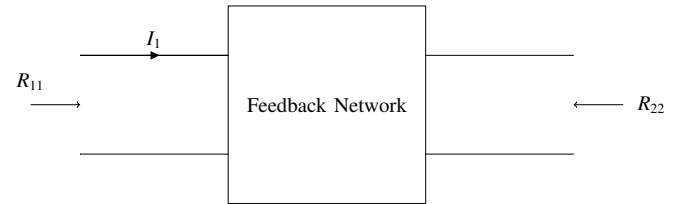


Fig. 4.4: feedback network

Solution:

$$R_{11} = R_{E1} || (R_F + R_{E2}) \quad (4.4.1)$$

$$R_{22} = R_{E2} || (R_F + R_{E1}) \quad (4.4.2)$$

4.5. Draw the block diagram and equivalent circuit for G .

Solution: The required block diagram is available in Fig. 4.5 and the equivalent circuit in

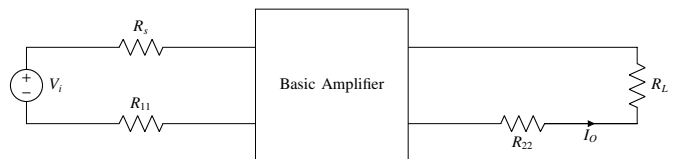


Fig. 4.5: Amplifier circuit block diagram

4.3. Find the feedback Factor H

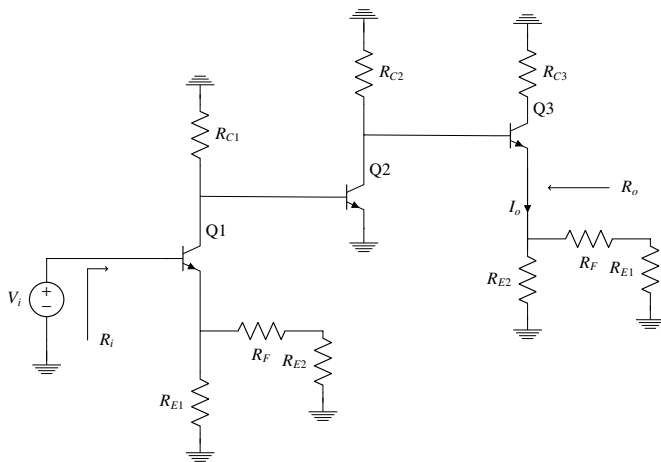


Fig. 4.5: G circuit

4.6. Find G

Solution: To find $G = \frac{I_0}{V_i}$ we determine the gain of first stage, this is written by inspection as-

$$\frac{V_{c1}}{V_i} = \frac{-\alpha(R_{c1} \parallel r_{\pi 2})}{r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))} \quad (4.6.1)$$

Next, we determine the gain of the second stage, which can be written by inspection (noting that $V_{b2} = V_{c1}$) as

$$\frac{V_{c2}}{V_{c1}} = -g_{m2} R_{c2} \parallel [(h_{fe} + 1)[r_{e3} + (R_{E2} \parallel (R_F + R_{E1}))]] \quad (4.6.2)$$

Finally, for the third stage we can write by inspection

$$\frac{I_0}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} \parallel (R_F + R_{E1}))} \quad (4.6.3)$$

4.7. Find closed loop gain T and Voltage Gain V_0/V_s numerically.

Solution:

$$T = \frac{I_0}{V_s} = \frac{G}{1 + GH} = \frac{20.7}{1 + 20.7 \times 11.9} = 83.7 \text{ mA/V} \quad (4.7.1)$$

4.8. Now assume Loop gain is large and find approximate expression for closed loop gain

$$T = \frac{I_0}{V_s}$$

Solution: When $GH \gg 1$,

$$T \approx \frac{I_0}{V_s} \approx \frac{1}{H} \quad (4.8.1)$$

$$= \frac{1}{11.9} = 84 \text{ mA/V} \quad (4.8.2)$$

$$\frac{I_c}{V_s} \approx \frac{I_0}{V_s} = 84 \text{ mA/V} \quad (4.8.3)$$

which we note is very close to the approximate value found in (4.7.1)

4.9. Tabulate all your results.

Solution: See Table 4.9.

Parameter	Value
G	20.7A/V
H	11.9Ω
T	83.7mA/V
V_o/V_s	-50.2V/V
R_{in}	3.38MΩ
R_{out}	2.19MΩ
R_{of}	35.6kΩ

TABLE 4.9: calculated parameters

4.10. Write a code for doing calculations and verify the values obtained in 4.9

Solution: The following code does all the calculations of above equations to give parameters in 4.9

codes/ee18btech11007/circuit_calc.py