

Shunt-Series Amplifiers: Practical Case

Ritwik Sahani*

CONTENTS

The feedback current amplifier in Fig 0 utilizes two identical NMOS transistor sized so that at $I_{D1} = 0.2mA$, they operate at $V_{OV} = 0.2V$. Both the devices have $V_t = 0.5V$ and $V_A = 10V$.

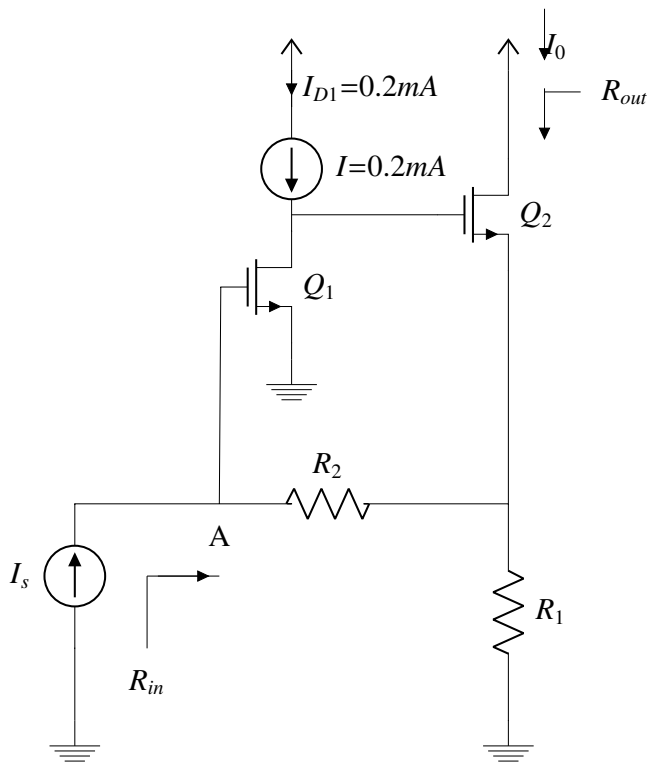


Fig. 0: Problem Figure

- If I_s has zero DC component, show that both Q_1 and Q_2 are, operating at $I_D = 0.2mA$. What is DC voltage at the input?
- Find g_m and r_o for each Q_1 and Q_2 .
- Find the open loop circuit and the value of R_i , G and R_o .

Parameter	Value
R_1	$3.5k\Omega$
R_2	$14k\Omega$
I_{D1}	$0.2mA$
V_{OV}	$0.2V$
V_t	$0.5V$
V_A	$10V$

TABLE 0: Given Parameters

- Find the value of H .
- Find GH and T
- Find R_{in} and R_{out} .

- Find the DC voltage at the node A.

Solution: Given that I_s has zero DC component, it can be neglected in DC analysis of the circuit. The current does not enter the Gate terminal of any mosfet. Thus the DC current flow is as shown in Fig 1.2

$$V_{GS1} = V_{OV} + V_t = 0.7V \quad (1.1)$$

$$\Rightarrow V_A = V_{G1} = V_{GS1} = 0.7V \quad (1.2)$$

- Show that the drain current for Q_2 is $I_{D2} = 0.2mA$.

Solution:

$$\because I_s = 0 \text{ and } I_{G1} = 0, \quad (2.1)$$

no current passes through R_2 and

$$\because I_s = 0 \text{ and } V_{S2} = V_A = 0.7 \quad (2.2)$$

$$\Rightarrow I_{D2} = \frac{V_{S2}}{R_1} \quad (2.3)$$

$$\Rightarrow I_{D2} = 0.2mA \quad (2.4)$$

- To find g_m and r_o

Solution: We know,

$$\text{transconductance, } g_m = \frac{2I_D}{V_{OV}} \quad (3.1)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

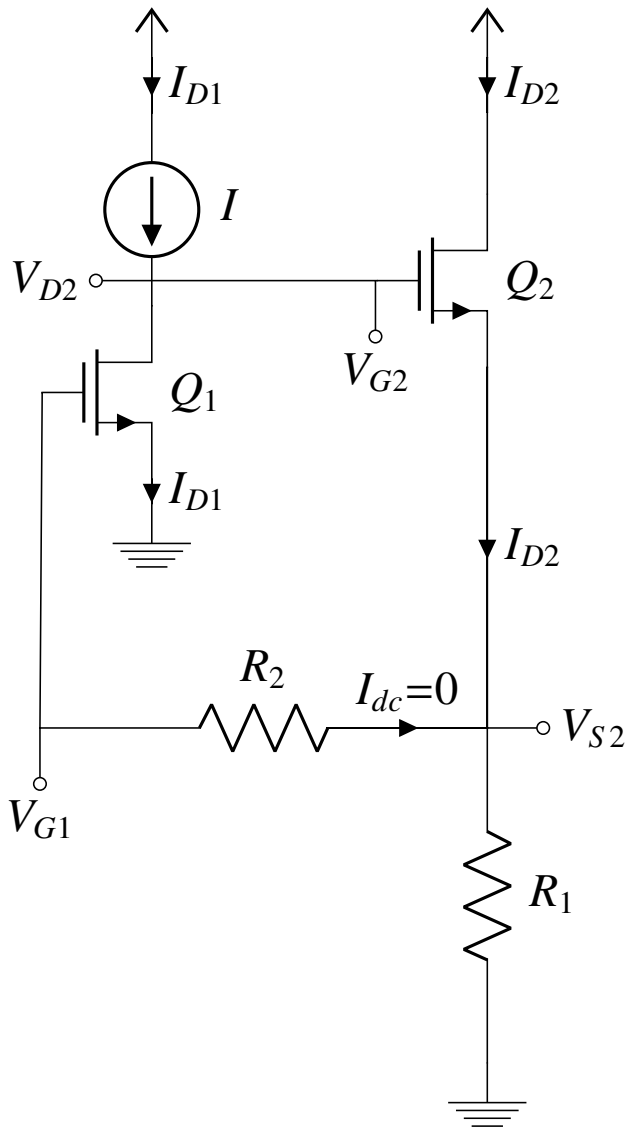


Fig. 1.2: DC Analysis Circuit

therefore-

$$g_{m1} = g_{m2} = \frac{(2)(0.2)(10^{-3})}{0.2} \quad (3.2)$$

$$\Rightarrow 2mA/V \quad (3.3)$$

r_o is given by,

$$r_o = \frac{V_A}{I_D} \quad (3.4)$$

$$\Rightarrow r_{o1} = r_{o2} = 50k\Omega \quad (3.5)$$

4. c) To find open loop circuit.

Solution: The general open loop circuit for a current(series-shunt) amplifier is shown in Fig 4.3.

For our problem, the small circuit model is

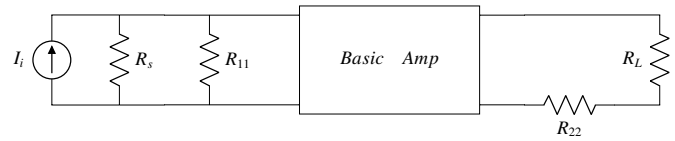


Fig. 4.3: General open loop circuit

Resistance	Description
R_{in}	Total Input Resistance
R_{out}	Total Output Resistance
r_{o1}	Output resistance of MOSFET1
r_{o2}	Output resistance of MOSFET2
R_i	Input resistance of Open Loop
R_o	Output resistance of Open Loop
R_{if}	Input resistance of Feedback
R_{of}	Output resistance of Feedback
R_s	Resistance of Current Source
R_L	Output Load Resistance
R_{11}	Input load resist. (due feedback)
R_{22}	Output load resist. (due feedback)

TABLE 4: Resistances

shown in Fig 4.4. All the different resistances are summarized in Table 4

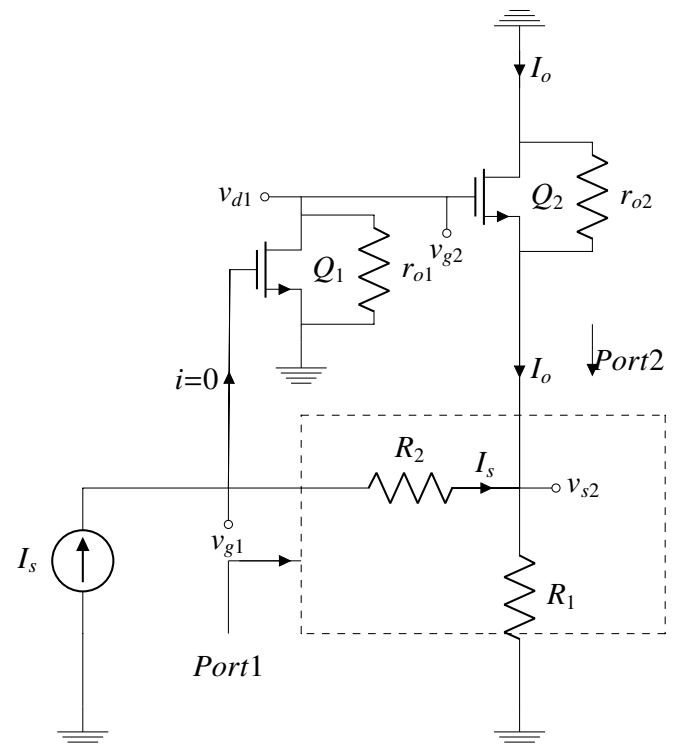


Fig. 4.4: Small Circuit Model

$$\Rightarrow R_\rho = r_{\rho 2} + R_1 \| R_2 + g_{m2} r_{\rho 2} (R_1 \| R_2) \quad (6.4)$$

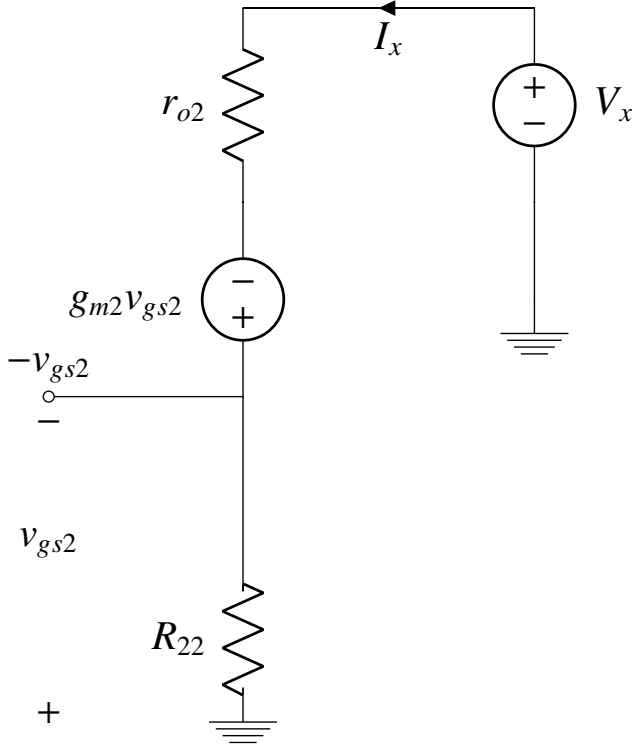


Fig. 6.7: Simplified Output Circuit

7. d) To find feedback gain,
- H

Solution: We know,

$$H = \frac{I_f}{I_0}, \text{ port1 shorted} \quad (7.1)$$

$$(7.2)$$

Therefore,

$$H = \frac{-R_1}{R_1 + R_2} \quad (7.3)$$

8. e) To find closed-loop gain
- T

Solution:

$$GH = \frac{g_{m1}g_{m2}r_{o1}R_1}{g_{m2}(R_1||R_2) + \frac{R_1||R_2}{r_{o2}||R_1||R_2}} \quad (8.1)$$

We know,

$$T = \frac{G}{1 + GH} \quad (8.2)$$

$$(8.3)$$

$$\Rightarrow \frac{-g_{m1}g_{m2}r_{o1}(R_1 + R_2)}{g_{m2}(R_1||R_2) + \frac{R_1||R_2}{r_{o2}||R_1||R_2} + g_{m1}g_{m2}r_{o1}R_1} \quad (8.4)$$

9. f) To find
- R_{in}
- and
- R_{out}

Solution: Since $R_L = 0$ and $R_s = \infty$,

$$R_{in} = R_{if} = \frac{R_i}{1 + GH} \quad (9.1)$$

and,

$$R_{out} = R_{of} = (1 + GH)R_o \quad (9.2)$$

Refer 5.1 for R_i and 6.4 for R_o . Expressions are large for R_{out} and R_{in} . Numerical values are calculated in Table 9.

Parameter	Value
g_{m1}	2mA/V
g_{m2}	2mA/V
r_{o1}	$50\text{k}\Omega$
r_{o2}	$50\text{k}\Omega$
R_s	∞
R_L	0
G	-526.3
R_i	$17.5\text{k}\Omega$
R_o	$332.8\text{k}\Omega$
H	-0.2
GH	105.26
T	-4.95
R_{in}	164Ω
R_{out}	$35.3\text{M}\Omega$

TABLE 9: Numerical Values