

Control Systems

G V V Sharma*

CONTENTS

1	Feedback Voltage Amplifier: Series-Shunt	1
1.1	Introduction	1
2	Feedback Current Amplifier: Shunt-Series	3
2.1	Introduction	3

Abstract—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

```
svn co https://github.com/gadepall/school/trunk/control/codes
```

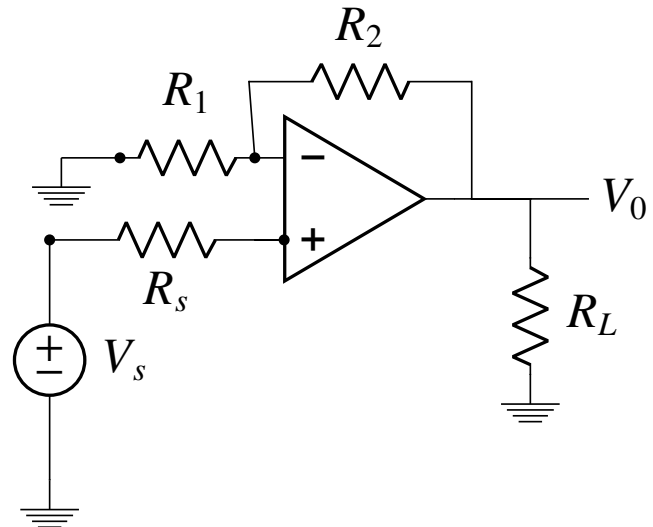


Fig. 1.1.1.1

1 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

1.1 Introduction

1.1.1. Fig. 1.1.1.1 shows a non-inverting op-amp configuration with parameters described in Table 1.1.1. Draw the equivalent control system.

Parameter	Value
input resistance	∞
output resistance	0
Input voltage	V_s
Output Voltage	V_o
Feedback resistance	R_2
load resistance	R_L

TABLE 1.1.1

Solution: See Fig. 1.1.1.2

1.1.2. Draw the small signal model for Fig. 1.1.1.1.

Solution: The equivalent circuit of the amplifier is in Fig. 1.1.2

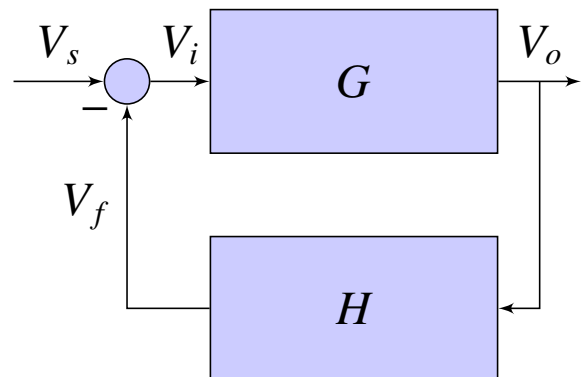


Fig. 1.1.1.2

1.1.3. Assuming that the operational amplifier has infinite input resistance and zero output resistance, find the *feedback factor* H . **Solution:** Let the gain of the operational amplifier be G . From the equivalent circuit, Applying Ohms law,

$$V_o = G(V_i) \quad (1.1.3.1)$$

$$\text{and, } V_i = V_+ - V_- \quad (1.1.3.2)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

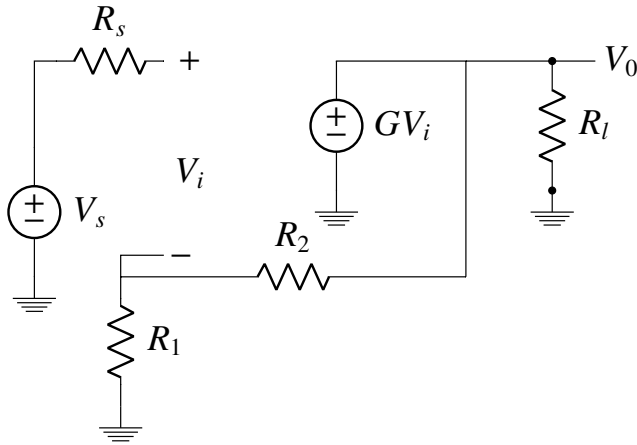


Fig. 1.1.2

Now, Applying voltage dividing rule

$$V_- = \left[\frac{R_1}{R_1 + R_2} \right] V_0 \quad (1.1.3.3)$$

Substituting in equ.1.1.3.1

$$V_0 = G(V_+ - \left[\frac{R_1}{R_1 + R_2} \right] V_0) \quad (1.1.3.4)$$

$$\Rightarrow V_0 = GV_+ - G \left[\frac{R_1}{R_1 + R_2} \right] V_0 \quad (1.1.3.5)$$

$$G(V_+) = V_0 + G \left[\frac{R_1}{R_1 + R_2} \right] V_0 \quad (1.1.3.6)$$

But,

$$V_s = V_+ \quad (1.1.3.7)$$

because, no current flows through resistor.

$$V_0 = G \left[\frac{1}{1 + \frac{GR_1}{R_1 + R_2}} \right] V_s \quad (1.1.3.8)$$

$$\text{Gain} = \frac{V_0}{V_s} = \left[\frac{G}{1 + \frac{GR_1}{R_1 + R_2}} \right] \quad (1.1.3.9)$$

For a negative feedback system,

$$\frac{V_0}{V_i} = \frac{G}{1 + GH} \quad (1.1.3.10)$$

$$\text{where, } H = \frac{R_1}{R_1 + R_2} \quad (1.1.3.11)$$

The equation.1.1.3.1 looks exactly similar to the Gain of a negative feedback system with

- Open loop gain = G
- Loop gain = P
- Amount of feedback = F

- Feedback factor = f
- closed loop gain = T

Parameters	Definition	For given circuit
Open loop gain	G	G
Feedback factor	H	$\frac{R_1}{R_1 + R_2}$
Loop gain	GH	$G \frac{R_1}{R_1 + R_2}$
Amount of feedback	1+GH	$1 + \frac{GR_1}{R_1 + R_2}$
Closed loop gain	$\frac{G}{1+GH}$	$\frac{G(R_1 + R_2)}{R_1 + R_2 + GR_1}$

TABLE 1.1.3

Therefore, So, the feedback factor ...

$$f = H = \frac{R_1}{R_1 + R_2} \quad (1.1.3.12)$$

1.1.4. Find the condition under which closed loop gain T is almost entirely determined by the feedback network. **Solution:** For T to entirely dependent on feedback network, it should be independent on G(open loop gain) T is given by...

$$T = \frac{G}{1 + \frac{GR_1}{R_1 + R_2}} \quad (1.1.4.1)$$

$$(1.1.4.2)$$

For T to be independent on G..

$$GH \gg 1 \quad (1.1.4.3)$$

$$G \frac{R_1}{R_1 + R_2} \gg 1 \quad (1.1.4.4)$$

$$G \gg 1 + \frac{R_2}{R_1} \quad (1.1.4.5)$$

Under such condition..

$$T = \frac{1}{H} \quad (1.1.4.6)$$

$$T = \frac{R_1 + R_2}{R_1} \quad (1.1.4.7)$$

$$T = 1 + \frac{R_2}{R_1} \quad (1.1.4.8)$$

so, the necessary condition for T depend only

on feedback network is

$$G \gg T \quad (1.1.4.9)$$

1.1.5. If the open loop voltage gain

$$G = 10^4 \quad (1.1.5.1)$$

Find the ratio of R2 and R1 to obtain a closed loop gain of 10. **Solution:** The closed loop gain T is given by

$$T = \frac{G}{1 + GH} = \frac{G}{1 + \frac{GR_1}{R_1 + R_2}} = 10 \quad (1.1.5.2)$$

$$\text{where...} G = 10^4 \quad (1.1.5.3)$$

$$10 = \frac{10^4}{1 + \frac{10^4 R_1}{R_1 + R_2}} \quad (1.1.5.4)$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = \frac{10^4}{\frac{10^4}{10} - 1} \quad (1.1.5.5)$$

$$1 + \frac{R_2}{R_1} = 10.010 \quad (1.1.5.6)$$

$$\frac{R_2}{R_1} = 9.010 \quad (1.1.5.7)$$

1.1.6. What is the amount of feedback in decibels?
Solution: The value of F in decibals is given by

$$F(dB) = 20 \log(F) \quad (1.1.6.1)$$

$$\text{where...} F = 1 + GH \quad (1.1.6.2)$$

$$F = \frac{G}{T} \quad (1.1.6.3)$$

$$\text{where...} G = 10^4 \quad (1.1.6.4)$$

$$T = 10 \quad (1.1.6.5)$$

$$F(dB) = 20 \log\left(\frac{10^4}{10}\right) = 20 \log(1000) \quad (1.1.6.6)$$

$$F(dB) = 60dB \quad (1.1.6.7)$$

1.1.7. If G decreases by 20%, what is the corresponding decrease in T? **Solution:** Given

$$G = 10^4 \quad (1.1.7.1)$$

If G decrease by 20% then, the value of G is..,

$$G = (1 - 0.2)10^4 \quad (1.1.7.2)$$

$$= 8000 \quad (1.1.7.3)$$

For this value of G and ,

$$\frac{R_2}{R_1} = 9.010 \quad (1.1.7.4)$$

The value of T can be solved as follows,

$$T = \frac{G}{1 + \frac{GR_1}{R_1 + R_2}} \quad (1.1.7.5)$$

$$T = \frac{8000}{1 + \frac{8000}{1+0.9010}} \quad (1.1.7.6)$$

$$T = 9.99749 \quad (1.1.7.7)$$

The percentage change in T is..,

$$\text{fractional change} = \frac{10 - 9.99749}{10} \quad (1.1.7.8)$$

$$= 2.51 \times 10^{-4} \quad (1.1.7.9)$$

$$\% \text{change in } T = 0.00251 \quad (1.1.7.10)$$

Therefore T decreases by 0.0025% when G decreases by 20%

1.1.8. Write a python code that can compute closed loop gain, loop gain, amount of feedback given all input parameters. **Solution:** Code to compute different gains.,

codes/ee18btech11005/ee18btech11005.py

2 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

2.1 Introduction

2.1.1. Draw the equivalent control system for the feedback current amplifier shown in 2.1.1.4

Solution: See Fig. 2.1.1.5.

2.1.2. For the feedback current amplifier shown in 2.1.1.4, draw the Small-Signal Model. Neglect the Early effect in Q_1 and Q_2 .

Solution: See Fig. 2.1.2.

While drawing a Small-Signal Model, we ground all constant voltage sources and open all constant current sources. All Small-Signal parameters are obtained from DC-Analysis of the circuit. Neglecting Early effect, in Small-Signal Analysis a N-MOSFET is modelled as a Current Source with value of current equal to $g_m v_{gs}$ flowing from Drain to Source. Whereas a P-MOSFET is modelled as a Current Source with value of current equal to $g_m v_{sg}$ flowing from Source to Drain.

2.1.3. Describe how the given circuit is a Negative Feedback Current Amplifier.

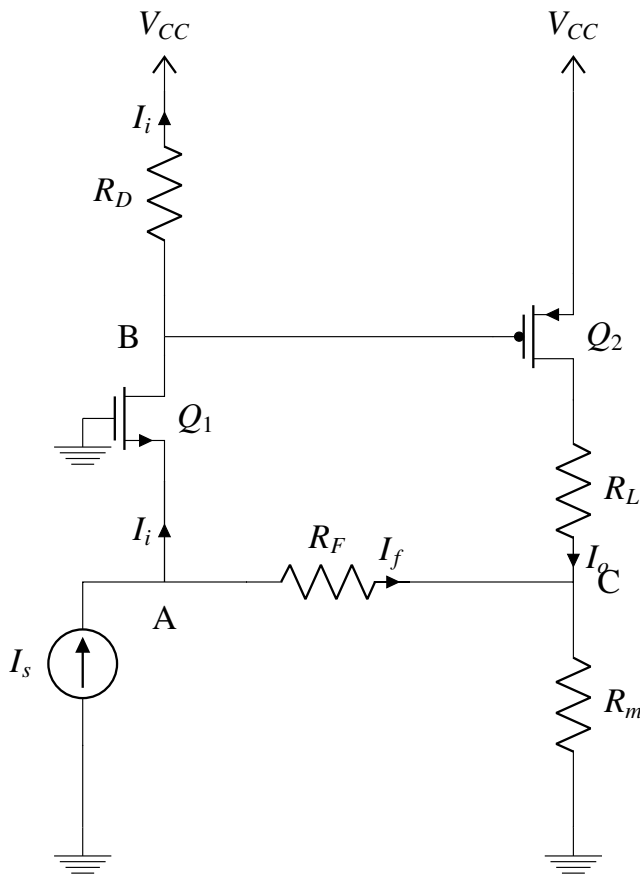


Fig. 2.1.1.4

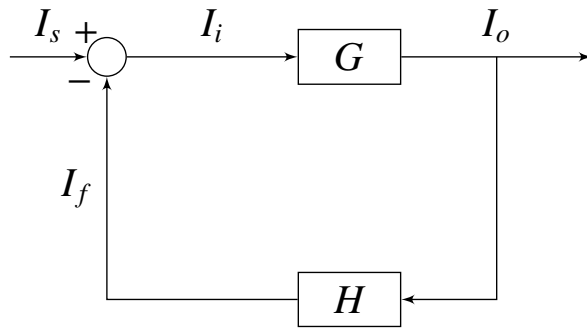


Fig. 2.1.1.5

Solution: For the feedback to be negative, I_f must have the same polarity as I_s . To ascertain that this is the case, we assume an increase in I_s and follow the change around the loop: An increase in I_s causes I_i to increase and the drain voltage of Q_1 will increase. Since this voltage is applied to the gate of the p-channel device Q_2 , its increase will cause I_o , the drain current of Q_2 , to decrease. Thus, the voltage across R_M will decrease, which will cause I_f to increase. This is the same polarity assumed

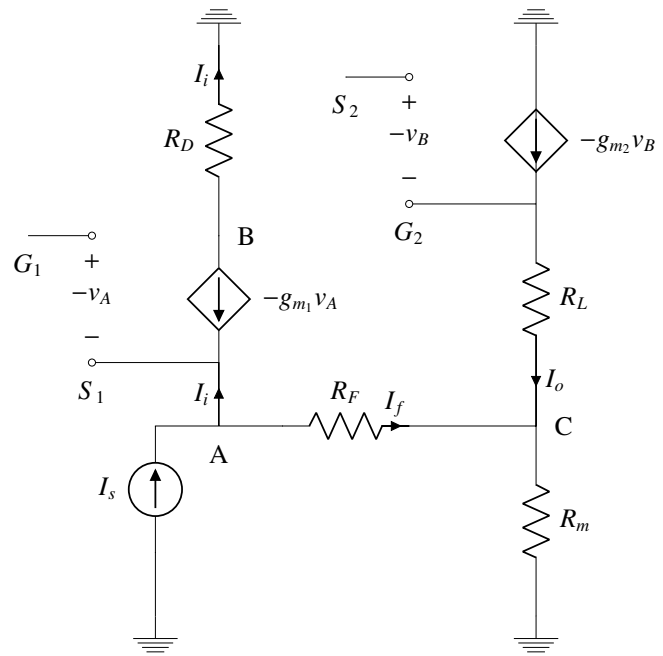


Fig. 2.1.2: Small Signal Model

for the initial change in I_s , verifying that the feedback is indeed negative.

- 2.1.4. Find the Expression for the Open-Loop Gain $G = \frac{I_o}{I_i}$, from the Small-Signal Model. in Fig. 2.1.2.

Solution: In Small-Signal Model,

$$v_B = I_i R_D \quad (2.1.4.1)$$

$$v_{gs2} = v_B = I_i R_D \quad (2.1.4.2)$$

In Small-Signal Analysis, P-MOSFET is modelled as a current source where current flows from Source to Drain. So, the value of current flowing from Source to Drain in P-MOSFET is,

$$I_o = -g_{m2} v_{gs2} = -g_{m2} I_i R_D \quad (2.1.4.3)$$

So, the Open-Circuit Gain is

$$G = \frac{I_o}{I_i} = -g_{m2} R_D \quad (2.1.4.4)$$

- 2.1.5. Find the Expression of the Feedback Factor $H = \frac{I_f}{I_o}$, from Small-Signal Model.

Solution: I_o is fed to a current divider formed by R_M and R_F . R_F is a Large Resistance compared to Input resistance of Amplifier and so most of the current flows through it leaving a small current as input to Amplifier. Hence the voltage at point 'A' is very small and is

considered, $v_A \simeq 0$. So R_F and R_M are parallel and Voltage Drop across them is same.

$$(I_o + I_f)R_M \simeq -I_f R_F \quad (2.1.5.1)$$

$$\frac{I_f}{I_o} \simeq -\frac{R_M}{R_F + R_M} \quad (2.1.5.2)$$

So, the Feedback Factor,

$$H \equiv \frac{I_f}{I_o} \simeq -\frac{R_M}{R_F + R_M} \quad (2.1.5.3)$$

2.1.6. Find the Expression for the Closed-Loop Gain

$$T = \frac{I_o}{I_s}.$$

Solution: From (2.1.4.4) and (2.1.5.3),

$$T = \frac{I_o}{I_s} = \frac{G}{1 + GH} \quad (2.1.6.1)$$

$$= -\frac{g_{m2}R_D}{1 + g_{m2}R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.2)$$

$$\Rightarrow T = -\frac{g_{m2}R_D}{1 + g_{m2}R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.3)$$