

OPAMP Compensation

K.Surya Prakash *
ee18btech11026@iith.ac.in

An op amp with open-loop voltage gain of 10^4 and poles at 10^6 , 10^7 and 10^8 Hz is to be compensated by the addition of a fourth dominant pole to operate stably with unity feedback ($|H| = 1$). What is the frequency of the required dominant pole? The compensation network placed in the negative feedback path of the op amp. The dc bias conditions are such that a $1M\Omega$ resistor can be tolerated in series with each of the negative and positive input terminals. What capacitor is required between the negative input and ground to implement the required fourth pole?

1. Find $G(s)$ for the OPAMP.

Solution:

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{P_1}\right)\left(1 + \frac{s}{P_2}\right)\left(1 + \frac{s}{P_3}\right)} \quad (1.1)$$

where the gain and poles are listed in Table 1.

Parameters	Value
P_1	$2\pi 10^6$ rad/sec
P_2	$2\pi 10^7$ rad/sec
P_3	$2\pi 10^8$ rad/sec
G_0	10^4

TABLE 1

2. Find the 4th dominant pole P_D that will stabilize the system.

Solution: Let the pole frequency be f_D . The 4 pole system will be stable if the gain begins to rolloff from 80dB at a -20 dB/dec rate from f_D and continues until f_{P1} where it cuts 0dB line. From Fig. 2.1,

$$f_D = \frac{f_{P1}}{10^4} \quad (2.1)$$

$$\Rightarrow f_D = 10^2 \text{ Hz} \quad (2.2)$$

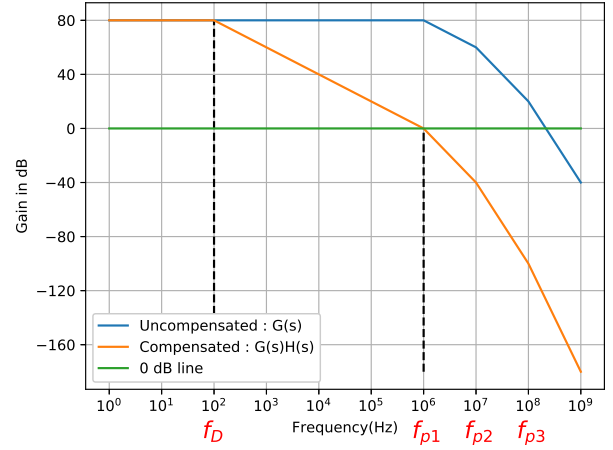


Fig. 2: Bode Plot using asymptotic approximations

3. Draw the block diagram for the stabilized circuit.

Solution: See Fig. 3.1, where

$$P_D = \frac{1}{R_f C_f} \quad (3.1)$$

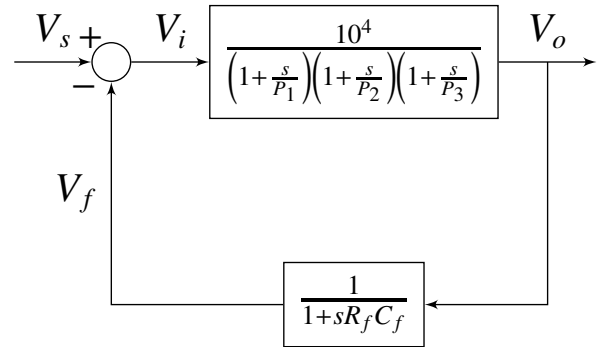


Fig. 3: Block Diagram

4. Design the OPAMP circuit for Fig. 3.1.

Solution: See Fig. 4.1.

$$H(s) = \frac{V_f}{V_o} = \frac{1}{1 + sR_f C_f} \quad (4.1)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

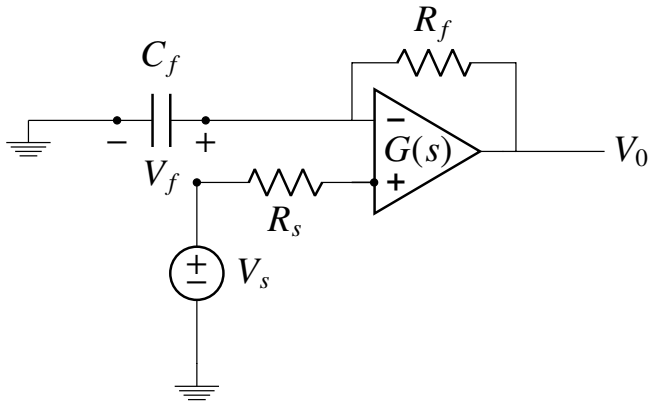


Fig. 4

5. Find R_f and C_f .

Solution:

$$\therefore P_D = 2\pi f_D, \quad (5.1)$$

$$C_f = \frac{1}{2\pi R_f f_D} \quad (5.2)$$

Choosing

$$R_f = R_s = 1M\Omega, C_f = 1.59nF \quad (5.3)$$

Table 5 summarizes this.

Elements	Value
R_f	$1M\Omega$
R_s	$1M\Omega$
C_f	1.59 nF

TABLE 5

6. Verify stability using Bode plots.

Solution: The loop gain of the compensated system is

$$\begin{aligned} L(s) &= G(s)H(s) \\ &= \frac{10^4}{(1 + sR_fC_f)(1 + \frac{s}{P_1})(1 + \frac{s}{P_2})(1 + \frac{s}{P_3})} \end{aligned} \quad (6.1)$$

The closed loop gain

$$T(s) = \frac{G(s)}{1 + L(s)} \quad (6.2)$$

Let

$$\angle L(j\omega_{180}) = -180^\circ \quad (6.3)$$

Then, for stability,

$$|L(j\omega_{180})| < 1 \quad (6.4)$$

For the uncompensated System

$$L_1(s) = G(s) \quad (6.5)$$

and

$$L_2(s) = G(s)H(s) \quad (6.6)$$

for the compensated system . The following code plots Figs. 2.1 and 6.1.

codes/ee18btech11026/ee18btech11026_1.py

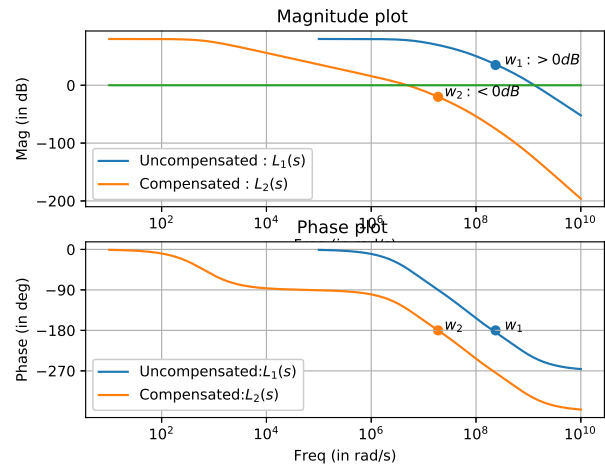


Fig. 6: Bode Plots for verification

From Fig. 6.1,

$$|L_1(j\omega_{180})| > 1 \quad (6.7)$$

$$\Rightarrow L_1 \text{ is unstable} \quad (6.8)$$

$$|L_2(j\omega_{180})| < 1 \quad (6.9)$$

$$\Rightarrow L_2 \text{ is stable} \quad (6.10)$$

Thus, $H(s)$ stabilizes the unity feedback system.

7. Describe the functionality of the feedback circuit.

Solution: The following code plots the Bode plot of $T(s)$ in Fig. 7.1.

codes/ee18btech11026/time_res.py

It can be seen that the feedback circuits acts as a DC buffer. It also behaves like a band pass filter and amplifies the frequencies lying between 0.1 MHz to 10 MHz.

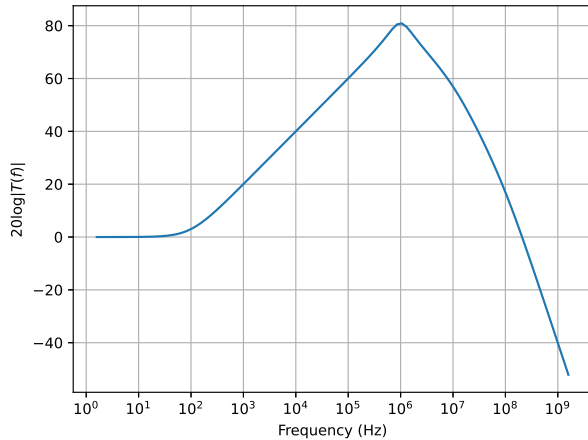


Fig. 7: Bode Plots of T(s)

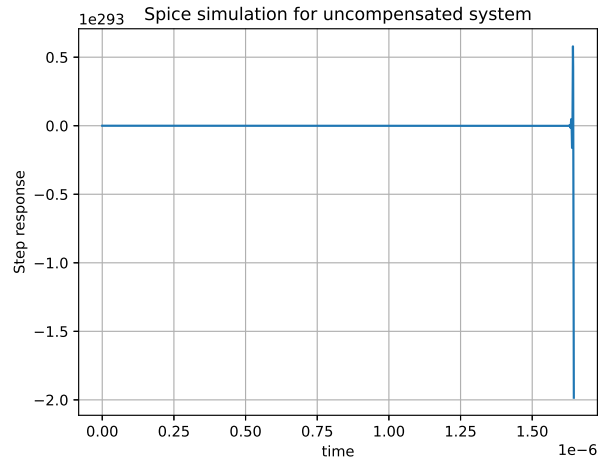


Fig. 8.1: Step response of Uncompensated System

8. Simulate the circuit using ngspice.

Solution: The following code provides instructions about the spice simulation.

```
codes/ee18btech11026/spice/README.md
```

The following netlist simulates the unity feedback system.

```
codes/ee18btech11026/spice/buffer_fb.net
```

The step response in spice is plotted using the following code in Fig. 8.1

```
codes/ee18btech11026/spice/
ee18btech11026_buffer.py
```

We can observe that the step response shoots up to a very large value (10^{293}). This was a consequence for the initial system being unstable.

The following netlist simulates the compensated system.

```
codes/ee18btech11026/spice/rc_bf.net
```

The step response in spice is plotted using the following code in Fig. 8.2

```
codes/ee18btech11026/spice/
ee18btech11026_rc_fb.py
```

Here we can observe that the system has a transient response and it eventually goes to 1. Fig. 8.4 shows how the circuit is actually implemented in spice using the parameters in Table 8

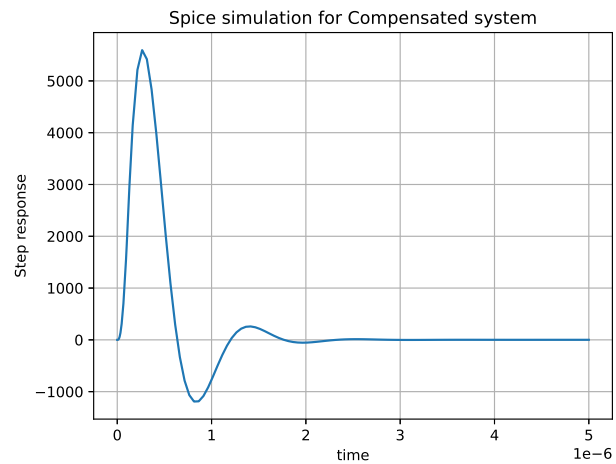


Fig. 8.2: Step response of Compensated System

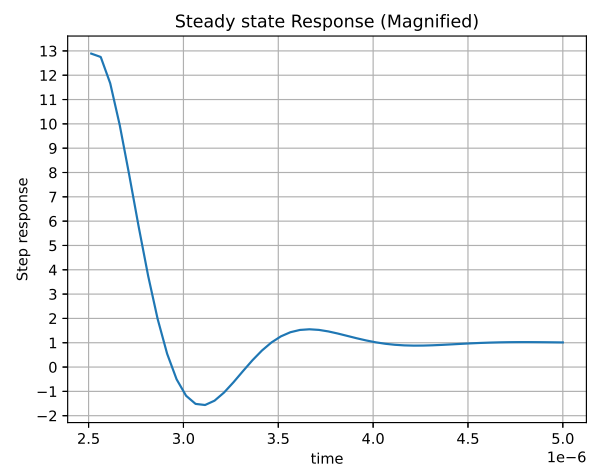


Fig. 8.3: Magnified Plot focussing on steady state

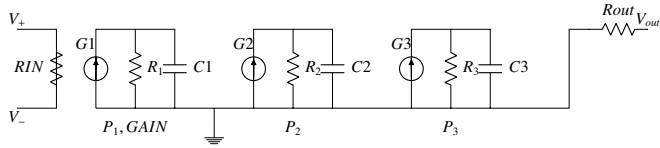


Fig. 8.4: Circuit resembling $G(s)$

Elements	Value
G_1	$10^{-2}(V_+ - V_-)A/V$
G_2	$10^{-6}A/V$
G_3	$10^{-6}A/V$
R_1	$1M\Omega$
R_2	$1M\Omega$
R_3	$1M\Omega$
C_1	$0.159pF$
C_2	$0.0159pF$
C_3	$0.00159pF$
R_{IN}	$1000M\Omega$
R_{OUT}	100Ω
R_f	$1M\Omega$
C_f	$1.59nF$
R_s	$1M\Omega$

TABLE 8