

Control Systems

G V V Sharma*

CONTENTS

Abstract—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/codes>

1 FEEDBACK CIRCUITS

1.1. The CE BJT amplifier in Fig. ?? employs shunt–shunt feedback: Feedback resistor R_F senses the output Voltage V_o and provides a feedback current to the base node. ($R_f = 56k\Omega$, $R_C = 5.6k\Omega$, $R_S = 10k\Omega$)

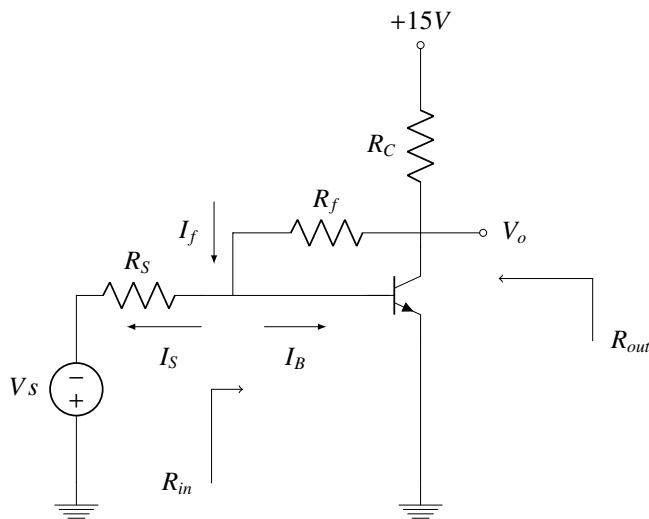


Fig. 1.1

1.2. If V_s has a zero dc component, find the dc collector current of the BJT. Assume the transistor $H = 100$.

Solution: Since, $V_E = 0$ and $V_S = V_{BE}$

$$I_S = \frac{V_{BE}}{R_S} = \frac{0.7}{10 * 10^3} \quad (1.2.1)$$

$$\Rightarrow I_S = 0.07mA \quad (1.2.2)$$

Applying KCL at feedback resistor output

$$-V_o + V_{BE} + I_f R_f = 0$$

$$(Since, I_f = I_B + I_S)$$

$$V_o = V_{BE} + (I_B + I_S) R_f$$

$$= 0.7 + (I_B + 0.07 * 10^{-3})(56 * 10^3)$$

$$\Rightarrow V_o = (56 * 10^3) I_B + 4.62 \quad (1.2.3)$$

Applying KCL at collector node

$$\frac{V_o - 15}{5.6 * 10^3} + I_C + I_f = 0$$

$$(Since, I_C = H I_B)$$

$$\frac{V_o - 15}{5.6 * 10^3} + H I_B + (I_B + I_S) = 0$$

$$\frac{V_o - 15}{5.6 * 10^3} + (100 + 1) I_B + (0.07 * 10^{-3}) = 0$$

$$\Rightarrow V_o = 14.608 - (565.5 * 10^3) I_B \quad (1.2.4)$$

Subtracting ?? from ??, we get,

$$I_B = 16.06\mu A \quad (1.2.5)$$

$$I_C = I_E = H I_B \quad (1.2.6)$$

$$Dc collector Current, I_C = 1.606mA \quad (1.2.7)$$

1.3. Find the small-signal equivalent circuit of the amplifier with the signal source represented by its Norton equivalent (as we usually do when the feedback connection at the input is shunt).

Solution: In fig ??

1.4. Find the G circuit and determine the value of G , R_i , and R_o .

Solution: G circuit in fig. ??

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

Parameter	Description
R_{in}	Total Input Resistance
R_{out}	Total Output Resistance
r_o	Output resistance of NPN
R_f	Feedback resistance
R_l	Input resistance of G circuit
R_o	Output resistance of G circuit
R_{if}	Input resistance of Feedback
R_{of}	Output resistance of Feedback
R_s	Resistance of Current Source
R_L	Output Load Resistance
g_m	Trans conductance
I_C	Collector current
I_E	Emitter Current
I_B	Base Current

TABLE 1.2

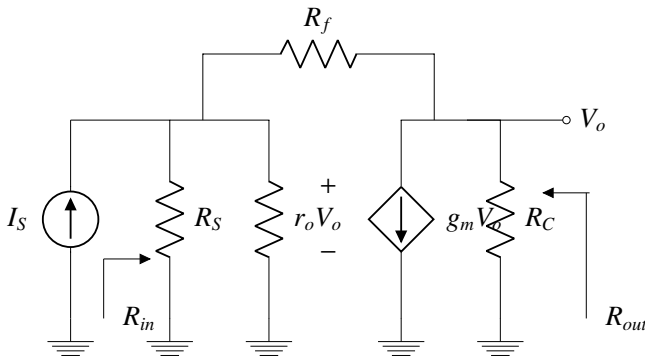


Fig. 1.3

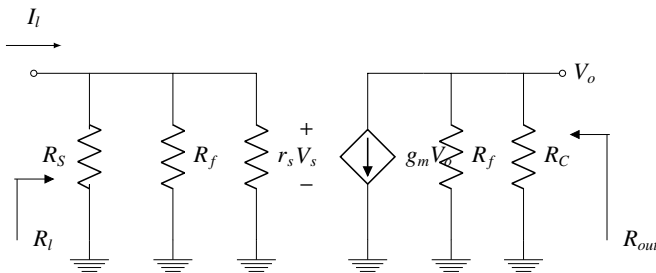


Fig. 1.4

$$g_m = \frac{I_C}{V_s} = \frac{1.606 \times 10^{-3}}{25 \times 10^{-3}} = 64 \text{ mA/V} \quad (1.4.1)$$

$$r_s = \frac{H}{g_m} = \frac{100}{64 \times 10^{-3}} = 1.56 \text{ k}\Omega \quad (1.4.2)$$

$$\text{Gain, } G = \frac{V_o}{I_l} \quad (1.4.3)$$

$$G = \frac{V_s}{I_l} \left(\frac{V_o}{V_s} \right) \quad (1.4.4)$$

$$V_o = -g_m V_s (R_f \parallel R_C) \quad (1.4.5)$$

$$V_s = I_l (R_s \parallel R_f \parallel r_s) \quad (1.4.6)$$

Substituting V_o V_s in ??,

$$G = -g_m (R_f \parallel R_C) (R_s \parallel R_f \parallel r_s) \quad (1.4.7)$$

$$G = -429 \text{ k}\Omega \quad (1.4.8)$$

Input Resistance

$$R_l = (R_s \parallel R_f \parallel r_s) = 1.31 \text{ k}\Omega \quad (1.4.9)$$

$$R_o = (R_f \parallel R_C) \quad (1.4.10)$$

$$\text{Output Resistance, } R_o = 5.09 \text{ k}\Omega \quad (1.4.11)$$

1.5. Find H and hence AH and 1+AH.

Solution:

$$H = \frac{I_f}{V_o} = -\frac{1}{R_f} \quad (1.5.1)$$

$$\Rightarrow H = -17.85 \times 10^{-4} \quad (1.5.2)$$

$$GH = 7.662 \quad (1.5.3)$$

$$1 + GH = 8.66 \quad (1.5.4)$$

1.6. Find T, R_{if} and R_{of} and hence R_{in} and R_{out} .

Solution:

$$T = \frac{G}{1 + GH} \quad (1.6.1)$$

$$= -49.54 \text{ k}\Omega \quad (1.6.2)$$

$$R_{if} = \frac{R_l}{1 + GH} \quad (1.6.3)$$

$$= \frac{1.31 \times 10^3}{8.66} \quad (1.6.4)$$

$$= 151.27 \Omega \quad (1.6.5)$$

$$R_{of} = \frac{R_o}{1 + GH} \quad (1.6.6)$$

$$= \frac{5.09 \times 10^3}{8.66} \quad (1.6.7)$$

$$= 587.7 \Omega \quad (1.6.8)$$

$$R_{in} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_s}} \quad (1.6.9)$$

$$= 153.2 \Omega \quad (1.6.10)$$

1.7. What voltage gain V_o/V_s is realized? How does this value compare to the ideal value obtained