

# Control Systems

G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Feedback Voltage Amplifier: Shunt-Series</b>	<b>1</b>
1.1	Introduction . . . . .	1

**Abstract**—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/codes>

## 1 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

### 1.1 Introduction

- 1.1.1. Draw the equivalent control system for the feedback current amplifier shown in 1.1.1.1

**Solution:** See Fig. 1.1.1.2.

- 1.1.2. For the feedback current amplifier shown in 1.1.1.1, draw the Small-Signal Model. Neglect the Early effect in  $Q_1$  and  $Q_2$ .

**Solution:** See Fig. 1.1.2.

While drawing a Small-Signal Model, we ground all constant voltage sources and open all constant current sources. All Small-Signal parameters are obtained from DC-Analysis of the circuit. Neglecting Early effect, in Small-Signal Analysis a N-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{gs}$  flowing from Drain to Source. Whereas a P-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{sg}$  flowing from Source to Drain.

- 1.1.3. Describe how the given circuit is a Negative Feedback Current Amplifier.

**Solution:** For the feedback to be negative,  $I_f$  must have the same polarity as  $I_s$ . To ascertain

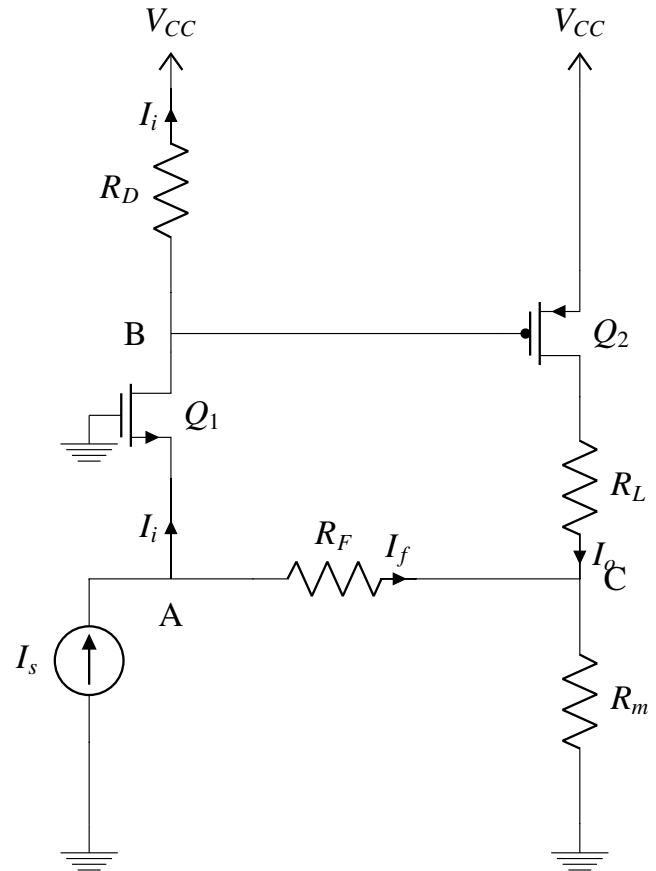


Fig. 1.1.1.1

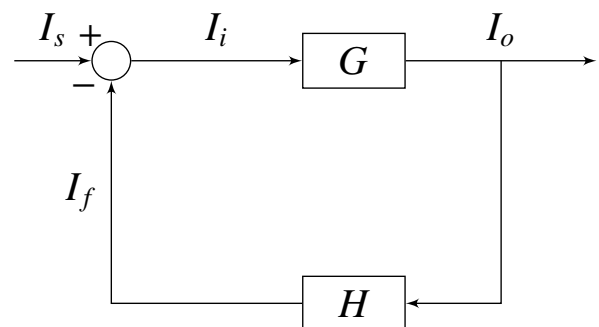


Fig. 1.1.1.2

that this is the case, we assume an increase in  $I_s$  and follow the change around the loop: An increase in  $I_s$  causes  $I_i$  to increase and the drain voltage of  $Q_1$  will increase. Since this

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

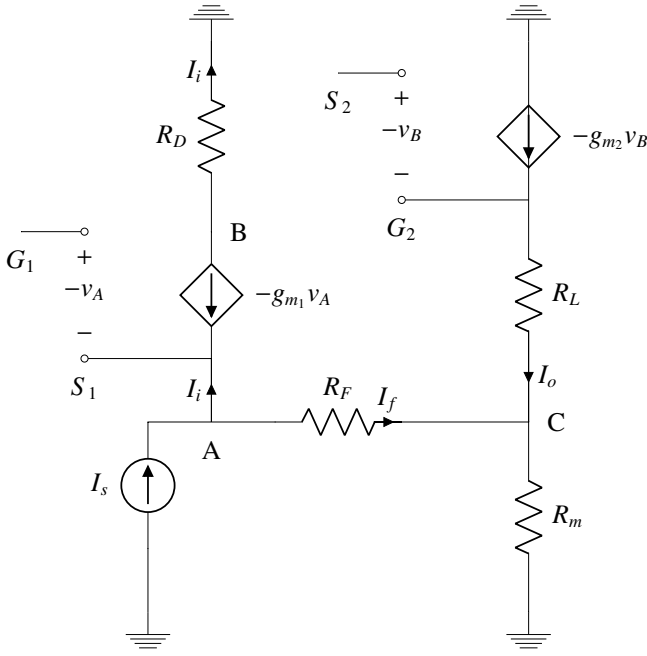


Fig. 1.1.2: Small Signal Model

voltage is applied to the gate of the p-channel device  $Q_2$ , its increase will cause  $I_o$ , the drain current of  $Q_2$ , to decrease. Thus, the voltage across  $R_M$  will decrease, which will cause  $I_f$  to increase. This is the same polarity assumed for the initial change in  $I_s$ , verifying that the feedback is indeed negative.

- 1.1.4. Find the Expression for the Open-Loop Gain  $G = \frac{I_o}{I_i}$ , from the Small-Signal Model. in Fig. 1.1.2.

**Solution:** In Small-Signal Model,

$$v_B = I_i R_D \quad (1.1.4.1)$$

$$v_{gs2} = v_B = I_i R_D \quad (1.1.4.2)$$

In Small-Signal Analysis, P-MOSFET is modelled as a current source where current flows from Source to Drain. So, the value of current flowing from Source to Drain in P-MOSFET is,

$$I_o = -g_{m2} v_{gs2} = -g_{m2} I_i R_D \quad (1.1.4.3)$$

So, the Open-Circuit Gain is

$$G = \frac{I_o}{I_i} = -g_{m2} R_D \quad (1.1.4.4)$$

- 1.1.5. Find the Expression of the Feedback Factor  $H = \frac{I_f}{I_o}$ , from Small-Signal Model.

**Solution:**  $I_o$  is fed to a current divider formed

by  $R_M$  and  $R_F$ .  $R_F$  is a Large Resistance compared to Input resistance of Amplifier and so most of the current flows through it leaving a small current as input to Amplifier. Hence the voltage at point 'A' is very small and is considered,  $v_A \approx 0$ . So  $R_F$  and  $R_M$  are parallel and Voltage Drop across them is same.

$$(I_o + I_f)R_M \approx -I_f R_F \quad (1.1.5.1)$$

$$\frac{I_f}{I_o} \approx -\frac{R_M}{R_F + R_M} \quad (1.1.5.2)$$

So, the Feedback Factor,

$$H \equiv \frac{I_f}{I_o} \approx -\frac{R_M}{R_F + R_M} \quad (1.1.5.3)$$

- 1.1.6. Find the Expression for the Closed-Loop Gain  $T = \frac{I_o}{I_s}$ .

**Solution:** From (1.1.4.4) and (1.1.5.3),

$$T = \frac{I_o}{I_s} = \frac{G}{1 + GH} \quad (1.1.6.1)$$

$$= -\frac{g_{m2} R_D}{1 + g_{m2} R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (1.1.6.2)$$

$$\Rightarrow T = -\frac{g_{m2} R_D}{1 + g_{m2} R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (1.1.6.3)$$