

# Control Systems

G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Feedback Voltage Amplifier: Series-Shunt</b>	<b>1</b>
1.1	Introduction . . . . .	1
<b>2</b>	<b>Feedback Current Amplifier: Shunt-Series</b>	<b>2</b>
2.1	Introduction . . . . .	2

*Abstract*—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/feedback/codes>

## 1 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

### 1.1 Introduction

1.1.1. Fig. 1.1.1.1 shows a non-inverting op-amp configuration with parameters described in Table 1.1.1. Draw the equivalent control system.

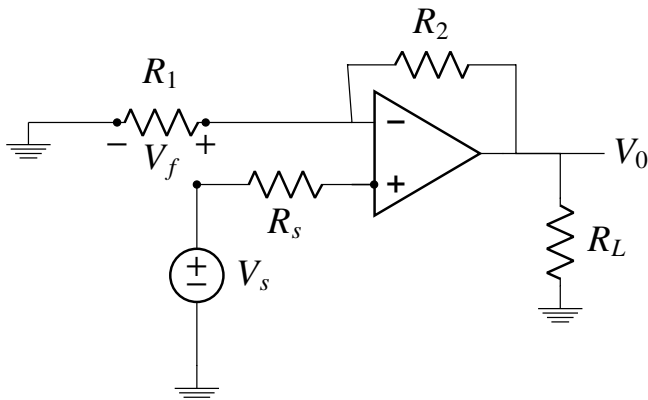


Fig. 1.1.1.1

**Solution:** See Fig. 1.1.1.2

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

Parameter	Value
input resistance	$\infty$
output resistance	<b>0</b>
Input voltage	$V_s$
Output Voltage	$V_o$
Feeding resistance	$R_1$
Feedback resistance	$R_2$
Source resistance	$R_s$
load resistance	$R_L$

TABLE 1.1.1

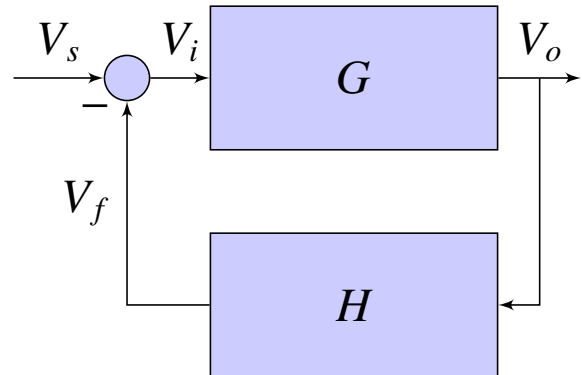


Fig. 1.1.1.2

1.1.2. Draw the small signal model for Fig. 1.1.1.1.  
**Solution:** The equivalent circuit of the amplifier is in Fig. 1.1.2

1.1.3. Assuming that the operational amplifier has infinite input resistance and zero output resistance, find the *feedback factor*  $H$ .

**Solution:** From Fig. 1.1.2,

$$V_o = G V_i \quad (1.1.3.1)$$

$$V_i = V_s - V_f \quad (1.1.3.2)$$

$$V_f = \frac{R_1}{R_1 + R_2} V_o \quad (1.1.3.3)$$

assuming that the current through  $R_s$  is very

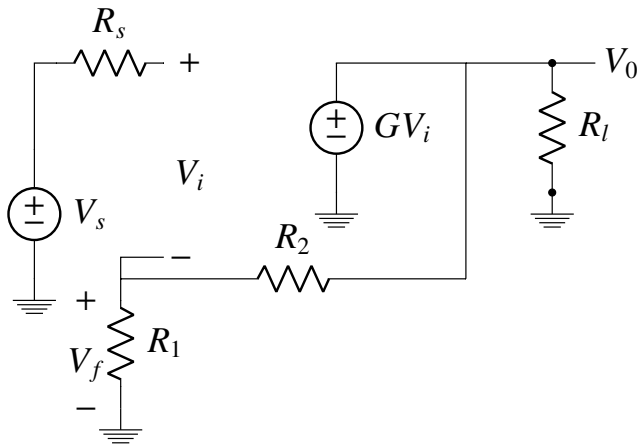


Fig. 1.1.2

small. Thus,

$$H = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \quad (1.1.3.4)$$

1.1.4. Obtain the closed loop gain  $T$  and summarize your results through a Table.

**Solution:** Table 1.1.4 provides a summary.

$$T = \frac{V_o}{V_i} = \frac{G}{1 + GH} \quad (1.1.4.1)$$

$$= \frac{G(R_1 + R_2)}{(R_1 + R_2) + GR_1} \quad (1.1.4.2)$$

Parameters	Definition	For given circuit
Open loop gain	$G$	$G$
Feedback factor	$H$	$\frac{R_1}{R_1 + R_2}$
Loop gain	$GH$	$G \frac{R_1}{R_1 + R_2}$
Amount of feedback	$1 + GH$	$1 + \frac{GR_1}{R_1 + R_2}$
Closed loop gain	$\frac{G}{1 + GH}$	$\frac{G(R_1 + R_2)}{R_1 + R_2 + GR_1}$

TABLE 1.1.4

1.1.5. Find the condition under which closed loop gain  $T$  is almost entirely determined by the feedback network.

**Solution:** If

$$GH \gg 1, \quad (1.1.5.1)$$

$$T \approx \frac{1}{H} = 1 + \frac{R_2}{R_1} \quad (1.1.5.2)$$

1.1.6. If

$$G = 10^4 \quad (1.1.6.1)$$

$$T = 10, \quad (1.1.6.2)$$

find  $H$ .

**Solution:** From Table 1.1.4

$$T = \frac{G}{1 + GH} = 10 \quad (1.1.6.3)$$

$$\Rightarrow H = 0.0999 \quad (1.1.6.4)$$

1.1.7. *Gain Desensitivity:* If  $G$  decreases by 20%, what is the corresponding decrease in  $T$ ? Comment.

**Solution:** From Table 1.1.4, Given

$$T = \frac{G}{1 + GH} \quad (1.1.7.1)$$

$$\Rightarrow dT = \frac{dG}{(1 + GH)^2} \quad (1.1.7.2)$$

$$\Rightarrow \frac{dT}{T} = \frac{1}{1 + GH} \frac{dG}{G} \quad (1.1.7.3)$$

From the information available so far,

$$dG = 20\%, G = 10^4, H = 0.0999 \Rightarrow \frac{dT}{T} = 0.025\% \quad (1.1.7.4)$$

using the following code.

```
codes/ee18btech11005/ee18btech11005.py
```

Thus the closed loop gain is almost invariant to a relatively large (20%) variation in the open loop gain  $G$ . This is known as gain desensitivity.

## 2 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

### 2.1 Introduction

2.1.1. Draw the equivalent control system for the feedback current amplifier shown in 2.1.1.4

**Solution:** See Fig. 2.1.1.5.

2.1.2. For the feedback current amplifier shown in 2.1.1.4, draw the Small-Signal Model. Neglect the Early effect in  $Q_1$  and  $Q_2$ .

**Solution:** See Fig. 2.1.2.

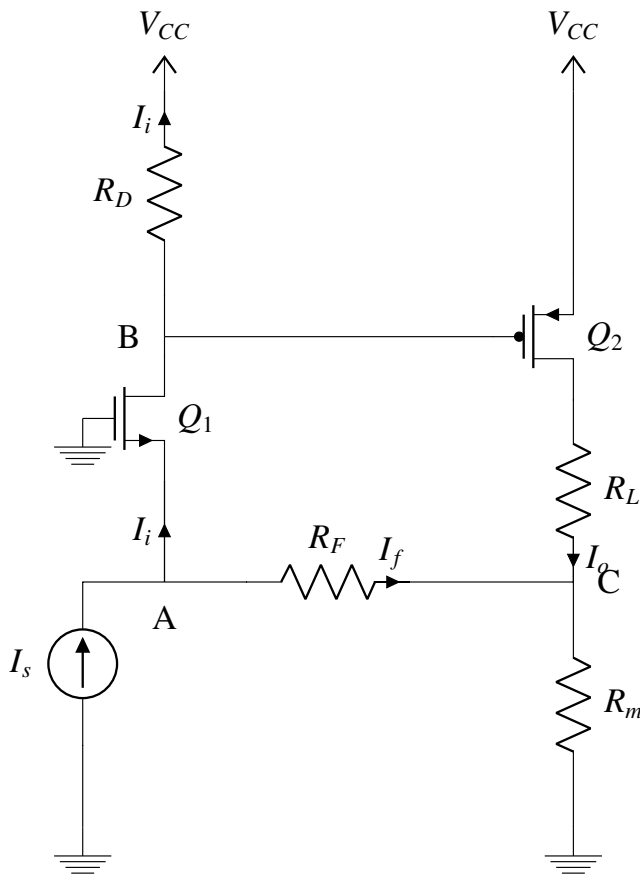


Fig. 2.1.1.4

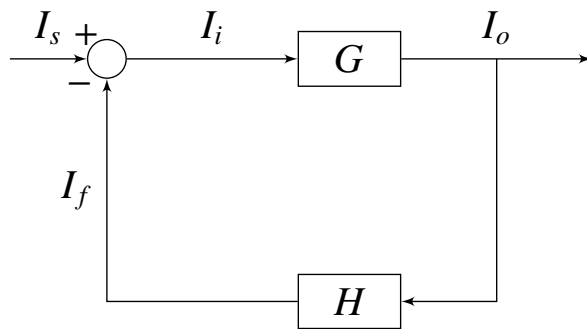


Fig. 2.1.1.5

While drawing a Small-Signal Model, we ground all constant voltage sources and open all constant current sources. All Small-Signal parameters are obtained from DC-Analysis of the circuit. Neglecting Early effect, in Small-Signal Analysis a N-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{gs}$  flowing from Drain to Source. Whereas a P-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{sg}$  flowing from Source to Drain.

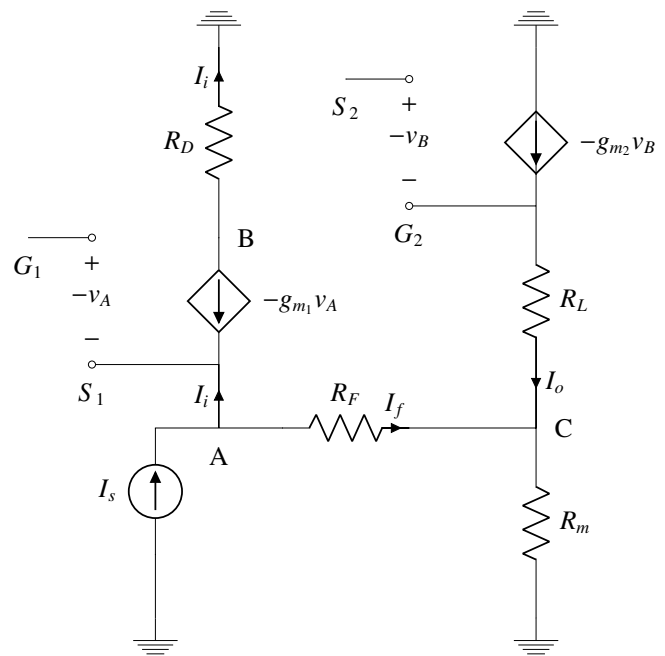


Fig. 2.1.2: Small Signal Model

2.1.3. Describe how the given circuit is a Negative Feedback Current Amplifier.

**Solution:** For the feedback to be negative,  $I_f$  must have the same polarity as  $I_s$ . To ascertain that this is the case, we assume an increase in  $I_s$  and follow the change around the loop: An increase in  $I_s$  causes  $I_i$  to increase and the drain voltage of  $Q_1$  will increase. Since this voltage is applied to the gate of the p-channel device  $Q_2$ , its increase will cause  $I_o$ , the drain current of  $Q_2$ , to decrease. Thus, the voltage across  $R_M$  will decrease, which will cause  $I_f$  to increase. This is the same polarity assumed for the initial change in  $I_s$ , verifying that the feedback is indeed negative.

2.1.4. Find the Expression for the Open-Loop Gain  $G = \frac{I_o}{I_i}$ , from the Small-Signal Model. in Fig. 2.1.2.

**Solution:** In Small-Signal Model,

$$v_B = I_i R_D \quad (2.1.4.1)$$

$$v_{gs2} = v_B = I_i R_D \quad (2.1.4.2)$$

In Small-Signal Analysis, P-MOSFET is modelled as a current source where current flows from Source to Drain. So, the value of current flowing from Source to Drain in P-MOSFET

is,

$$I_o = -g_{m2}v_{gs2} = -g_{m2}I_i R_D \quad (2.1.4.3)$$

So, the Open-Circuit Gain is

$$G = \frac{I_o}{I_i} = -g_{m2}R_D \quad (2.1.4.4)$$

2.1.5. Find the Expression of the Feedback Factor  $H = \frac{I_f}{I_o}$ , from Small-Signal Model.

**Solution:**  $I_o$  is fed to a current divider formed by  $R_M$  and  $R_F$ .  $R_F$  is a Large Resistance compared to Input resistance of Amplifier and so most of the current flows through it leaving a small current as input to Amplifier. Hence the voltage at point 'A' is very small and is considered,  $v_A \simeq 0$ . So  $R_F$  and  $R_M$  are parallel and Voltage Drop across them is same.

$$(I_o + I_f)R_M \simeq -I_f R_F \quad (2.1.5.1)$$

$$\frac{I_f}{I_o} \simeq -\frac{R_M}{R_F + R_M} \quad (2.1.5.2)$$

So, the Feedback Factor,

$$H \equiv \frac{I_f}{I_o} \simeq -\frac{R_M}{R_F + R_M} \quad (2.1.5.3)$$

2.1.6. Find the Expression for the Closed-Loop Gain  $T = \frac{I_o}{I_s}$ .

**Solution:** From (2.1.4.4) and (2.1.5.3),

$$T = \frac{I_o}{I_s} = \frac{G}{1 + GH} \quad (2.1.6.1)$$

$$= -\frac{g_{m2}R_D}{1 + g_{m2}R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.2)$$

$$\Rightarrow T = -\frac{g_{m2}R_D}{1 + g_{m2}R_D / \left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.3)$$