

# Control Systems

G V V Sharma\*

## CONTENTS

**Abstract**—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/feedback/codes>

Parameter	Value
input resistance	$\infty$
output resistance	<b>0</b>
Input voltage	$V_s$
Output Voltage	$V_o$
Feeding resistance	$R_1$
Feedback resistance	$R_2$
Source resistance	$R_s$
load resistance	$R_L$

TABLE 1.1

## 1 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

1.1. Fig. 1.1.1 shows a non-inverting op-amp configuration with parameters described in Table 1.1. Draw the equivalent control system.

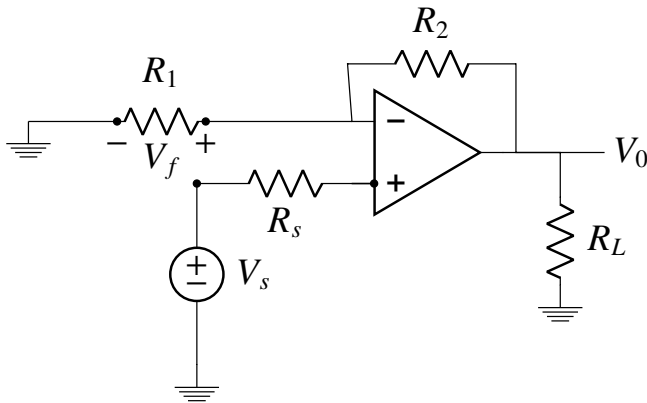


Fig. 1.1.1

**Solution:** See Fig. 1.1.2

1.2. Draw the small signal model for Fig. 1.1.1.

**Solution:** The equivalent circuit of the amplifier is in Fig. 1.2

1.3. Assuming that the operational amplifier has infinite input resistance and zero output resistance, find the *feedback factor H*.

**Solution:** From Fig. 1.2,

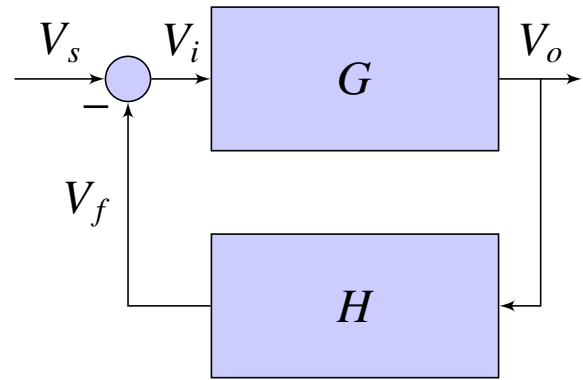


Fig. 1.1.2

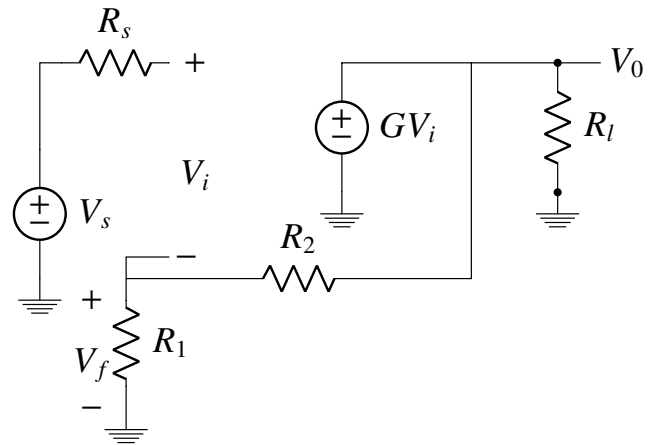


Fig. 1.2

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

$$V_o = GV_i \quad (1.3.1)$$

$$V_i = V_s - V_f \quad (1.3.2)$$

$$V_f = \frac{R_1}{R_1 + R_2} V_o \quad (1.3.3)$$

assuming that the current through  $R_s$  is very small. Thus,

$$H = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \quad (1.3.4)$$

1.4. Obtain the closed loop gain  $T$  and summarize your results through a Table.

**Solution:** Table 1.4 provides a summary.

$$T = \frac{V_o}{V_i} = \frac{G}{1 + GH} \quad (1.4.1)$$

$$= \frac{G(R_1 + R_2)}{(R_1 + R_2) + GR_1} \quad (1.4.2)$$

Parameters	Definition	For given circuit
Open loop gain	G	G
Feedback factor	H	$\frac{R_1}{R_1 + R_2}$
Loop gain	GH	$G \frac{R_1}{R_1 + R_2}$
Amount of feedback	$1 + GH$	$1 + \frac{GR_1}{R_1 + R_2}$
Closed loop gain	$\frac{G}{1 + GH}$	$\frac{G(R_1 + R_2)}{R_1 + R_2 + GR_1}$

TABLE 1.4

1.5. Find the condition under which closed loop gain  $T$  is almost entirely determined by the feedback network.

**Solution:** If

$$GH \gg 1, \quad (1.5.1)$$

$$T \approx \frac{1}{H} = 1 + \frac{R_2}{R_1} \quad (1.5.2)$$

1.6. If

$$G = 10^4 \quad (1.6.1)$$

$$T = 10, \quad (1.6.2)$$

find  $H$ .

**Solution:** From Table 1.4

$$T = \frac{G}{1 + GH} = 10 \quad (1.6.3)$$

$$\Rightarrow H = 0.0999 \quad (1.6.4)$$

1.7. *Gain Desensitivity:* If  $G$  decreases by 20%, what is the corresponding decrease in  $T$ ? Comment.

**Solution:** From Table 1.4, Given

$$T = \frac{G}{1 + GH} \quad (1.7.1)$$

$$\Rightarrow dT = \frac{dG}{(1 + GH)^2} \quad (1.7.2)$$

$$\Rightarrow \frac{dT}{T} = \frac{1}{1 + GH} \frac{dG}{G} \quad (1.7.3)$$

From the information available so far,

$$dG = 20\%, G = 10^4, H = 0.0999 \Rightarrow \frac{dT}{T} = 0.025\% \quad (1.7.4)$$

using the following code.

codes/ee18btech11005/ee18btech11005.py

Thus the closed loop gain is almost invariant to a relatively large (20%) variation in the open loop gain  $G$ . This is known as gain desensitivity.

## 2 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

### 2.1 Ideal Case

2.1.1. Draw the equivalent control system for the feedback current amplifier shown in 2.1.1.1

**Solution:** See Fig. 2.1.1.2.

2.1.2. For the feedback current amplifier shown in 2.1.1.1, draw the Small-Signal Model. Neglect the Early effect in  $Q_1$  and  $Q_2$ .

**Solution:** See Fig. 2.1.2.

While drawing a Small-Signal Model, we ground all constant voltage sources and open all constant current sources. All Small-Signal parameters are obtained from DC-Analysis of the circuit. Neglecting Early effect, in Small-Signal Analysis a N-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{gs}$  flowing from Drain to Source. Whereas a P-MOSFET is modelled as a Current Source with value of current equal to  $g_m v_{sg}$  flowing from Source to Drain.

2.1.3. Write all the node/loop equations using KCL/KVL.

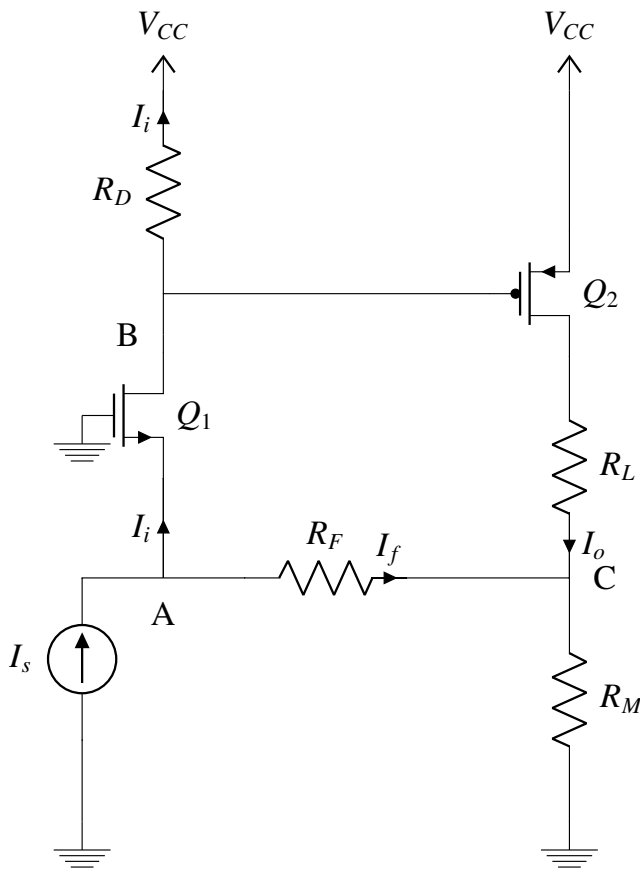


Fig. 2.1.1.1

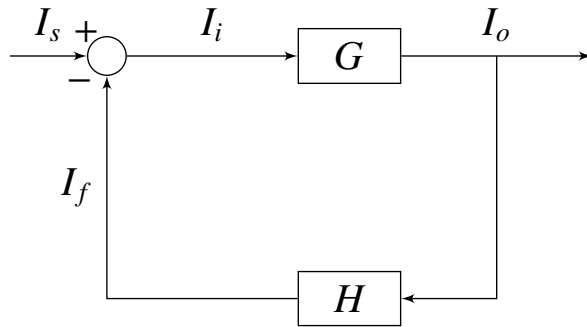


Fig. 2.1.1.2

**Solution:** From Figs. 2.1.1.1 and 2.1.2,

$$I_i = \frac{v_B}{R_D} \quad (2.1.3.1)$$

$$I_o = -g_{m2}v_B \quad (2.1.3.2)$$

$$v_C - v_A = -I_f R_F \quad (2.1.3.3)$$

$$v_C = (I_o + I_f)R_M \quad (2.1.3.4)$$

$$I_i = g_{m1}v_A \quad (2.1.3.5)$$

2.1.4. Find the Expression for the Open-Loop Gain  $G$ .

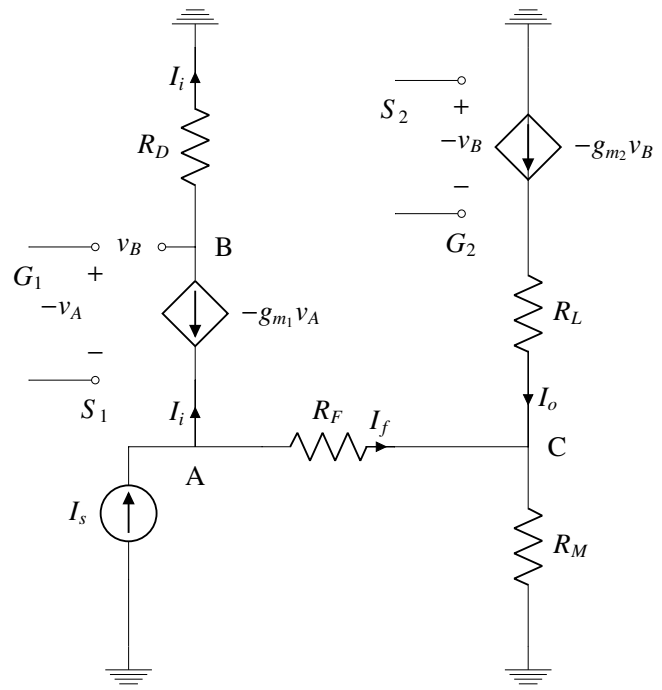


Fig. 2.1.2: Small Signal Model

**Solution:** From (2.1.3.1) and (2.1.3.2),

$$G = \frac{I_o}{I_i} = -g_{m2}R_D \quad (2.1.4.1)$$

2.1.5. Find the Expression of the Feedback Factor  $H$ .

**Solution:**

$$H = \frac{I_f}{I_o}, \quad (2.1.5.1)$$

From (2.1.3.3) and (2.1.3.4),

$$(I_o + I_f)R_M - v_A = -I_f R_F \quad (2.1.5.2)$$

$$\Rightarrow (I_o + I_f)R_M + \frac{I_i}{g_{m1}} = -I_f R_F \quad (2.1.5.3)$$

from (2.1.3.5). Dividing by  $I_o$ ,

$$\Rightarrow (1 + H)R_M + \frac{1}{g_{m1}G} = -H R_F \quad (2.1.5.4)$$

upon substituting from and . Simplifying further, we obtain

$$\Rightarrow H = \frac{\frac{1}{g_{m1}g_{m2}R_D} - R_M}{R_F + R_M} \quad (2.1.5.5)$$

$$\approx -\frac{R_M}{R_F + R_M} \quad (2.1.5.6)$$

for  $R_M \gg \frac{1}{g_{m1}g_{m2}R_D}$ .

2.1.6. Find the Expression for the Closed-Loop Gain

$$T = \frac{I_o}{I_s}$$

**Solution:** From (2.1.5) and (2.1.5.6),

$$T = \frac{I_o}{I_s} = \frac{G}{1 + GH} \quad (2.1.6.1)$$

$$= -\frac{g_{m2}R_D}{1 + g_{m2}R_D \left(1 + \frac{R_F}{R_M}\right)} \quad (2.1.6.2)$$

While calculating  $R_{22}$ , Port-1 should be shorted. Hence,

$$R_{22} = R_F \parallel R_M \quad (2.2.3.2)$$

$$= \frac{R_F R_M}{R_F + R_M} \quad (2.2.3.3)$$

2.2.4. Draw the block diagram and circuit diagram for calculating  $G$ .

**Solution:** See Figs. 2.2.4.1 and 2.2.4.2

## 2.2 Practical Case

2.2.1. Draw the Block Diagram and Circuit Diagram for  $H$ .

**Solution:** The Block Diagram is available in Fig. 2.2.1.1

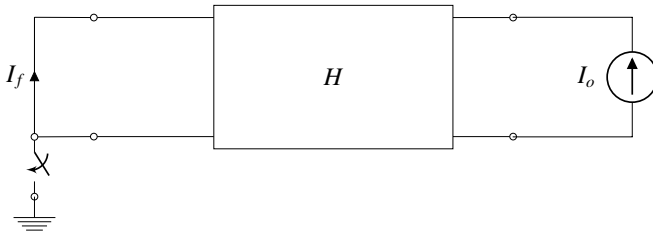


Fig. 2.2.1.1: Feedback Block Diagram

and the corresponding circuit diagram in Fig. 2.2.1.2

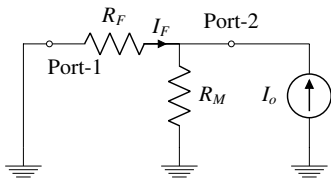


Fig. 2.2.1.2: Feedback Network

2.2.2. Find  $H$  from Fig. 2.2.1.2.

**Solution:** Using current division,

$$\frac{I_f}{I_o} = -\frac{R_M}{R_F + R_M} \quad (2.2.2.1)$$

$$\Rightarrow H = -\frac{R_M}{R_F + R_M} \quad (2.2.2.2)$$

2.2.3. Find  $R_{11}$  and  $R_{22}$  of Feedback Network where  $R_{11}$  is input resistance through Port-1 and  $R_{22}$  is Input Resistance through Port-2.

**Solution:**  $R_{11}$  is calculated by opening the current source at Port-2. Hence,

$$R_{11} = R_F + R_M \quad (2.2.3.1)$$

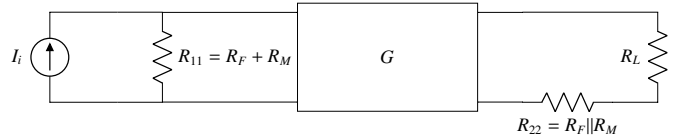


Fig. 2.2.4.1: Open-Loop Block Diagram

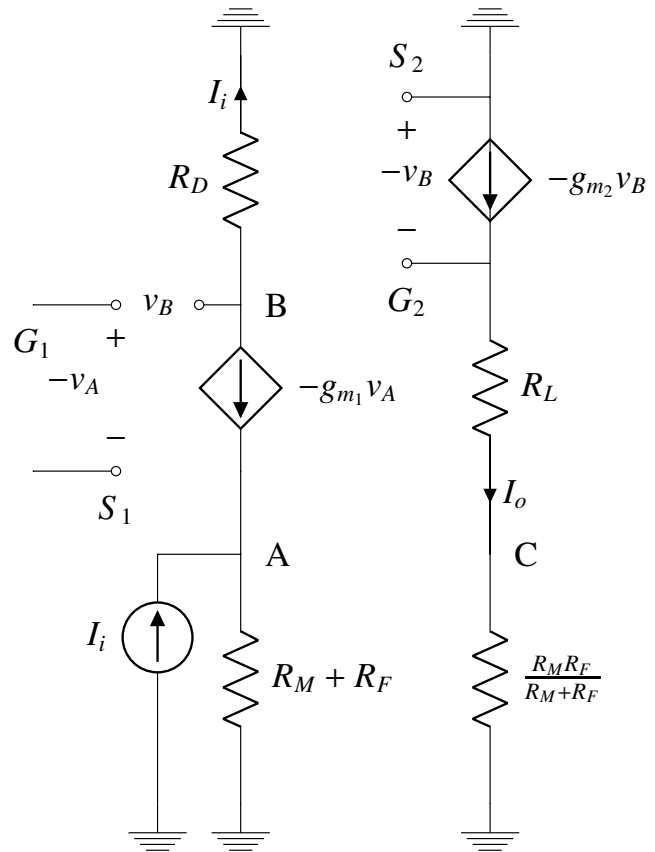


Fig. 2.2.4.2: Open-Loop Network

2.2.5. Find  $G$ .

**Solution:** The analysis is the same as Problem 2.1.4.

## 3 FEEDBACK CURRENT AMPLIFIER: EXAMPLE

3.1. Consider a Feedback Current Amplifier formed by cascading an Inverting Opamp  $\mu$  with a

MOSFET (NMOS) as shown in Fig. 3.1.1. The output current is the Drain Current of the NMOS. Assume that Opamp has an input resistance  $R_{id}$ , an Open Circuit Voltage Gain  $\mu$ , and an output resistance  $r_{o1}$ . Express this as a control system.

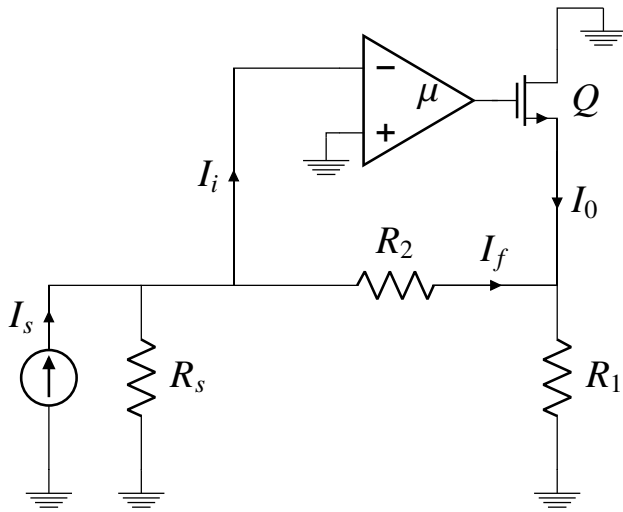


Fig. 3.1.1: Complete Circuit

**Solution:** See Fig. 3.1.2

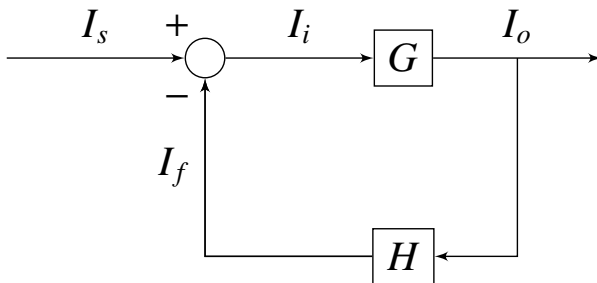


Fig. 3.1.2: Block Diagram

3.2. Represent Fig. 3.1.1 using a Small Signal Equivalent Model.

**Solution:** See Fig. 3.2

3.3. Find  $G$ .

**Solution:** From Fig. 3.2 we have the following

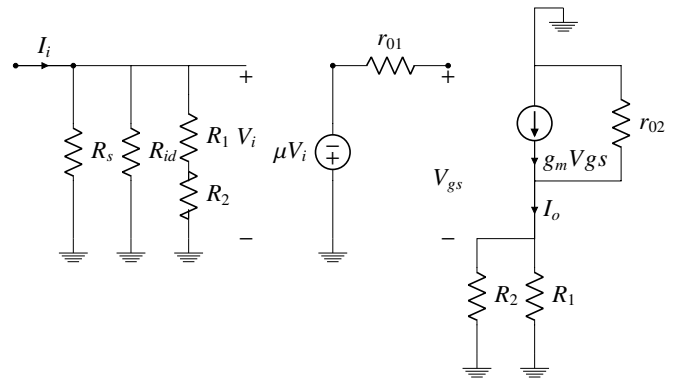


Fig. 3.2: Small Signal Model

equations

$$V_g = -\mu V_i \quad (3.3.1)$$

$$\frac{V_i}{R_{id}} = I_i \quad (3.3.2)$$

$$I_s = \frac{V_i}{R_s} + I_f + I_i \quad (3.3.3)$$

$$I_f = \frac{V_i - V_s}{R_2} \quad (3.3.4)$$

$$\frac{V_g}{R_2} = I_f + I_o \quad (3.3.5)$$

$$I_o = g_m (V_g - V_s) + \frac{V_s}{r_{o2}} \quad (3.3.6)$$

$$G = \frac{I_o}{I_i} \quad (3.3.7)$$

$$H = \frac{I_f}{I_o} \quad (3.3.8)$$

$$R_i = R_s \parallel R_{id} \parallel (R_1 + R_2) \quad (3.3.9)$$

where  $R_i$  is the resistance seen by the current source  $I_s$  and  $R_{id}$  is the internal resistance of the OPAMP.

$$V_i = I_s R_i \quad (3.3.10)$$

$$I_i = I_s \frac{R_s \parallel (R_1 + R_2)}{R_s + R_{id} + R_1 + R_2} \quad (3.3.11)$$

for small values of  $I_f$ .

$$I_o = -\mu V_i \frac{1}{1/g_m + (R_1 \parallel R_2 \parallel r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 \parallel R_2)} \quad (3.3.12)$$

$$G = \frac{I_o}{I_i} = -\mu \frac{R_i}{1/g_m + (R_1 || R_2 || r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 || R_2)} \quad \Rightarrow R_{if} = R_i || \frac{R_2}{\mu} \quad (3.6.5)$$

We use the approximation

$$1/g_m \ll (R_1 || R_2 || r_{o2}) \quad (3.3.14)$$

This is because the  $\frac{1}{g_m}$  is in order of few  $\Omega$ s but,  $R_1$ ,  $R_2$  and  $r_{o2}$  are in order of k $\Omega$ s

$$G = -\mu \frac{R_i}{R_1 || R_2} \quad (3.3.15)$$

$$R_o = r_{o2} + (R_1 || R_2) + (g_m r_{o2})(R_1 || R_2) \quad (3.3.16)$$

$$\Rightarrow R_o \simeq g_m r_{o2} (R_1 || R_2) \quad (3.3.17)$$

### 3.4. Find expression for Loop Gain H

**Solution:**

$$H = \frac{I_f}{I_o} = -\frac{R_1}{R_1 + R_2} \quad (3.4.1)$$

### 3.5. If loop gain is large, find approximate expression for closed loop gain T

**Solution:** Given,

$$GH \gg 1 \quad (3.5.1)$$

$$T = \frac{G}{1 + GH} \simeq \frac{1}{H} \quad (3.5.2)$$

$$T \simeq \frac{1}{H} = -\left(1 + \frac{R_2}{R_1}\right) \quad (3.5.3)$$

### 3.6. Give expressions for GH, T, $R_{if}$ , $R_{in}$ , $R_{of}$ , $R_{out}$

**Solution:**

$$GH = \mu \frac{R_i}{\frac{1}{g_m} + (R_1 || R_2 || r_{o2})} \frac{r_{o2}}{r_{o2} + (R_1 || R_2)} \frac{R_1}{R_1 + R_2} \quad (3.6.1)$$

Once again, using the approximation,

$$\Rightarrow GH \simeq \mu \frac{R_i}{R_1 || R_2} \frac{R_1}{R_1 + R_2} = \mu \frac{R_i}{R_2} \quad (3.6.2)$$

For Input Resistance,

$$R_{if} = R_i / (1 + GH) \quad (3.6.3)$$

$$\Rightarrow \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{\mu}{R_2} \quad (3.6.4)$$

Substituting the value of  $R_i$ ,

$$R_{if} = R_s || R_{id} || (R_1 + R_2) || \frac{R_2}{\mu} \quad (3.6.6)$$

$$R_{if} = R_s || R_{in} \quad (3.6.7)$$

$$\Rightarrow R_{in} = R_{id} || (R_1 + R_2) || \frac{R_2}{\mu} \quad (3.6.8)$$

$$R_{in} \simeq \frac{R_2}{\mu} \quad (3.6.9)$$

For Output Resistance,

$$R_{of} = R_o (1 + GH) \simeq GHR_o \quad (3.6.10)$$

$$R_{of} \simeq \mu \left(\frac{R_i}{R_2}\right) (g_m r_{o2}) (R_1 || R_2) \quad (3.6.11)$$

$$R_{out} = R_{of} = \mu \frac{R_i}{R_1 + R_2} (g_m r_{o2}) R_1 \quad (3.6.12)$$

### 3.7. Given the following values

Parameter	Value
$\mu$	1000
$R_s$	$\infty$
$R_{id}$	$\infty$
$r_{o1}$	1k $\Omega$
$R_1$	10k $\Omega$
$R_2$	90k $\Omega$
$g_m$	5mA/V
$r_{o2}$	20k $\Omega$

TABLE 3.7

Find numerical value of  $R_i$  and use it to find the value of G

**Solution:** Using the given numerical values on the previously obtained equations, we obtain:

$$R_i = \infty || \infty || (10 + 90) = 100k\Omega \quad (3.7.1)$$

$$G = -1000 \frac{100}{10 || 90} = -11.11 \times 10^3 \quad (3.7.2)$$

- 3.8. Check the validity of the approximation that we use to neglect  $1/g_m$

**Solution:**

$$1/g_m = 0.2k\Omega \ll (10||90||20)k\Omega = 6.2k\Omega \quad (3.8.1)$$

Hence, we can see that our approximation is valid

- 3.9. Find the value of feedback gain  $H$  and open loop gain  $GH$

**Solution:**

$$H = -\frac{R_1}{R_1 + R_2} = -\frac{10}{10 + 90} = -0.1 \quad (3.9.1)$$

$$GH = 1111 \gg 1 \quad (3.9.2)$$

- 3.10. Find the approximate value of closed loop gain  $T$

**Solution:**

$$T \simeq \frac{1}{H} = -\frac{1}{0.1} = -10 \quad (3.10.1)$$

- 3.11. Find the values of  $R_{in}$  and  $R_{out}$

**Solution:**

$$R_{in} = \frac{R_2}{\mu} = \frac{90k\Omega}{1000} = 90\Omega \quad (3.11.1)$$

$$R_o = g_m r_{o2}(R_1||R_2) = 5 \times 20(10||90) = 900k\Omega \quad (3.11.2)$$

$$R_{out} = (1 + GH)R_o = 1112 \times 900 \simeq 1000M\Omega \quad (3.11.3)$$

Parameter	Value
$R_i$	$100k\Omega$
$1/g_m$	$200\Omega$
$G$	$-1.11 \times 10^4$
$H$	$-0.1$
$GH$	$1111$
$T$	$-10$
$R_{in}$	$90\Omega$
$R_o$	$900k\Omega$
$R_{out}$	$1000M\Omega$

TABLE 3.11

- 3.12. Verify the above calculations using a Python code.

**Solution:**

codes/ee18btech11021/ee18btech11021\_calc.py

#### 4 FEEDBACK TRANSCONDUCTANCE AMPLIFIER: SERIES-SERIES

- 4.1. Part of the circuit of the MC1553 Amplifier is shown in circuit1 in Fig. 4.1.1 with values of various parameters given in Table 4.1. Draw the equivalent block diagram.

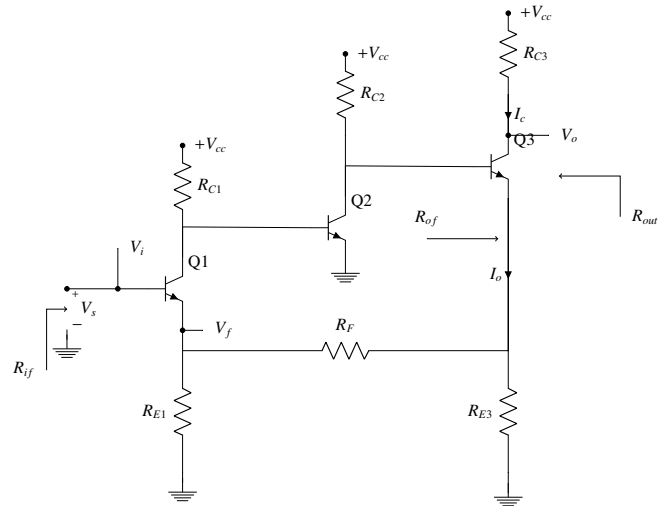


Fig. 4.1.1

**Solution:** The block diagram is available in Fig. 4.1.2

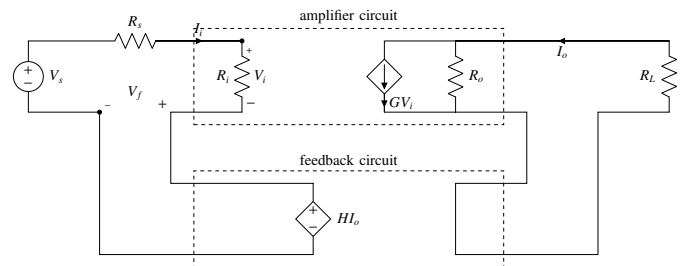


Fig. 4.1.2: Feedback Transconductance Amplifier

- 4.2. Draw the block diagram and equivalent circuit for  $H$  for Fig. 4.1.2.

**Solution:** Fig. 4.2.1 gives the required block diagram

$$H = \frac{V_f}{I_o} \Big|_{I_1=0} \quad (4.2.1)$$

and the equivalent  $H$  circuit is available in Fig. 4.2.2.

Parameter	Value
$R_{C1}$	$9k\Omega$
$R_{E1}$	$100\Omega$
$R_{C2}$	$5k\Omega$
$R_F$	$640\Omega$
$R_{E2}$	$100\Omega$
$R_{C3}$	$600\Omega$
$h_{fe}$	<b>100</b>
$r_o$	$\infty\Omega$
$I_{C1}$	<b>0.6mA</b>
$I_{C2}$	<b>1mA</b>
$I_{C3}$	<b>4mA</b>
$r_{e1}$	$41.7\Omega$
$r_{\pi2}$	$2.5k\Omega$
$\alpha_1$	<b>0.99</b>
$g_{m2}$	<b>40mA/V</b>
$r_{e3}$	$6.25\Omega$
$r_{o3}$	$25k\Omega$
$r_{\pi3}$	$625\Omega$

TABLE 4.1: parameters

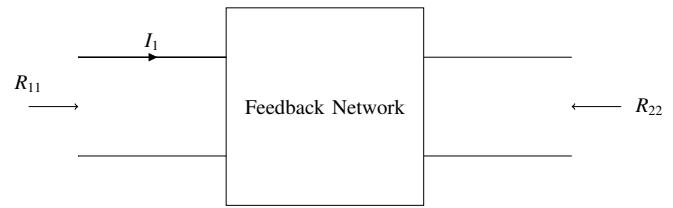


Fig. 4.4: feedback network

**Solution:**

$$R_{11} = R_{E1} \parallel (R_F + R_{E2}) \quad (4.4.1)$$

$$R_{22} = R_{E2} \parallel (R_F + R_{E1}) \quad (4.4.2)$$

4.5. Draw the block diagram and equivalent circuit for  $G$ .

**Solution:** The required block diagram is available in Fig. 4.5 and the equivalent circuit in

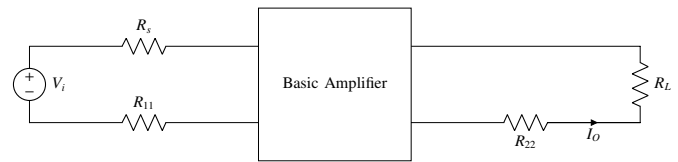


Fig. 4.5: Amplifier circuit block diagram

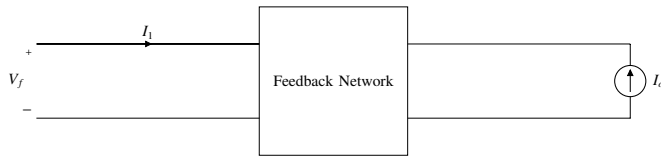


Fig. 4.2.1: Feedback circuit block diagram

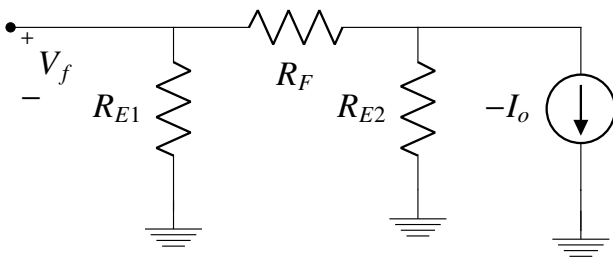


Fig. 4.2.2: H circuit

4.3. Find the feedback Factor  $H$

**Solution:** From Fig. 4.2.2,

$$H = \frac{V_f}{I_o} = \frac{R_{E1}R_{E2}}{R_{E2} + R_F + R_{E1}} \quad (4.3.1)$$

4.4. Find  $R_{11}$  and  $R_{22}$  from Figs. 4.4 and 4.2.2

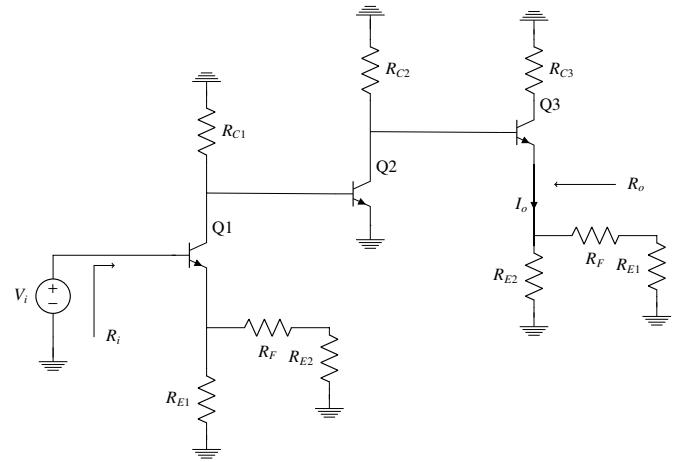


Fig. 4.5: G circuit

4.6. feedback analysis to find open loop gain  $G$

**Solution:** employing equivalent amplifier block diagram fig.4.5 into circuit in fig.4.1.1,  $R_{11}$  and  $R_{22}$  are found from feedback circuit in fig.4.2.2 using rule from fig.4.4 we finally obtain

$$R_s, R_L = 0 \quad (4.6.1)$$



$$R_{11} = R_{E1} \parallel (R_F + R_{E2}) \quad (4.6.2)$$

$$R_{22} = R_{E2} \parallel (R_F + R_{E1}) \quad (4.6.3)$$

finally Amplifier circuit is obtained shown in fig.4.5 to find  $G = \frac{I_0}{V_i}$  we determine the gain of

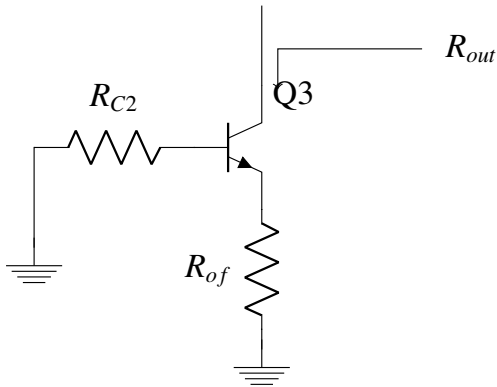


Fig. 4.6: circuit4

first stage, this is written by inspection as-

$$\frac{V_{c1}}{V_i} = \frac{-\alpha(R_{c1} \parallel r_{\pi 2})}{r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))} \quad (4.6.4)$$

using values from 4.1

$$\frac{V_{c1}}{V_i} = -14.92V/V \quad (4.6.5)$$

Next, we determine the gain of the second stage, which can be written by inspection (noting that  $V_{b2} = V_{c1}$ ) as

$$\frac{V_{c2}}{V_{c1}} = -g_{m2} R_{c2} \parallel (h_{fe} + 1) [r_{e3} + (R_{E2} \parallel (R_F + R_{E1}))] \quad (4.6.6)$$

substituting, results in

$$\frac{V_{c2}}{V_{c1}} = -131.2V/V \quad (4.6.7)$$

Finally, for the third stage we can write by inspection

$$\frac{I_0}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} \parallel (R_F + R_{E1}))} \quad (4.6.8)$$

substituting values from 4.1 gives

$$\frac{I_0}{V_{c2}} = 10.6mA/V \quad (4.6.9)$$

combining the gains of the three stages results

in

$$G = \frac{I_0}{V_i} = -14.92 \times -131.2 \times 10.6 \times 10^{-3} = 20.7A/V \quad (4.6.10)$$

4.7. Find closed loop gain T and Voltage Gain  $V_0/V_s$

**Solution:**

$$T = \frac{I_0}{V_s} = \frac{G}{1 + GH} = \frac{20.7}{1 + 20.7 \times 11.9} = 83.7mA/V \quad (4.7.1)$$

the voltage gain is found from

$$\frac{V_0}{V_s} = \frac{-I_c R_{c3}}{V_s} \approx \frac{-I_0 R_{c3}}{V_s} = -T R_{c3} \quad (4.7.2)$$

$$= -83.7 \times 10^{-3} \times 600 = -50.2V/V \quad (4.7.3)$$

4.8. Now assume Loop gain is large and find approximate expression for closed loop gain  $T = \frac{I_0}{V_s}$

**Solution:** When  $GH \gg 1$ ,

$$T = \frac{I_0}{V_s} \approx \frac{1}{H} \quad (4.8.1)$$

as

$$H = \frac{V_f}{I_0} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \quad (4.8.2)$$

$$= \frac{100}{100 + 640 + 100} \times 100 = 11.9\Omega \quad (4.8.3)$$

thus,

$$T = \frac{1}{11.9} = 84mA/V \quad (4.8.4)$$

$$\frac{I_c}{V_s} \approx \frac{I_0}{V_s} = 84mA/V \quad (4.8.5)$$

which we note is very close to the approximate value found in (4.7.1)

4.9. Find  $R_{in}$  and  $R_{out}$  for circuit in fig.4.1.1

**Solution:**

$$R_{in} = R_{if} = R_i(1 + GH) \quad (4.9.1)$$

where  $R_i$  is the input resistance of the G circuit. The value of  $R_i$  can be found from the circuit in fig.4.5 as follows:

$$R_i = (h_{fe} + 1)(r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))) = 13.65K\Omega \quad (4.9.2)$$

$$R_{if} = 13.65(1 + 20.7 \times 11.9) = 3.38M\Omega \quad (4.9.3)$$

$$R_{of} = R_o(1 + GH) \quad (4.9.4)$$

where  $R_o$  can be determined to be

$$R_o = (R_{E2} \parallel (R_F + R_{E1})) + r_{e3} + \frac{R_{C2}}{h_{fe} + 1} \quad (4.9.5)$$

from values in Table 4.1, yields  $R_o = 143.9\Omega$ . The output resistance  $R_{of}$  of the feedback amplifier can now be found as

$$R_{of} = R_o(1 + GH) = 143.9(1 + 20.7 \times 11.9) = 35.6K\Omega \quad (4.9.6)$$

$R_{out}$  is found by using circuit4 in fig.4.5

$$R_{out} = r_{o3} + [R_{of} \parallel (r_{\pi3} + R_{C2})](1 + g_{m3}r_{o3} \frac{r_{\pi3}}{r_{\pi3} + R_{C2}}) \quad (4.9.7)$$

$$= 25 + [35.6 \parallel (5.625)][1 + 160 \times 25 \frac{0.625}{5.625}] = 2.19M\Omega \quad (4.9.8)$$

thus  $R_{out}$  is increased (from  $r_{o3}$ ) but not by  $(1+GH)$

4.10. put the obtained parameters in a table

**Solution:** ?? table gives us the calculated values

Parameter	Value
<b>G</b>	<b>20.7A/V</b>
<b>H</b>	11.9 $\Omega$
<b>T</b>	<b>83.7mA/V</b>
$V_o/V_s$	<b>-50.2V/V</b>
$R_{in}$	3.38M $\Omega$
$R_{out}$	2.19M $\Omega$
$R_{of}$	35.6k $\Omega$

TABLE 4.10: calculated parameters

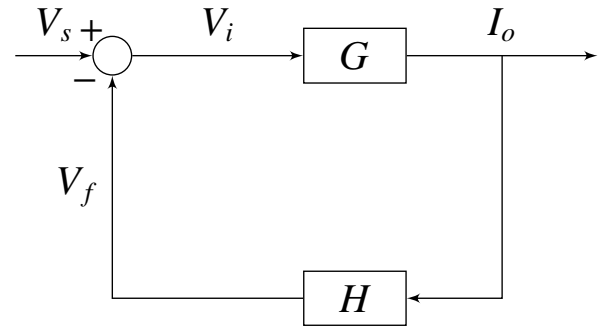


Fig. 4.11: block diagram

codes/ee18btech11007/circuit\_calc.py

4.11. Represent this amplifier in a control system Block Diagram

**Solution:** figure in fig.?? represents our control system

4.12. write a code for doing calculations and verify the values obtained in ??

**Solution:** following code does all the calculations of above equations to give parameters in ??